

Digital Logic


CO 2206 Computer Organization

Topics

- Analog vs Digital
- Digital Systems
- Logic Signal
- Integrated Circuit (IC)
- Logic Gates
- Boolean Algebra


Our Nature is Analog

- Real world is mainly *analog*: size, weight, color, illumination, feeling, senses, voltage, current, etc
 - we do not have a finite number of values; there is always a value in between two: what's between 2.001 and 2.002?
- Properties of *analog* signals:
 - varies smoothly between two extremes
 - has continuous range of values, i.e., it has infinite number of possible levels
 - is time-continuous

 

Analog vs Digital

 - Dealing with *analog* signals is demanding
 - infinite values to process (including compares)
 - how accurate can we get to?
 - how reliable (repetitive) can we get to?
- It will be easier to deal with signals having finite values
- ***Digital*** signal has the following properties:
 - has finite levels, i.e. discrete values
 - is time-discrete



Digital Systems

- Computer is a *digital system*
- *Advantages* of digital system:
 - Digital systems are easier to design because exact level/value is not important
 - Digital systems are less affected by noise. Digital signal can be reconstructed. Digital signals are more reliable.
 - The operation of a digital system/network is programmable
- *Disadvantage* of digital system :
 - The real world is mainly analog. There is a need of analogue-to-digital conversion.


Digital Logic

- Most digital system uses digital signal with two levels — called **logic level** :
 - *Logic 1* = High level
 - *Logic 0* = Low level
- This is called a **binary signal** or **logic signal**
 - *HIGH* and *LOW* are referred to as *Logic States*
- **Positive Logic** - *logic 1* has a voltage level more positive than that of *logic 0*
- **Negative Logic** - *logic 0* has a voltage more positive than that of *logic 1*
- We use *positive logic* throughout this course. It is most widely used.

Digital Electronic

(Digital Logic Circuits)

- *Electronic circuits* are analog in nature
- **Digital Logic Circuits** are electronic circuits designed to work on **digital logic signals** (voltage levels)
 - Computers are mainly build from logic circuits
- Usually, a band of voltage is used to represent each *logic level*. Commonly used logic signals are:
 - *TTL logic level* (for circuits using TTL technology):
 - Logic 1 = +2.0V — +5.5V
 - Logic 0 = -0.5V — +0.8V
 - *CMOS logic level* (for circuits using CMOS technology):
(at supply voltage of +5.0V):
 - Logic 1 = +3.5V — +5.5V
 - Logic 0 = -0.5V — +1.5V

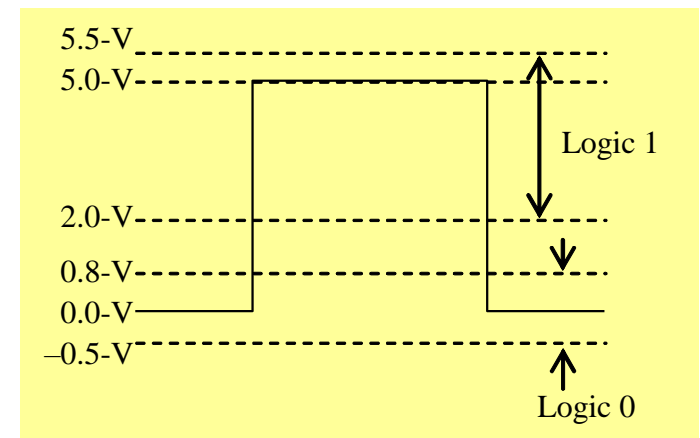

Integrated Circuit (IC) - 1

- *Digital logic circuit*, including *logic gates* are build from basic electronic components like resistors, capacitors, diodes and transistors
- Digital ***Integrated-Circuits (ICs)*** are a collection of resistors, diodes and transistors fabricated on a single piece of *semiconductor* material (usually *Silicon*) called a *Substrate*, which is commonly referred to as a “*chip*”
- *Logic gates* and *logic systems* usually come in *IC* forms

Integrated Circuit (IC) - 2

- *Advantages* of *IC*:
 - *IC* packs a lot more circuitry than discrete-component-circuit in a small package, so that the overall *size* of almost any digital system is reduced
 - *IC* is *cheaper* to produce, than discrete-component-circuit, in large volume
 - *IC* is more *reliable* than discrete-component-circuit because it reduces the number of external interconnections (soldered connections) from one device to another
 - *IC* has *reduced power consumption* and so it will reduce power supply costs and requirement for cooling

Levels of Integration


SSI	Small-scale	10+ transistors	Basic gates, flip-flops
MSI	Medium-scale	100+	Decoder, register, counter
LSI	Large-scale	10,000+	Small memory, microprocessor
VLSI	Very large-scale	100,000+	microprocessor, memory
ULSI	Ultra large-scale	1,000,000+	latest processors

- Being the most important component in *IC*, **transistors** are *electronic switches*, responsible for generating the *logic levels* (*ON* or *OFF*)
- *Intel 8086* has about *29k* transistors; *Pentium* > *3M* transistors


Moore's Law

- **Gordon Moore** observed in 1965 that the no. of transistors on a chip was doubling every year
- Development slowed down since 1970s
 - Until 1990s, transistor count doubled every 18-24 months
 - In 1990s, doubling about every 2.5 years
- Cost of a chip has remained almost unchanged

Growth in CPU transistors count

 

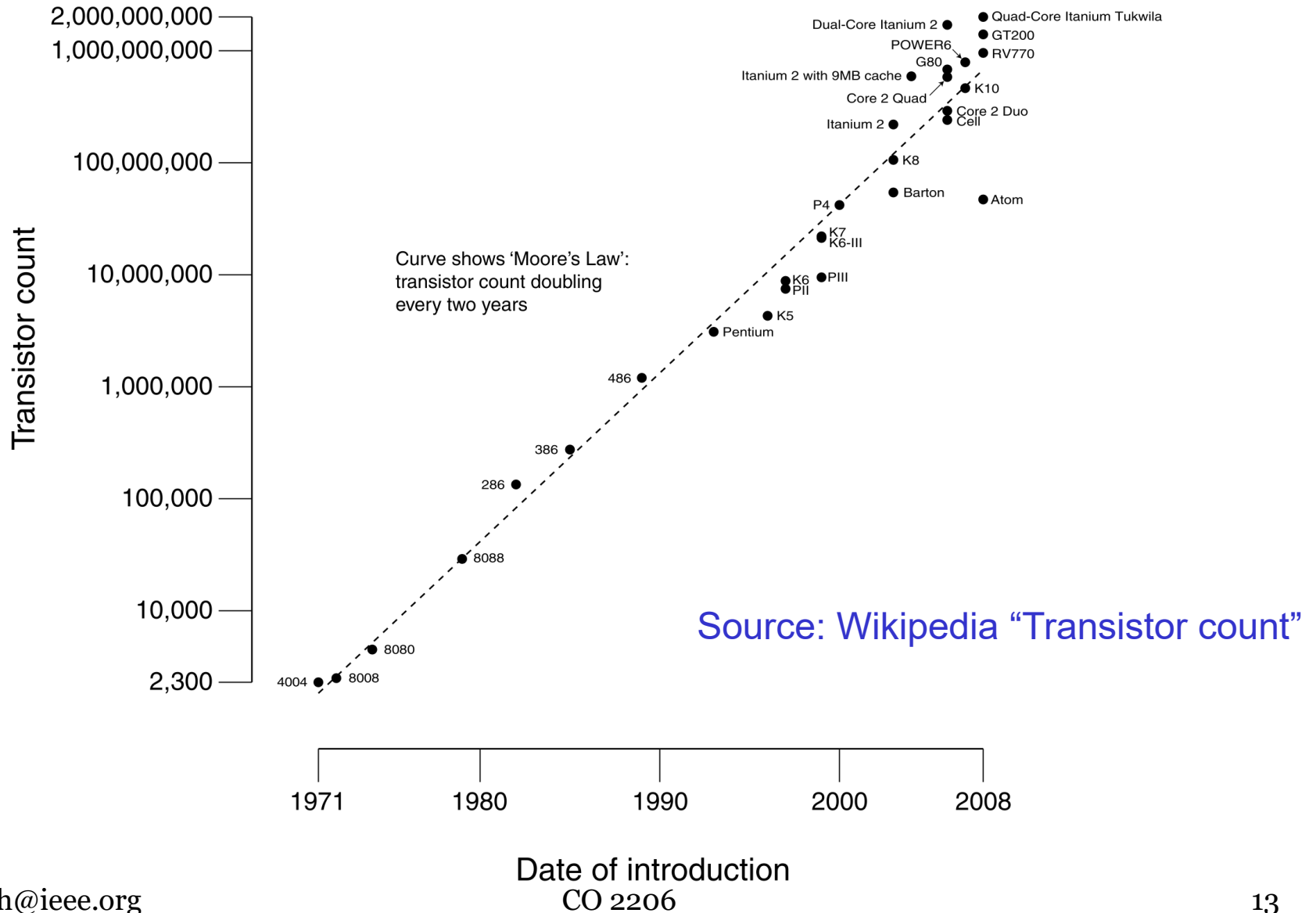CPU Transistor Counts 1971-2008 & Moore's Law



Logic Gates


- **Logic Gates** are basic building blocks for *digital logic circuits*
 - *Logic gate* is a circuit that may have a number of inputs but has only one output that will be either logic 1 or logic 0 as determined by the condition of the inputs
- Two types of *representation* for *logic gates*:
 - *International Symbol* (MIL, ANSI)
 - *British Standards Institute Symbol* (BSI)
- **ANSI** is more commonly used compared to **BSI**
 - **ANSI** representation will be used throughout the course

Logic Families


- There are different technologies used to fabricate digital ICs. They are referred to as **logic families**. Popular logic families are:
 - *Transistor-transistor logic (TTL)*
 - *Complementary metal oxide semiconductor (CMOS)*
 - *Emitter coupled transistor logic (ECL)*
- Each **logic family** has a different set of characteristics. For example:
 - *ECL* is the fastest
 - *CMOS* has low power consumption but slow
 - *TTL* is a compromise between the two

Logic Gate ICs

 - Logic gates come in multiple form in commercial *ICs*, i.e. an *IC* contains more than one gate.
 - e.g. *OR* gate can come in the form of *Quad 2-input OR*, *Dual 4-input OR* or *Triple 3-input OR*.
- Digital *ICs* normally come in the form of *14 pins Dual-In-Line (DIL)* package or *16 pins DIL ICs*.



 - (c) 24-pin DIL
- (b) 20-pin DIL
- (a) 14-pin DIL




TTL NAND gates ICs

Basic Logic Gates - 1


- **Basic Logic operations:**
 - AND, OR, NOT, Exclusive OR (XOR)
- **AND**

Truth Table

Inputs		Output
A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

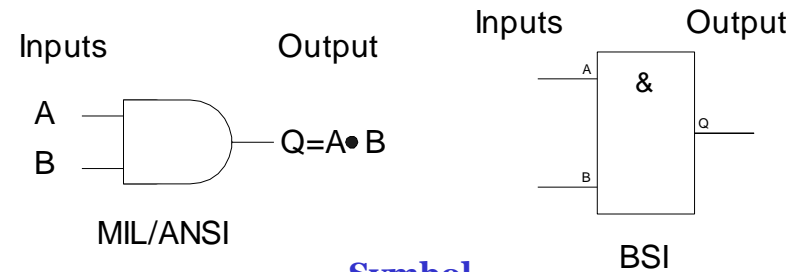

Symbol

 


Illustration

Basic Logic Gates - 2


- OR**

Truth Table

Inputs		Output
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

 

Symbol

 


Illustration

Basic Logic Gates - 3


- NOT**

Truth Table

Input	Output
A	Q
0	1
1	0

 

Symbol

 


Illustration

Basic Logic Gates - 4


- XOR**

Truth Table

Inputs		Output
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

 

Symbol

 



Derived Logic Gates

- Derived Logic operations:

- NAND (Not-AND)



- NOR (Not-OR)

- NAND**

  

Inputs		Output
A	B	
0	0	1
0	1	1
1	0	1
1	1	0




- NOR**

  

Inputs		Output
A	B	
0	0	1
0	1	0
1	0	0
1	1	0


Universal Gates - 1

   - *NAND* and *NOR* gates are called **universal gates** because any logical function can be implemented using only *NAND* or *NOR* gates
- Implementations of *AND*, *OR* and *NOT* gates using only *NAND*:



Universal Gates - 2

 
- Implementation of *AND*, *OR* and *NOT* gates using only *NOR*



OR gate



NOT gate

 

AND gate

Boolean Algebra

- Analysis of logic networks is greatly aided by the logical algebra developed in the last century by *George Boole*, an English mathematician.
- The ***theorems of Boolean algebra*** are used to simplify digital logic networks in much the same fashion that mathematical algebra is used to manipulate ordinary algebraic expressions.
 - the variables in *Boolean expressions* can assume only one of two possible values

Boolean Notation


- **Boolean notation** is an “arithmetic” symbol used to represent the logic operations *AND*, *OR*, *NOT* and *XOR*
 - the “•” (*AND*) notation is sometimes omitted, for example, $Q=A \bullet B$ is sometimes written as $Q=AB$

Logic Operation	Boolean Notation
<i>AND</i>	•
<i>OR</i>	+
<i>NOT</i>	bar over the input variable, e.g. \bar{A}
<i>XOR</i>	\oplus

Describing Logic Circuit

- A logic circuit can be described in *three ways*:
 - *circuit schematic*
 - *truth table*
 - *Boolean expression*


Inputs			Output
A	B	C	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 

Boolean Expression

(aka Logical Expression)

- **Boolean expression** is an alternative way of describing the behaviour of a logic gate or a logic network besides the *truth table*
- A **Boolean expression** has three parts :
 - **Function** - *output* which we want to express
 - **Variables** - the *input* variables
 - *literals* are the variables and their inverted form
 - **Operators** - **Boolean notations** used to express the logic operations on the inputs

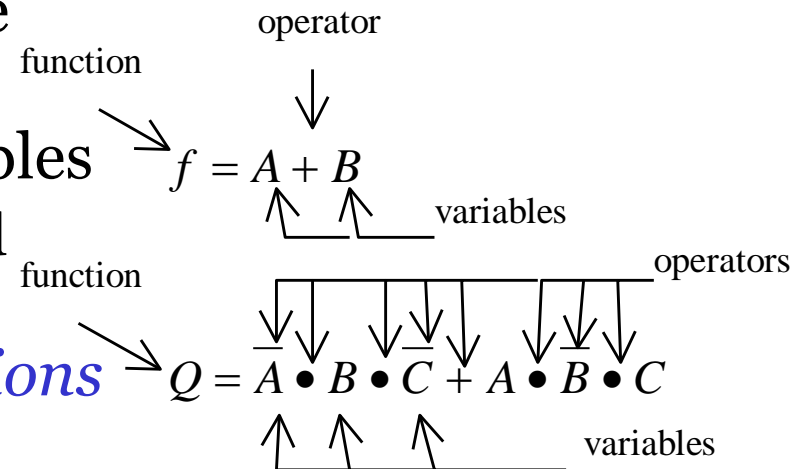

Boolean Algebra Laws – 1

(Theorems of Boolean Algebra)

law	<i>and</i> version	<i>or</i> version
Identity	$X \cdot 1 = X$	$X + 0 = X$
Complement	$X \cdot X' = 0$	$X + X' = 1$
Commutative	$X \cdot Y = Y \cdot X$	$X + Y = Y + X$
Idempotent	$X \cdot X = X$	$X + X = X$
Null	$X \cdot 0 = 0$	$X + 1 = 1$

Boolean Algebra Laws – 2

(Theorems of Boolean Algebra)

law	<i>and</i> version	<i>or</i> version
Distribution	$x \cdot (y + z) = (x \cdot y) + (x \cdot z)$	$x + (y \cdot z) = (x + y) \cdot (x + z)$
Involution	$(x')' = x$	-
Absorption	$x \cdot (x + y) = x$	$x + (x \cdot y) = x$
Associative	$x \cdot (y \cdot z) = (x \cdot y) \cdot z$	$x + (y + z) = (x + y) + z$
De Morgan's	$(x \cdot y)' = x' + y'$	$(x + y)' = x' \cdot y'$

XOR Identities

XOR: $x \oplus y = xy' + x'y$

XNOR: $(x \oplus y)' = xy + x'y$

Basic theorems

T1. $x \oplus x = 0$ T2. $x \oplus x' = 1$ T3. $x \oplus 0 = x$ T4. $x \oplus 1 = x'$

Inversion theorems

T5. $(x \oplus y)' = x' \oplus y = x \oplus y'$

T6. $x' \oplus y' = x \oplus y$

T7. $x \oplus y = y \oplus x$

T8. $(x \oplus y) \oplus z = x \oplus (y \oplus z)$

T9. $x(y \oplus z) = xy \oplus xz$

T9'. $x(y \oplus z) = (x'+y) \oplus (x'+z)$

T10. If: $f = g \oplus h$ and $gh = 0$, then $f = g + h$

T11. If: $f = g \oplus h$, then $g = f \oplus h$ and $h = g \oplus f$

Commutative law

Associative law

Distributive law

Distributive law with OR function

Disjunction theorem

Transposition theorem

Duality Principle

- **De Morgan's Duality Law** is useful in coming up with *NAND* or *NOR* based design
- **Duality** allows us to transform a law from *AND* version to *OR* version by replacing each **1** with **0**, **0** with **1**, **+** with **·**, and **·** with **+**
 - *Duality* principle states that a *Boolean* equation remains valid if we take the dual of the expressions on both sides of the equal sign.
 - Complement of a function can be derived by taking the dual and complement each literal

$$A = BC'D$$

$$A' = B'+C+D'$$

$$ABC = (A'+B'+C)'$$

$$A+B'+C = (A'BC)'$$

Logical Equivalence

- If 2 logical circuits are performing the same logical function, they are ***equivalent***
- Establishing equivalence is important because it allows us to pick an efficient design for ***implementation***
 - efficient here means using less number of gates
- Equivalence can be proved by ***truth table*** or by ***Boolean algebra rules***
 - proving equivalence can be from left to right, or right to left, whichever is more convenient

Summary

- Digital signals are easier and more reliable to deal with
- Logic signal is the most common digital signal
- Computer deals with digital logic signals and is a digital systems
- Basic building blocks of digital systems are the logic gates
- Logic gates are electronic circuits designed to deal with digital signals
- Logic gates are available in IC forms
- Boolean Algebra is a useful mathematical expression for describing logic functions, as well as manipulating the functions