

Logic Circuit Design

CO 2206 Computer Organization

Topics

- The Process
- Standard Forms
- Simplification techniques
 - Algebraic manipulation
 - Karnaugh Map (K Map)
 - Quine-McCluskey method
- Implementation matters
 - Circuit Implementation
 - 2-level implementations
 - XOR Implementation
 - Hi-Z and Enable


Introduction

- Logic circuits for digital systems may be
 - *Combinational logic circuit/network (CLN)*
 - *Sequential logic circuit/network (SLN)*

Combinational Logic

- **Combinational circuits**

 - Consist of logic gates whose **outputs** at any time are **determined** directly (and solely) from the **present combination of inputs**



- For n input variables, there are 2^n possible binary input combinations
- Combinational circuit can be described by m Boolean functions, one for each output variable

Sequential Logic

- Outputs of ***sequential circuits*** depend not only on present **inputs**, but also on **stored values** (states), which are a function of previously applied inputs
- Output determined by
 - **inputs**
 - **present state** of the storage elements
 - **‘previous’ outputs**

Logic Design Process

- A simple *logic design process* involves
 1. **Problem specification** - discover the *input and output requirement*
 2. **Problem formulation** – e.g. derive a *truth table* from the input and output requirement
 3. Derivation of **logical expression(s)** – e.g. from the *truth table*, derive the *Boolean expression*
 4. **Optimization** – in simplest is to *minimize* the *Boolean expression(s)* if necessary, however more to it (cost factors)
 5. **Implementation** - build the *circuit(s)* from the simplest *Boolean expression(s)*
- If there are more than one output, we treat each output as a separate design or circuit

Design Example: the Problem

- Access to a compound that contains dangerous high voltage equipment can be gained by a maintenance electrician under the following conditions:
 - The *high voltage* is *off* (*Logic 0*).
 - A keyswitch on the *control panel* 100 yards away is *off* (*Logic 0*).
 - A keyswitch on the *gate* is turned *on* (*Logic 1*).
- Under all the other conditions the gate cannot physically be opened.

Design Example: Solution - 1

- *Step 1: Discover the input and output requirements*
 - The input and output requirements are given in the question
- *Step 2: Derive a truth table from the input and output requirement*
 - Assignment input variables and output function.

A = High voltage

B = Control panel switch

C = Gate switch

Design Example: Solution - 2

- Conditions for entry : $Q=1$
 - Requirements are $A=0, B=0, C=1$
- truth table

A	B	C	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Design Example: Solution - 3


- *Step 3: From the truth table, derive the **Boolean expression***

$$Q = \overline{\overline{A}}BC$$

- *Step 4: **Minimize** the Boolean expression if necessary*

– There is only one possible output condition and the expression is in its simplest form

 - *Step 5: Build the **circuit** from the simplest Boolean expression*



Standard Forms

- *Standard forms* facilitate the simplification
- *Standard forms* contain
 - *Product terms*
 - e.g. $xy'z$
 - *Sum terms*
 - e.g. $x + y + z'$
- *Minterms*
 - Product terms in which all the variables appear exactly once, either primed or unprimed
- *Maxterms*
 - Sum terms in which all the variables appear exactly once

Deriving Logical Expression

- *Logical expression* can be expressed as:
 - *Sum of Minterms*
 - *Product of Maxterms*
- In *sum of minterms*
 - we specify combination inputs for which the output is 1
- In *product of maxterms*
 - we specify combination inputs for which the output is 0

Example - 1

- 3-input majority function

- *Sum of minterms*

$$F_1 = A'BC + AB'C + ABC' + ABC$$

$$F_1 = \Sigma m(3,5,6,7)$$

- *Product of maxterms*

$$F'_1 = (A+B+C) (A+B+C') (A+B'+C) (A'+B+C)$$

$$F'_1 = \Pi M(0,1,2,4)$$

The selected *minterm*, $A'BC$, will give an output of 1 when $A=0$, $B=1$, $C=1$.

The selected *maxterm*, $A'+B+C$, will give an output of 0 (hence F') when $A=1$, $B=0$, $C=0$.

A	B	C	F_1
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Example - 2

- 3-input even parity function

- *Sum of minterms*

$$F_2 = A'B'C + A'BC' + AB'C' + ABC$$

$$F_2 = \Sigma m(1,2,4,7)$$

- *Product of maxterms*

$$F'_2 = (A+B+C) (A+B'+C') (A'+B+C') (A'+B'+C)$$

$$F'_2 = \Pi M(0,3,5,6)$$


Note that the *maxterms* are expressed in inverted form, i.e. 000 = ABC and 111 = A'B'C'.

Whereas *minterms* are expressed non-inverted, i.e. 000 = A'B'C' and 111 = ABC

A	B	C	F ₂
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Straight Implementation

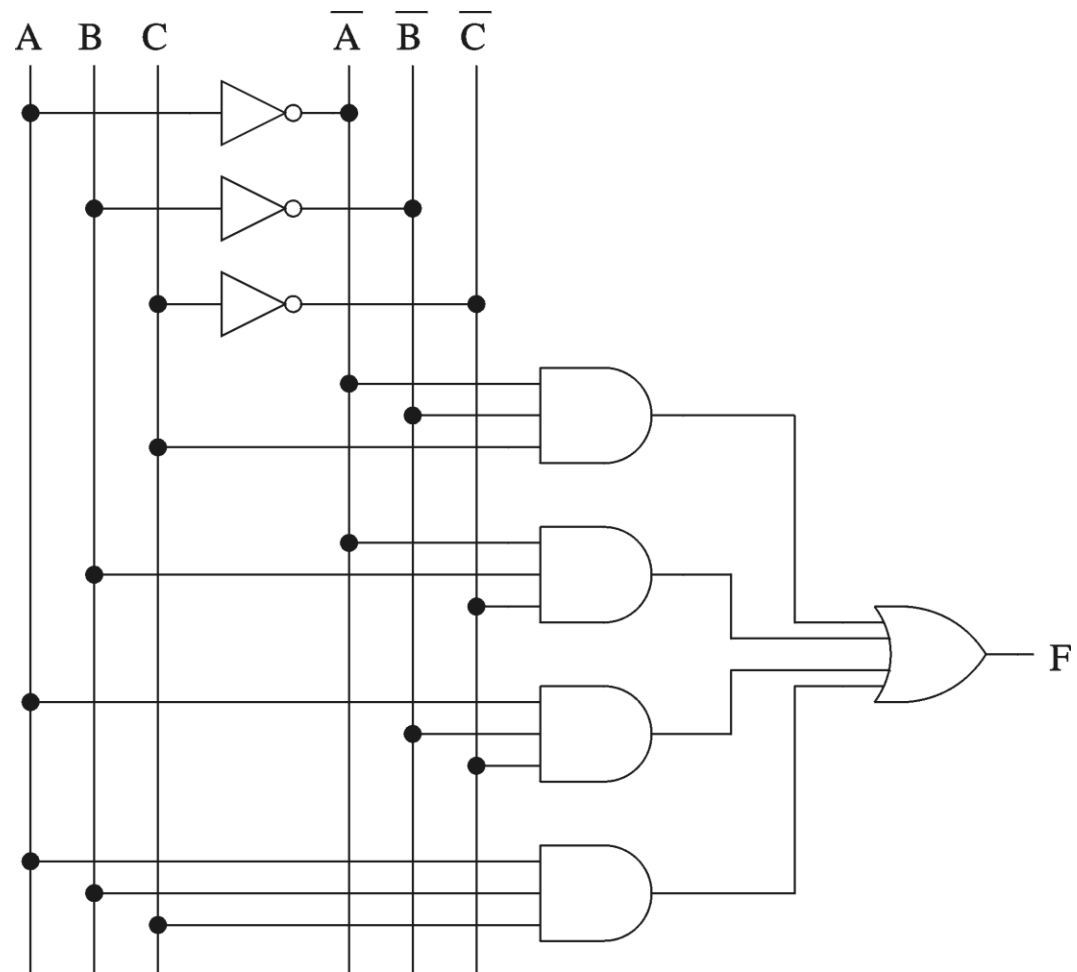- Implementing 3-input even parity function
 - from sum of *minterms*



Simplifying Logical Expression

- *Sum of minterms* and *product of maxterms* can be obtained directly from the truth table,
 - but the expression contains maximum number of literals (or variables) in each term and usually has more terms than necessary
- It may require simplification

Simplifying Techniques

- 3 techniques
 - *Algebraic manipulation*
 - Do not know if expression is in final simplified form
 - *Karnaugh map (K map)*
 - Graphical method suitable for expression with 4 or less number of variables
 - *Quine-McCluskey methods*
 - Tabular method for simplifying expression with large no. of variables
 - Can be automated (programmed)

Algebraic Manipulation

- Using *Theorems of Boolean Algebra*
 - no fixed steps to follow
 - requires good intuition and experience
 - inherent problem of which rule to apply

- Example:


$$\begin{aligned}F_1 &= A'BC + AB'C + ABC' + ABC \\ &= A'BC + AB'C + ABC' + ABC + ABC + ABC \\ &= A'BC + ABC + AB'C + ABC + ABC' + ABC \\ &= BC(A'+A) + AC(B'+B) + AB(C'+C) \\ &= BC + AC + AB\end{aligned}$$

Karnaugh Map - 1

- **Karnaugh Map** (pronounced *car-no*), like a *truth table*, is a mean for showing the relationship between logic inputs and the desired output
- *Karnaugh map* is usually abbreviated **K-map**. *K-map* can be used for problems involving *two-*, *three-*, *four-*, *five-* or *six-* different input variables
 - *K-map* for more than six-variable is practically impossible
 - Solving *five-* and *six-* variable *K-map* is extremely cumbersome; they can be more practically solved using advanced computer techniques
- In this course, we will only deal with *two-*, *three-* and *four-*variable *K-map*


K-Map Format - 1

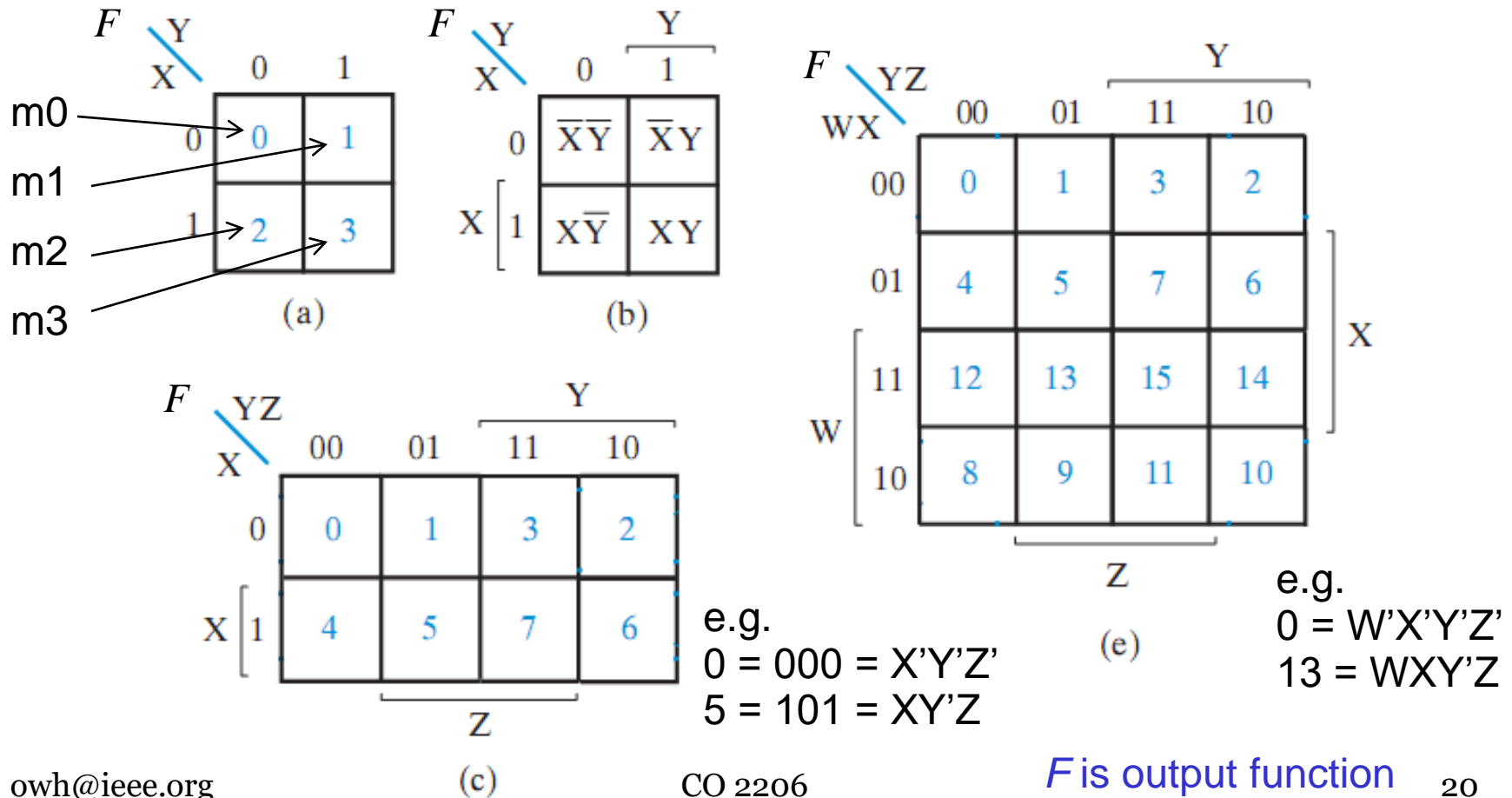- Size depends on number of input variables, 2, 3, 4



K-Map Format - 2

- *K-map* is a map describing all possible combinations of variables present in the logic function of interest
 - A *K-map* consists of 2^N cells, where N is the number of logic variables
 - each square represents one *minterm*
- *Minterms* are arranged in sequence similar to *Gray code*
- Any 2 adjacent cells differ by only one variable, which is primed in one cell and unprimed in another
- Possible to derive a number of algebraic expressions for the same function

 



K-Map Examples

Inputs			Output
A	B	C	Q
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

$\leftarrow \overline{\overline{ABC}}$
 $\leftarrow \overline{ABC}$
 $\leftarrow \overline{A\overline{B}C}$
 $\leftarrow \overline{A\overline{B}C}$
 $\leftarrow \overline{ABC}$
 $\leftarrow \overline{ABC}$
 $\leftarrow \overline{ABC}$
 $\leftarrow \overline{ABC}$
 \leftarrow

Inputs		Output
A	B	Q
0	0	1
0	1	0
1	0	0
1	1	1

  
$\leftarrow \overline{\overline{AB}}$
 $\leftarrow \overline{AB}$
 $\leftarrow \overline{A\overline{B}}$
 $\leftarrow \overline{AB}$



2-variable K-Map can be 2x4 or 4x2

From TT to K-Map

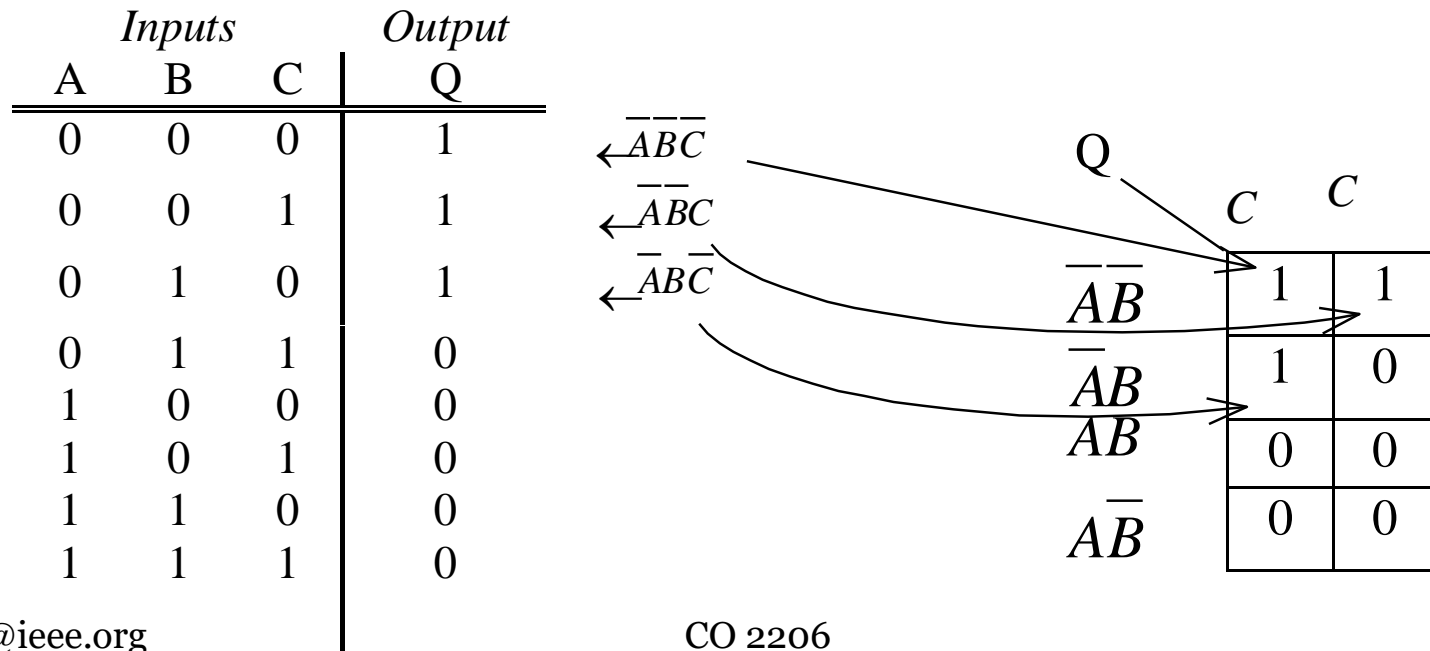- To transfer a *truth table* into a *K-map*, we simply transfer the output level for each case of the *truth table* into the corresponding cell in *K-map*



From Expression to K-Map - 1

- The following steps can be followed to transform *Boolean expression* into *K-map*
 - Express the *Boolean expression* into *Sum-Of-Product (SOP) expression*. For example

$$Q = \bar{A}(\bar{B}C + \bar{B}\bar{C}) + \bar{A}BC$$

$$= \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + \bar{A}BC \leftarrow SOP$$

product terms

$$Q = A(\bar{B} + C)$$

$$= A\bar{B} + AC \leftarrow SOP$$


product terms

Note the *product terms* need not be *minterms*

- Fill in each of the *cells* which has the *product terms* with a "1". See next slide for example.

From Expression to K-Map - 2

$$Q = \overline{A}\overline{B} + AC$$

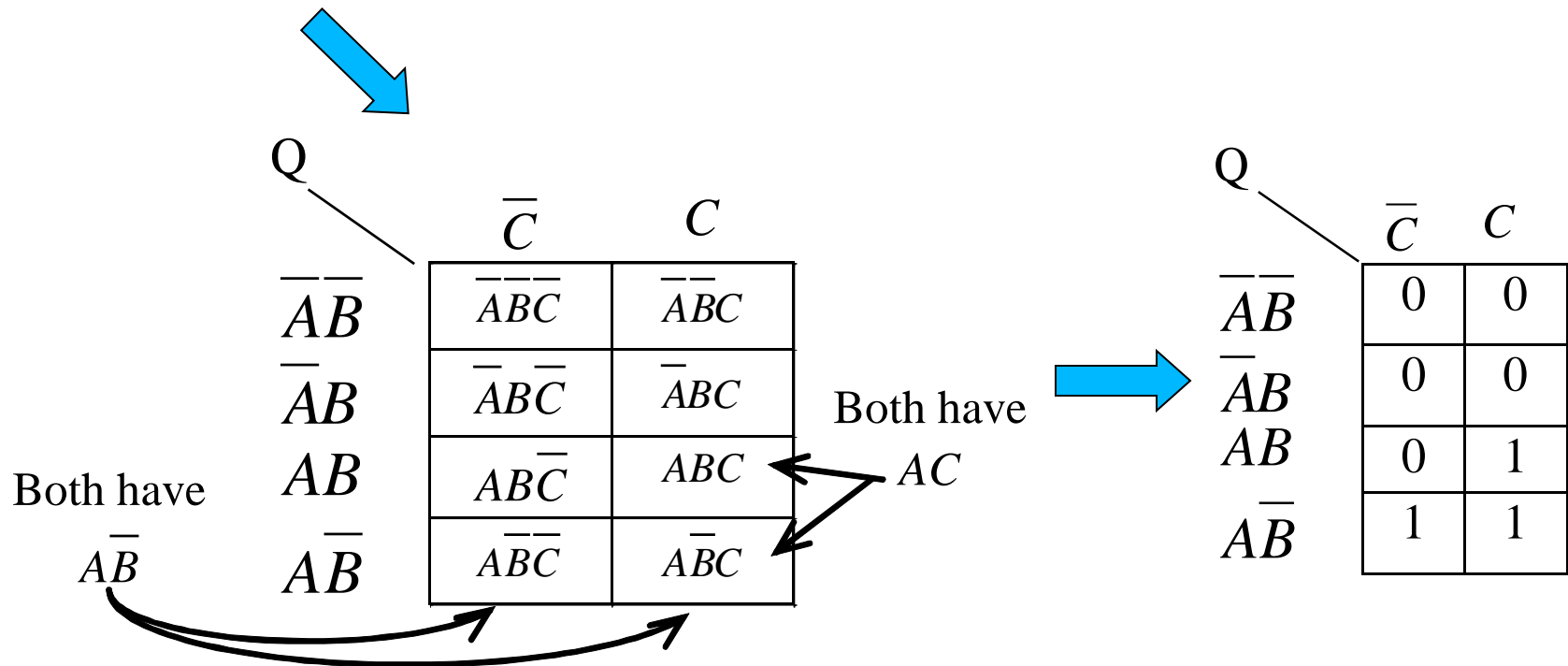

From Expression to K-Map - 3

- Alternatively, derive the *truth table* from the *expression* and then transfer the *truth table* to *K-map*

Simplest Expression from K-Map

- The following steps can be followed to obtain a simplest *Boolean expression* from the *K-map*:
 - Encircle *adjacent cells* filled with "1" in *groups* of 2, 4, 8, etc. (i.e. *power of 2*)
 - For each *group* or *circle*, find the *product term* which is common in all *cells* within the *group*.
 - The simplest expression is given by the *sum* of the *product terms* for all *groups*


Grouping Rules

- The following ***grouping rules*** should be followed:
 - the number of cells must be a power of 2 using the rule 2^N
 - the more *adjacent cells* encircled, the simpler the final expression will be; for the simplest expression the **maximum number** of cells must be grouped
 - a cell can appear in more than one group
 - cells must have a common edge, i.e. the map can be imagined as a sphere opened out (just like the map of the World) so that the *top edge is adjacent to the bottom edge* and the *right edge is adjacent to the left edge*
 - all the "1" should be encircled

Some Grouping Terms

- The following terms are associated with K-maps:
 - ***Pair*** – group of 2 cells (with 1 less variable in the product term, i.e. for 3-variable function, a *pair* will be a product term with 2 variables)
 - ***Quad*** – group of 4 cells (with 2 less variables)
 - ***Octet*** – group of 8 cells (with 3 less variables)
 - ***Redundant group*** – a group with all its 1's already in other groups

Example - Grouping

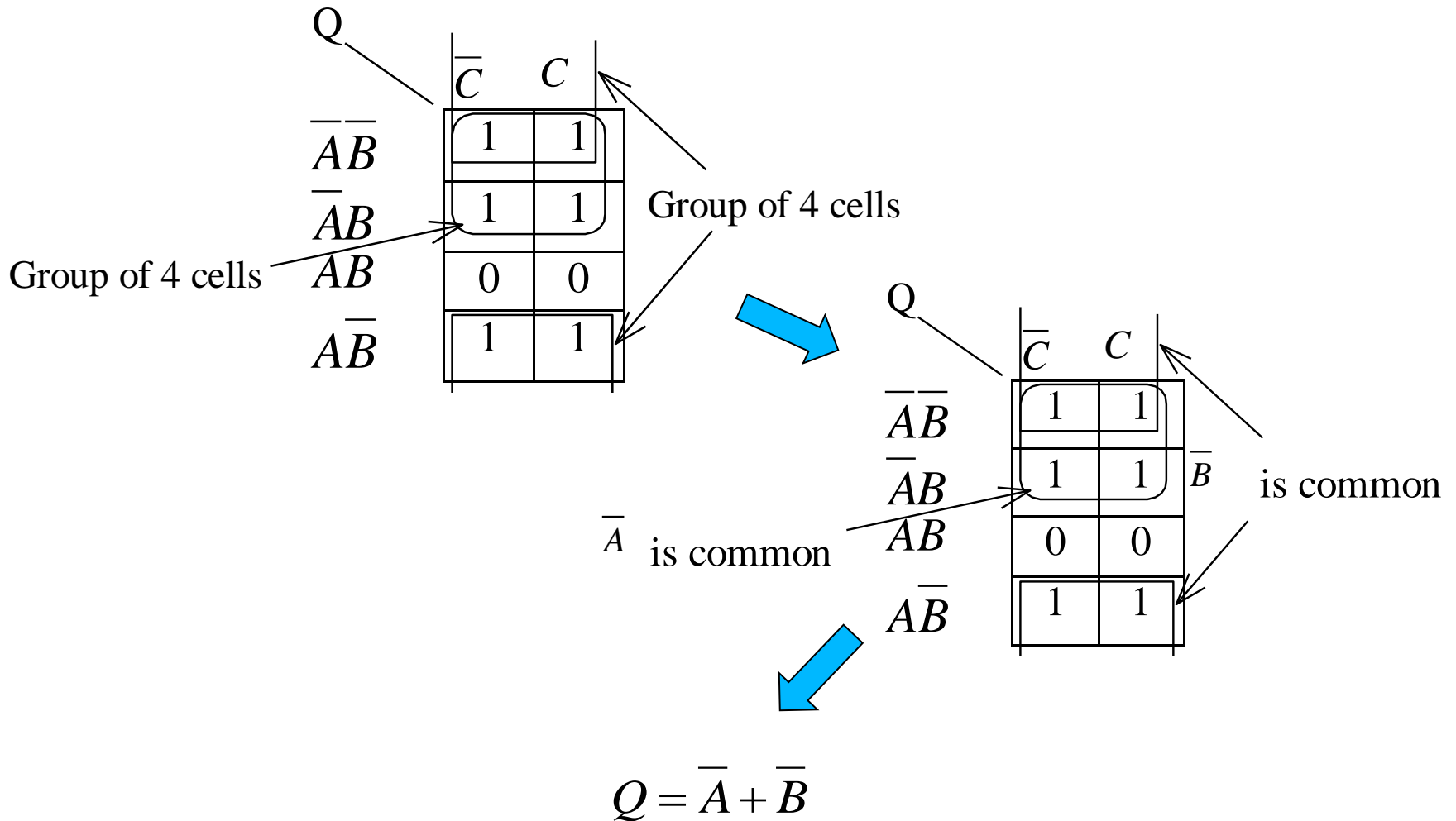

SOP Method

- In summary, the following steps, called **SOP Method**, are used to simplify *Boolean Equations*:
 - Enter a *1* on the *K-map* for each fundamental product that produces a *1* output in *truth table*. Enter *0* elsewhere.
 - Encircle the *octets*, *quads* and *pairs*. Remember to roll or overlap to get the largest groups possible
 - If any isolated *1* remains, encircle each
 - Eliminate any *redundant group*
 - Write the *Boolean Equation* by *ORing* the products corresponding to the encircled groups

3-variable Examples - 1

		yz		y	
		00	01	11	10
x	0			1	1
	1	1	1		

z


$$F_1 = xy' + x'y$$

		yz		y	
		00	01	11	10
x	0			1	
	1	1		1	1


z

$$F_2 = yz + xz'$$

3-variable Example - 2

 

$$F_3 = z' + xy'$$

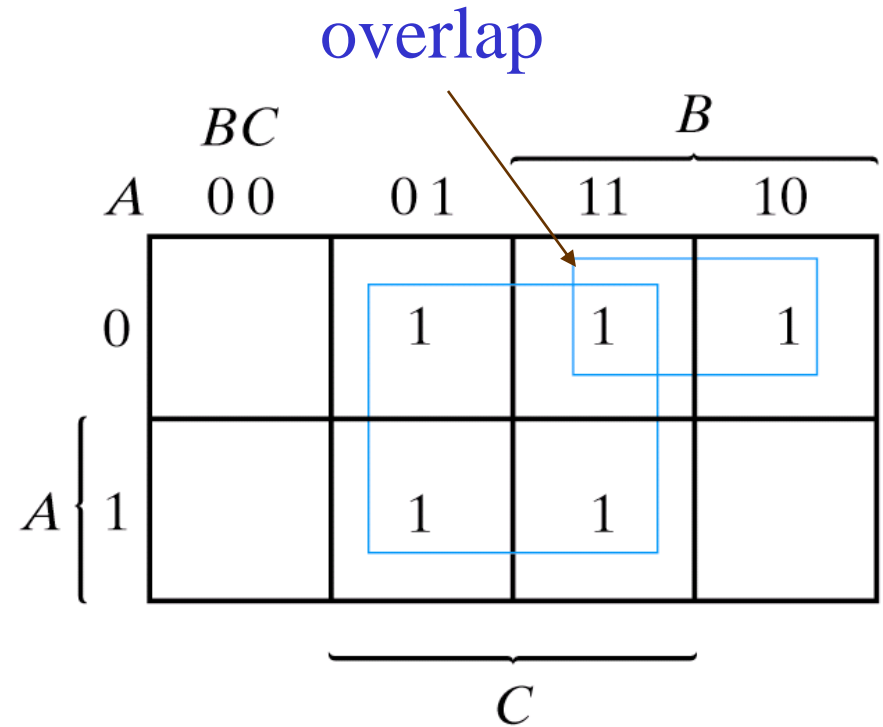


$$F_4 = C + A'B$$


3-variable Example - Observations

- More cells in the group, fewer literals in the product term
 - 1 cell represent 1 minterm, giving a term of 3 literals
 - 2 adjacent cells represent a term of 2 literals
 - 4 adjacent cells represent a term of 1 literal
 - adjacent cells encompass the entire map, function always equal to 1

4-variable Example - 1

 


$$F_5 = y' + w'z' + xz'$$

 


$$F_6 = B'D' + B'C' + A'CD'$$

4-variable Example - 2

 - Minimal expression will depend on groupings



(a)

 


(b)

More Examples

$$F_2 = A'B'C + A'BC' + AB'C' + ABC$$


(not all functions can be simplified)

 

 (a) Majority function

$$F_1 = AB + AC + BC$$

(before simplification: $F = A'BC + AB'C + ABC' + ABC$)



(b) Even-parity function

Essential Prime Implicants - 1

- On a *K map*, **prime implicants** correspond to all rectangles (groups) containing 1's
- If a *minterm* of a function is included in only one *prime implicant*, that *prime implicant* is said to be **essential**
- Optimised expression obtained from
 - Sum of all *essential prime implicants*, plus
 - Other *prime implicants* needed to include remaining minterms not included in the essential prime implicants

Essential Prime Implicants - 2

AB \ CD	CD			
	00	01	11	10
00	0	0	1	0
01	1	1	1	0
11	0	1	1	1
10	0	1	0	0

Diagram (a) shows a Karnaugh map with groupings: a vertical group of 1s in column CD=11 (AB=00, 01, 11); a horizontal group of 1s in row AB=01 (CD=00, 01, 11); a vertical group of 1s in column CD=01 (AB=01, 11); a horizontal group of 1s in row AB=11 (CD=11, 10); and a vertical group of 1s in column CD=01 (AB=11, 10). A blue arrow points from the word 'redundant' to the group in row AB=11, column CD=11.

(a) Nonminimal simplification **redundant**


AB \ CD	CD			
	00	01	11	10
00	0	0	1	0
01	1	1	1	0
11	0	1	1	1
10	0	1	0	0

Diagram (b) shows the same Karnaugh map with groupings: a vertical group of 1s in column CD=11 (AB=00, 01, 11); a horizontal group of 1s in row AB=01 (CD=00, 01, 11); a vertical group of 1s in column CD=01 (AB=01, 11); a horizontal group of 1s in row AB=11 (CD=11, 10); and a vertical group of 1s in column CD=01 (AB=11, 10).

 (b) Minimal simplification

Product of Sums – the Alternative

- Cells with 1's give F , cells with 0's give F'
- Combining squares marked with 0's
 - $F' = AB + CD + BD'$
- Taking the dual
 - $F = (AB + CD + BD')'$
 - $= (AB)'(CD)'(BD)'$
- Dual each product term
 - $F = (A'+B')(C'+D')(B'+D)$
- Note 1st and 2nd step can be skipped by observing that product term XY becomes sum term $X'+Y'$




Don't Care Conditions - 1

- In some applications, some outputs are not specified for certain combinations of variables because
 - The input combinations never occur
 - We do not care what the outputs are in response to the input combinations
- These outputs are unspecified and are called ***don't care conditions***

Don't Care Conditions - 2

 - “*Don't cares*” are marked ‘x’ in *K map* and may be assumed to be 0 or 1
 - assumptions are made in the way to produce simplest expression



Quine-McCluskey Method

- The **Quine-McCluskey** algorithm (or the method of prime implicants) is a method used for minimization of boolean functions which was developed by *W.V. Quine* and *Edward J. McCluskey*
- It is functionally identical to *K-map*, but the *tabular form* makes it more efficient for use in computer algorithms, and it also gives a deterministic way to check that the minimal form of a *Boolean* function has been reached
 - it is sometimes referred to as the **tabulation method**
- The method involves two major steps:
 - **Table** - finding all *prime implicants* of the function
 - **Chart** - use those *prime implicants* in a *prime implicant chart* to find the *essential prime implicants* of the function, as well as other *prime implicants* that are necessary to cover the function

Quine-McCluskey: the Table

	(a)		(b)		(c)
Group 0	$A'B'C'D'$	✓	$A'B'C'$		$B'D'$
Group 1	$A'B'C'D$	✓	$A'B'D'$	✓	$B'D'$
	$A'B'CD'$	✓	$B'C'D'$	✓	AC
	$AB'C'D'$	✓	$B'CD'$	✓	AC
Group 2	$AB'CD'$	✓	$AB'D'$	✓	
Group 3	$AB'CD$	✓	$AB'C$	✓	
	$ABCD'$	✓	ACD'	✓	
Group 4	$ABCD$	✓	ACD	✓	
			ABC	✓	

Quine-McCluskey: Step 1.1

- Specify the function in *Sum of Minterms*
- Group the *minterms* in accordance to “number of true conditions (1’s)” and arranged in a column (a). Example:
 - $a'b'c'd' \equiv 0000$ (no 1’s) is in group 0
 - $a'b'c'd \equiv 0001$ (one 1’s) is in group 1
 - $ab'cd' \equiv 1010$ (two 1’s) is in group 2, etc
- *First iteration*: remove one variable from the *minterms* by looking at a pair of terms in *adjacent groups* that contain a variable and its complement e.g. $a'b'c'd' + a'b'c'd = a'b'c'$
 - equivalent to forming group of size 2 in *K-map*


Quine-McCluskey: Step 1.2

- From the first iteration:
 - a set of product terms (with one less variable) is generated
 - these product terms are grouped in number of true conditions (1's) and arranged in next column (b)
 - terms not simplified in the first iteration will be left in column (a).
- *Second iteration*: remove one variable from the terms in (b) by looking at a pair of terms in *adjacent groups* that contain a variable and its complement e.g. $a'b'c' + a'bc' = a'c'$
 - equivalent to forming group of size 4 (2x2) in *K-map*
 - a set of product terms (with one less variable) is generated
 - these product terms are grouped in number of true conditions (1's) and arranged in next column (c)
 - terms not simplified in this iteration will be left in column (b)

Quine-McCluskey: Step 1.3

- Continue the iteration until no further reduction (in variable) can be done. In each iteration:
 - tick those terms that have been reduced
 - cross (remove) duplicating terms generated in each iteration
 - leave those terms that cannot be reduced unticked
- The outcome of the iterations is a table, where each column to the right has one less variable (reduction)
 - those terms not ticked are the *prime implicants*
- The next step is to draw the *Prime Implicant Chart*

Quine-McCluskey: the Chart

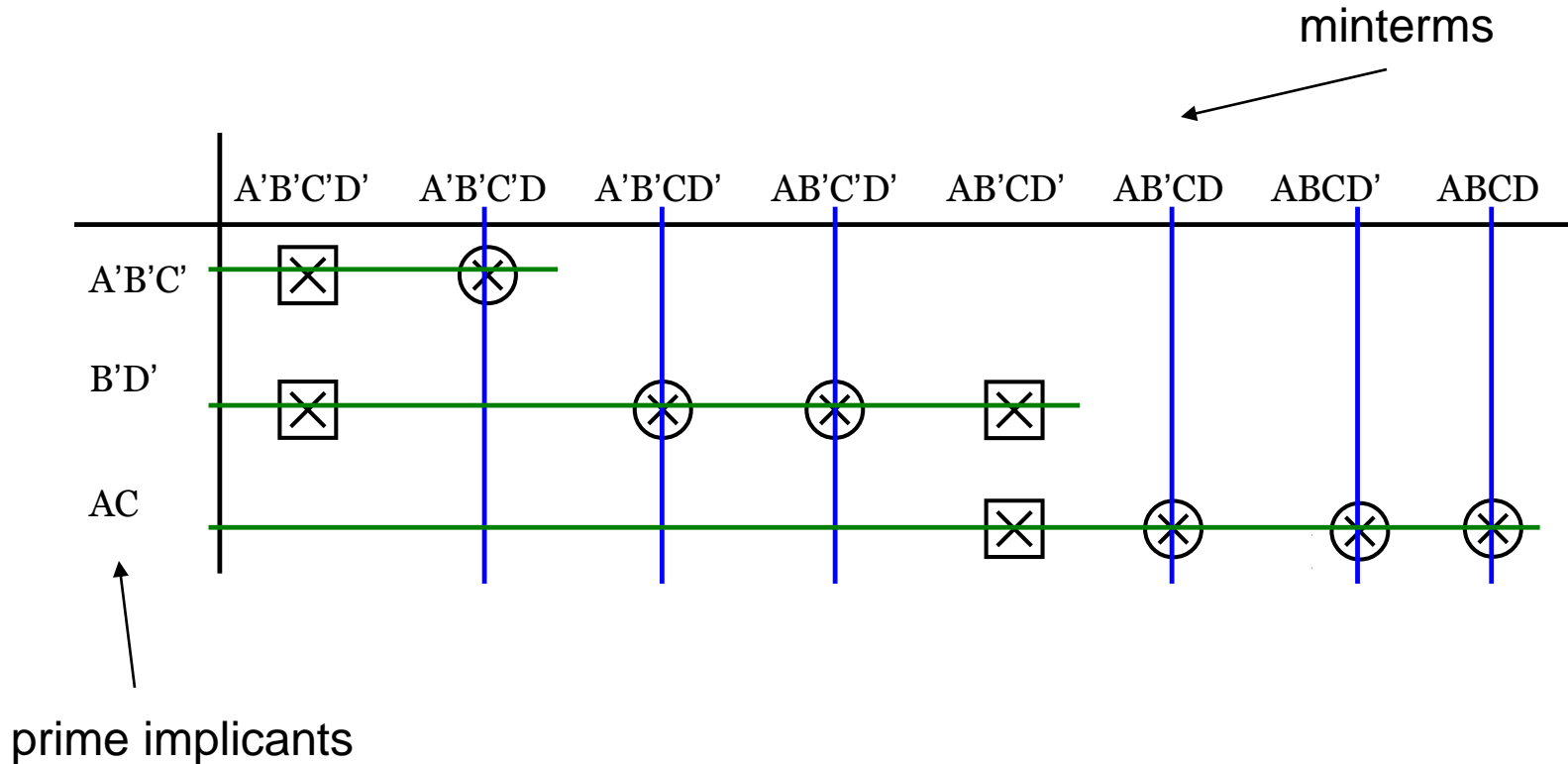


Quine-McCluskey: Step 2.1

- One row for each *prime implicant*
- One column for each *minterm* in original expression
- Mark \times where *prime implicant* for row is in column terms
- Circle each \times that is alone in a column. These are *essential prime implicants* that must appear in any final simplified expression.
- Place a square around all \times in a row that has a \otimes . This indicates those *minterms* with \boxtimes under it (as in column) has been included together with the *essential prime implicants* (those marked \otimes).

Quine-McCluskey: Step 2.2

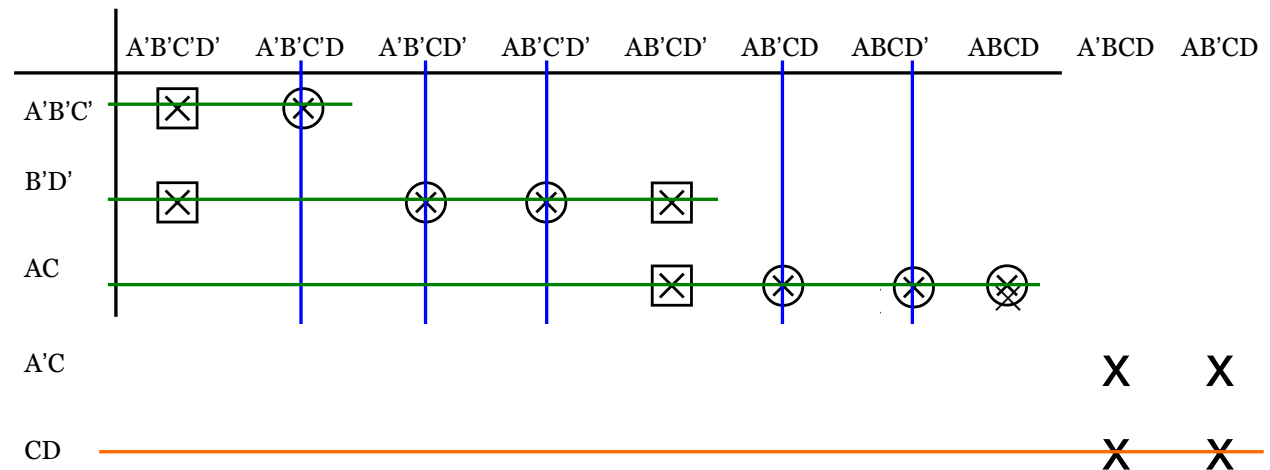- If there are columns without a \otimes or \boxtimes
 - select a minimum number of *prime implicants* to cover these columns
- To incorporate *don't care* conditions
 - include the *don't care* terms in the 1st step (table) and then ignore them as we apply the 2nd step (chart)



Quine-McCluskey Example

- Simplify $F = \Sigma m(0,1,2,8,10,11,14,15)$

no.		ABCD		min	group
0	=	0000	≡	$A'B'C'D'$	0
1	=	0001	≡	$A'B'C'D$	1
2	=	0010	≡	$A'B'CD'$	1
8	=	1000	≡	$AB'C'D'$	1
10	=	1010	≡	$AB'CD'$	2
11	=	1011	≡	$AB'CD$	3
14	=	1110	≡	$ABCD'$	3
15	=	1111	≡	$ABCD$	4

Quine-McCluskey Example: Table

(a)				(b)		(c)	
Group 0	0	A'B'C'D'	✓	A'B'C' (0,1)		B'D'	
Group 1	1	A'B'C'D	✓	A'B'D' (0,2)	✓	B'D'	
	2	A'B'CD'	✓	B'C'D' (0,8)	✓	AC	
	8	AB'C'D'	✓	B'CD' (2,10)	✓	AC	
Group 2	10	AB'CD'	✓	AB'D' (8,10)	✓		
Group 3	11	AB'CD	✓	AB'C (10,11)	✓		
	14	ABCD'	✓	ACD' (10,14)	✓		
Group 4	15	ABCD	✓	ACD (11,15)	✓		
				ABC (14,15)	✓		

Quine-McCluskey Example: Chart

	A'B'C'D'	A'B'C'D	A'B'CD'	AB'C'D'	AB'CD'	AB'CD	ABCD'	ABCD
A'B'C'	☒	⊗						
B'D'	☒		⊗	⊗	☒			
AC					☒	⊗	⊗	⊗

$$F = A'B'C' + B'D' + AC$$

Quine-McCluskey Exercise

- Simplify

$$F(A,B,C,D,E) = \Sigma m(0,1,4,5,16,17,21,25,29)$$

Quine-McCluskey Exercise: Table

0 A'B'C'D'E' *	0 A'B'C'D' *	0 B'C'D'
1 A'B'C'D'E' *	A'B'D'E' *	A'B'D'
A'B'CD'E' *	B'C'D'E' *	B'C'D' -
AB'C'D'E' *	1 A'B'D'E' *	A'B'D' -
2 A'B'CD'E' *	B'C'D'E' *	B'C'D' -
AB'C'D'E' *	A'B'CD' *	1 B'D'E
3 AB'CD'E' *	AB'C'D' *	B'D'E -
ABC'D'E' *	2 B'CD'E' *	2 AD'E
4 ABCD'E' *	AB'D'E' *	AD'E -
	AC'D'E' *	
	3 ACD'E' *	
	ABD'E' *	

Quine-McCluskey Exercise: Chart

	A'	A'	A'	A	A'	A	A	A	A	A
	B'	B'	B'	B'	B'	B'	B'	B	B	B
	C'	C'	C	C'	C	C'	C	C'	C	C
	D'	D'	D'	D'	D'	D'	D'	D'	D'	D'
	E'	E	E'	E'	E	E	E	E	E	E
B'C'D'	x	x		x		x				
A'B'D'	x	x	x		x					
B'D'E		x			x	x	x			
AD'E						x	x	x	x	

$$F = B'C'D' + A'B'D' + AD'E$$


Implementation

- Simple circuit can be directly implemented (from the expression)
- Technology mapping
 - Transform the logic diagram or netlist to a new diagram or netlist that implementation technology supports, e.g. NAND
 - Optimization and mapping may repeat multiple times to meet technology specifications, e.g. e.g. gate cost, gate delay, fan-out limits, etc
- Verification
 - Verify the correctness of final design

2-Level Implementations - 1

- Implementation can be directly using the *Sum-of-Product* (SOP) function, which is a *2-level AND-OR implementation*: the *AND* gates generates the *product terms*, which the outputs are summed by an *OR* gate

- e.g. $F = xy' + x'y + z$

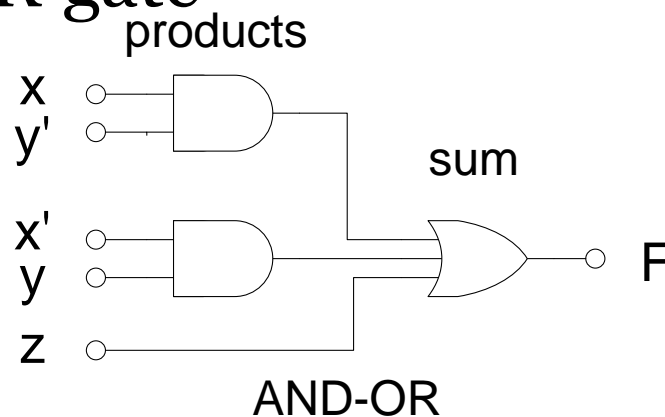

NOT gates are required to implement the inverted literals, however they are not usually considered a level

2-Level Implementations - 2

- By converting SOP into other forms, including POS, *2-level implementations* can be either:
 - AND-OR from SOP
 - NOR-OR
 - NAND-NAND
 - OR-NAND
 - AND-NOR
 - NOR-NOR
 - NAND-AND
 - OR-AND from POS

An Example Function

F	yz	y'z'	y'z	yz	yz'
X	00	01	11	10	
X'	0 0	1 1	3 1	2 1	
X	4 1	5 1	7 1	6 0	

$$F = xy' + x'y + z$$


$$F' = x'y'z' + xyz'$$

F	yz	y'z'	y'z	yz	yz'
X	00	01	11	10	
X'	0 0	1 1	3 1	2 1	
X	4 1	5 1	7 1	6 0	


From F to other forms - 1

- By applying *De Morgan's Duality*, F can be converted into three other forms for *2-level implements*:
 - original F
 - $F = xy' + x'y + z$ (AND-OR)
 - applying duality to each product term in original F
 - $F = (x' + y)' + (x + y')' + z$ (NOR-OR)
 - applying duality to both side of original F
 - $F' = (xy' + x'y + z)' = (xy')'(x'y)'z'$
 $F = ((xy')'(x'y)'z')'$ (NAND-NAND)
 - applying duality on each product term of NAND-NAND function
 - $F = ((x' + y)(x + y')z')'$ (OR-NAND)


From F to other forms - 2

 


AND-OR

 

NAND-NAND

 

NOR-OR




 


OR-NAND


From F' to other forms - 1

- By applying *De Morgan's Duality*, F' can be converted into four different forms for *2-level implements*:
 - original F'
 - $F' = x'y'z' + xyz'$
 - $F = (x'y'z' + xyz')'$ (AND-NOR)
 - applying duality to each product term in AND-NOR function
 - $F = ((x+y+z)' + (x'+y'+z))'$ (NOR-NOR)
 - applying duality to AND-NOR function
 - $F = (x'y'z')'(xyz)'$ (NAND-AND)
 - applying duality to each term in NAND-AND function
 - $F = (x+y+z)(x'+y'+z)$ (OR-AND)

From F' to other forms - 2

 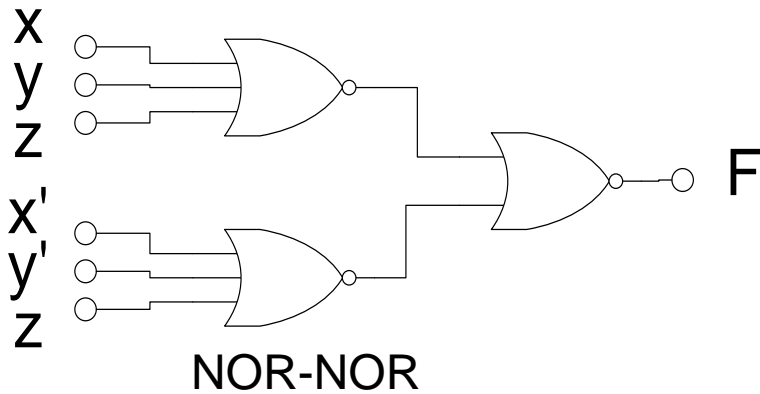 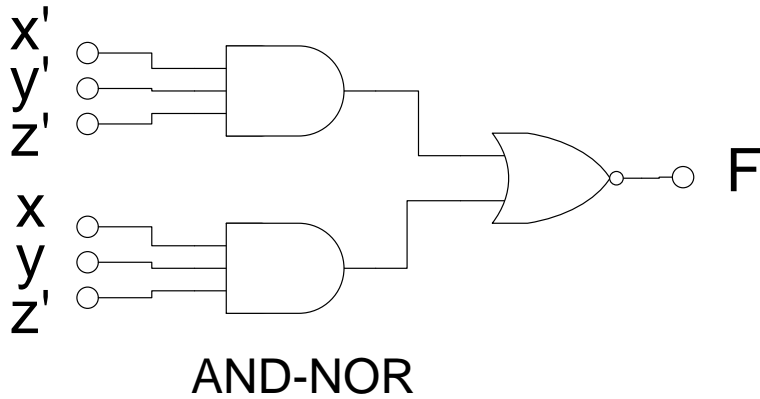


Duality on Logic Gate

 

Technology Mapping


- Mapping to NAND or NOR

 


(a) Mapping to NAND gates

 (b) Mapping to NOR gates

- Fine tuning the circuit for optimization with the selected technology



(c) Pushing an inverter through a "dot"




 


(d) Cancelling inverter pairs

Technology Mapping: NAND


- NAND technology
 - Consists of a collection of cell types
 - each of which includes a NAND gate with fixed number of inputs
 - the cells have numerous properties
 - e.g. propagation delay, fan-in, fan-out, etc
- E.g. Implement $F = AB + (AB)'C + (AB)'D' + E$ with NAND gates
 - next slide

NAND Example

    

NOR Example

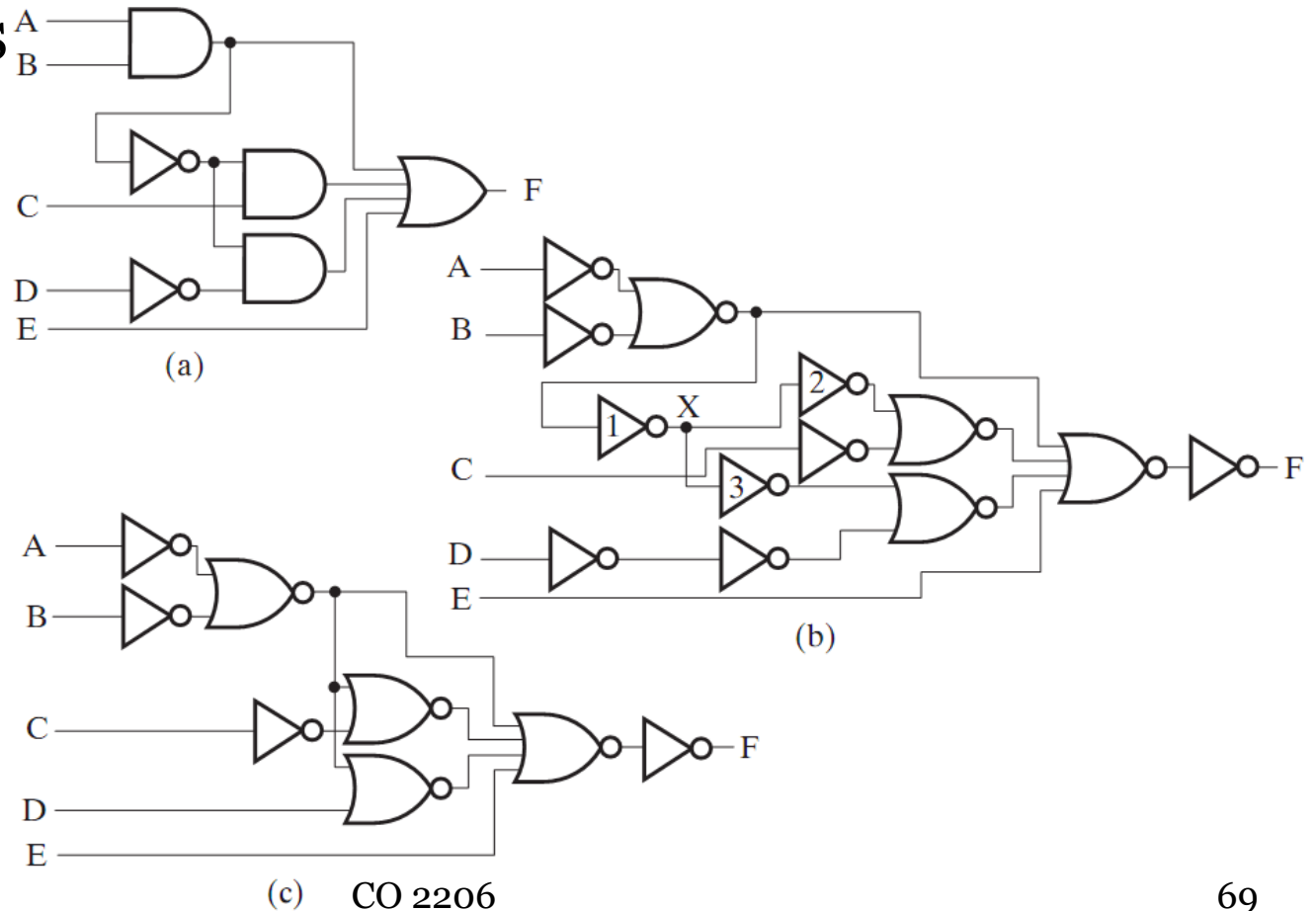- Implement $F = AB + (AB)'C + (AB)'D' + E$ with NOR gates




NAND vs NOR

- Comparisons
 - Gate-input cost
 - NAND implementation is 12
 - NOR implementation is 14
 - Gate delay
 - NAND – max. 3 gates in series
 - NOR – max. 5 gates in series
 - So for the e.g. NAND circuit is superior to NOR circuit in both cost and delay

Implementation using XOR

 - If the true conditions (1's) in a K-map is scattered, it may be difficult to obtain a simple expression. An example is the even parity function earlier.



(b) Even-parity function

- However, it may be possible to obtain simplified expression using XOR operators

XOR Identities

XOR: $x \oplus y = xy' + x'y$

XNOR: $(x \oplus y)' = xy + x'y$

Basic theorems

T1. $x \oplus x = 0$ T2. $x \oplus x' = 1$ T3. $x \oplus 0 = x$ T4. $x \oplus 1 = x'$

Inversion theorems

T5. $(x \oplus y)' = x' \oplus y = x \oplus y'$

T6. $x' \oplus y' = x \oplus y$

T7. $x \oplus y = y \oplus x$

T8. $(x \oplus y) \oplus z = x \oplus (y \oplus z)$

T9. $x(y \oplus z) = xy \oplus xz$

T9'. $x(y \oplus z) = (x'+y) \oplus (x'+z)$

T10. If: $f = g \oplus h$ and $gh = 0$, then $f = g + h$

T11. If: $f = g \oplus h$, then $g = f \oplus h$ and $h = g \oplus f$

Commutative law

Associative law

Distributive law

Distributive law with OR function

Disjunction theorem

Transposition theorem

XOR general properties

- Multiple-variable XOR operation is defined as an *odd function*
 - Function equal 1 if odd number of variables equal 1
- *Even function*
 - Even number of variables is equal to 1
 - Complement of odd function

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

3 variable XOR

XOR function from K-map

- In view of XOR properties, the following rules enable determining of XOR function from K-map:
 - there must be overlap of the groups
 - cells with true condition (1) must be encircled odd number of times (includes one time)
 - cells with false condition (0) must be encircled even number of times (includes zero time)

F	y'	y
x'	0	1
x	1	0

$$F = x \oplus y$$

XOR function examples - 1

F	$y'z'$	$y'z$	yz	yz'
x'	0	1	0	1
x	0	0	1	1

$$F = y \oplus x'z$$

F	$y'z'$	$y'z$	yz	yz'
x'	0	0	1	0
x	0	1	1	1

$$F = xz \oplus xy \oplus yz$$

XOR function examples - 2

F	$y'z'$	$y'z$	yz	yz'
$w'x'$		1	1	
$w'x$			1	1
wx	1	1		1
wx'	1			

$$F = w \oplus x'z \oplus xy \oplus wyz'$$

XOR function illustrations

- Start by plotting (encircle) variable **a** as shown in (b)
 - this covers three of the 1s in the map but places an additional 1 (in grey) at position **abc**
- Next plot variable **c** as shown in (c)
 - this cancels the extra 1 at **abc**, covers the 1s at position **a'bc** and **a'b'c** but cancels the 1 at position **ab'c**
- To regain a 1 at this position we place an additional 1 there and map that position as shown in (d)

	c	0	1	1
a	b	0	1	0
0			1	1
1		1	1	1

(a)

	c	0	1	1
a	b	0	1	0
0			1	1
1		1	1	1

(b)

	c	0	1	1
a	b	0	1	0
0			1	1
1		1	1	1

(c)

	c	0	1	1
a	b	0	1	0
0			1	1
1		1	1	1

(d)


$$y = a \oplus c \oplus ab'c$$

High-Impedance Output

- Gates may produce a third output value known as high-impedance state, Hi-Z, Z or z
- Hi-Z behaves as an open circuit, thus output appears to be disconnected
 - allows the output of a logic circuit to be disconnected from the main circuit
- Gates with Hi-Z output can have their outputs connected together
 - Provided that no 2 gates drive the line at the same time to opposite 0 and 1 values

Three-State Buffers - 1

 - Tri-state buffer is distinguished from normal buffer by the *enable* input




(a) Logic symbol

EN	IN	OUT
0	X	Hi-Z
1	0	0
1	1	1

(b) Truth table

Three-State Buffers - 2

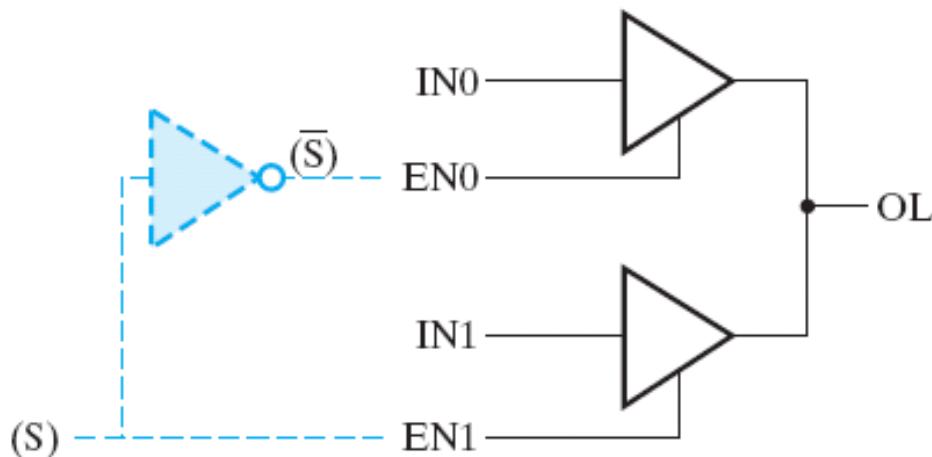

(a) Logic Diagram

EN1	EN0	IN1	IN0	OL
0	0	X	X	Hi-Z
(S) 0	$\overline{(S)}$ 1	X	0	0
0	1	X	1	1
1	0	0	X	0
1	0	1	X	1
1	1	0	0	0
1	1	1	1	1
1	1	0	1	0
1	1	1	0	0

(b) Truth table

Three-State Buffers - 3


- If conflicting output appears at the connecting line
 - then the current is often large enough to cause heating and may even destroy the circuit
 - designer must ensure that EN0 and EN1 never equal 1 at the same time
 - e.g. by using a decoder to generate the EN signals

Enabling - 1

- In general, enabling permits an input signal to pass through to (affect) an output
 - Enable (EN) input signal is required to determine whether the output is enabled
 - Enable the operation of the logic circuit
- In addition to replacing the input signal with the Hi-Z (high impedance) state
 - Disabling also can replace the input signal with a fixed output value of 0 or 1

Enabling - 2

 - Disabled value 0
 - If $EN = 1$
 - Input X reaches output
 - If $EN = 0$
 - Output always 0
- Disabled value 1
 - If $EN = 1$
 - Input X reaches output
 - If $EN = 0$
 - Output always 1



Summary

- Five steps in logic circuit design
- Three techniques for minimization (simplification) with K-map being simplest while Quine-McCluskey method being systematic
- Variations in implementation including AND-OR, NAND-NAND and NOR-NOR being most common
- XOR offers alternative to SOP and POS in simplifying functions with scattered ones
- Enable and Hi-Z facilitate circuit interconnections