

# Combinational Logic (CLN)

CO 2206 Computer Organization

# Topics

- Design process refined
- Design example
- Combinational Functional Blocks
  - Decoders / Encoders
  - Multiplexers / Demultiplexers
  - Arithmetic

# Design Procedure - 1

## 1. Specification

- Write a specification for the circuit
- Text or HDL description
  - Hardware Description Language (HDL) will be covered in future lectures

## 2. Formulation

- Derive truth table or Boolean expressions that defines the relations between inputs and outputs

## 3. Optimization

- Provide a netlist (connection information) for the resulting circuit

# Design Procedure - 2

- Simplification or optimization based on specific criteria
  - e.g. gate cost, gate delay, fan-out limits, etc

## 4. Technology mapping

- Transform the logic diagram or netlist to a new diagram or netlist that implementation technology supports
- Optimization and mapping may repeat multiple times to meet specification

## 5. Verification

- Verify the correctness of final design

# BCD-to-Excess-3 Code Converter

- Specification
  - Excess-3 code: binary combination corresponding to the decimal digit plus 3
  - E.g. excess-3 code for 5 is 1000 (i.e.  $5+3=8$ )
- Formulation
  - Can be obtained from BCD code word by adding 0011(3) to it
  - 1010 through 1111 are not listed since they have no meaning in BCD code





# BCD-to-Excess-3 Code Converter

Truth Table for Code Converter Example

Decimal Digit	Input BCD				Output Excess-3			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0


# BCD-to-Excess-3 Code Converter

- Optimization

    

# BCD-to-Excess-3 Code Converter


- Direct implementation

 



# BCD-to-Excess-3 Code Converter

- Technology mapping (NAND, NOR)

 

# Verification - 1

- Verification
  - Determination of whether or not a given circuit implements its specified function
    - if the circuit does not meet its spec, then it is incorrect
  - It is essential that the spec is unambiguous and correct
    - Spec such as truth table, Boolean equations and HDL code are most useful


# Verification - 2

- Manual logic analysis
  - Finding the equations and then using them to find the truth table, if necessary
  - If new truth table matches the original one, the circuit is correct
  - E.g. manual verification of BCD-to-Excess-3 code converter

# Verification - 3

Input BCD				Output Excess-3			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

(a)

 


(b)

Input BCD				Output Excess-3			
A	B	C	D	W	X	Y	Z
0	0	0	0				1
0	0	0	1				
0	0	1	0		1		1
0	0	1	1		1	1	
0	1	0	0				1
0	1	0	1	1			
0	1	1	0	1			1
0	1	1	1	1		1	
1	0	0	0	1			1
1	0	0	1	1			

W, Z correct (c)  
X, Y incorrect
 
# Verification - 4

- Using computer simulation
  - Useful for large number of variables
  - Greatly reduces the tedious analysis effort required




# Combinational Functional Blocks
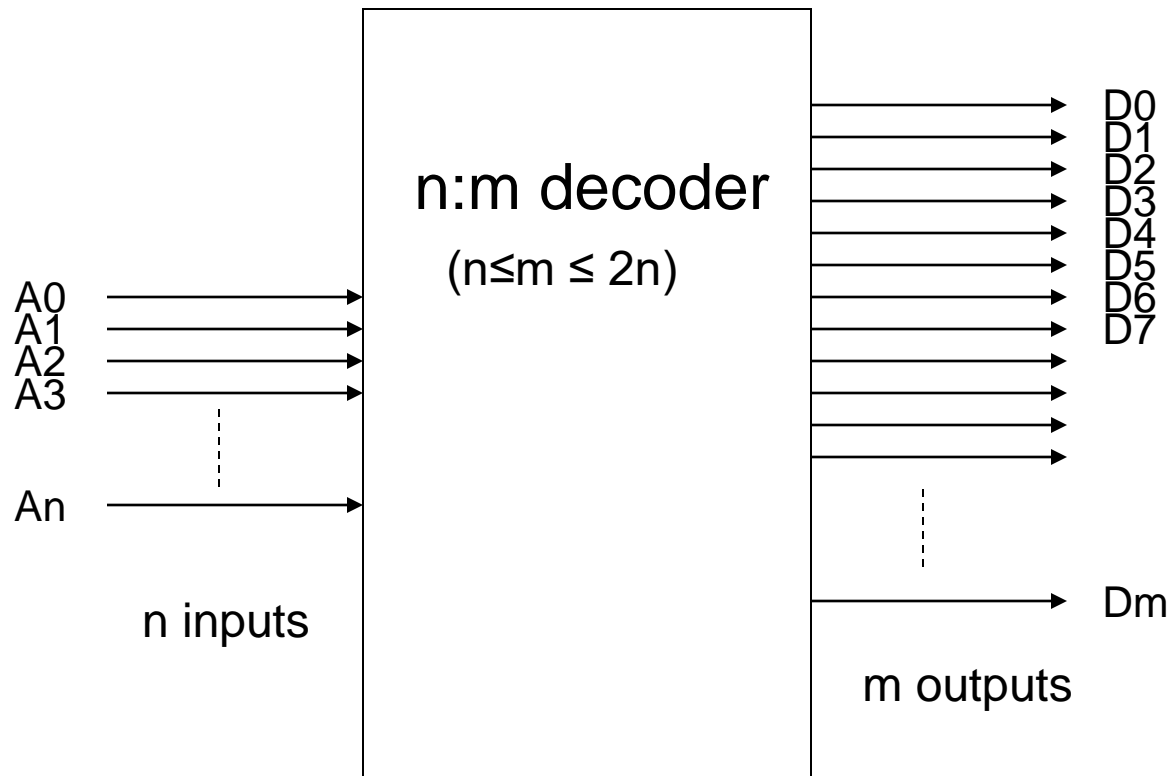
# n-to-m Decoder

$$(n \leq m \leq 2^n)$$



- A decoder converts binary information from  $n$  input lines to a maximum of  $2^n$  unique output
  - If there are unused or don't care input combinations, the decoder output will have fewer than  $2^n$  outputs
  - Each output represents one minterm
  - Only one output is active at any one time
  - Equivalent to binary-to-decimal
    - Decode: binary is the code, decimal is the meaning
  - Usages:
    - selecting boards or devices connecting to same bus
    - decode instructions to determine the operations to be performed in the processor



$D_0=1$  when  $A_n \dots A_3 A_2 A_1 A_0 = 0$        $D_6=1$  when  $A_n \dots A_3 A_2 A_1 A_0 = 6$




# 1-to-2 Decoder

  

<b>A0</b>	<b>D1</b>	<b>D0</b>
0	0	1
1	1	0


# 2-to-4 Decoder

 

- 2-to-4 line decoder
  - Only one output can be equal to 1 at any one time

$A_1$	$A_0$	$D_0$	$D_1$	$D_2$	$D_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

(a)

 


(b)

Each minterm is implemented by an AND
 
# Decoder: Minterm Implementation

- Large decoders can be constructed by
  - Implementing each minterm using a AND gate with more inputs
  - Unfortunately, this approach gives high gate-input costs
    - number of inputs




# Decoders: Hierarchy Implementation

- Large decoders can be constructed using smaller decoders
- General procedure
  - If  $n$  is even
    - Use  $2^n$  AND gates driven by
      - 2 decoders of output size  $2^{n/2}$
  - If  $n$  is odd
    - Use  $2^n$  AND gates driven by
      - 1 decoder of output size  $2^{(n+1)/2}$
      - 1 decoder of output size  $2^{(n-1)/2}$
  - Continue to divide  $n$  by 2 until  $n=1$ 
    - For  $n=1$ , use a 1-to-2 decoder

# 3-to-8 Decoder - 1


- 3-to-8-line decoders, i.e.  $n=3$ 
  - $k_1=n=3$ 
    - $2^{k_1}=8$  2-input AND gates
    - Driven by
      - 1 decoder of output size  $2^{k_1-1/2}=2$  (no further reduction)  
and
      - 1 decoder of output size  $2^{k_1+1/2}=4$  ( $k_2=k_1+1/2=2$ )
  - $k_2=2$ 
    - $2^{k_2}=4$  2-input AND gates
    - Driven by 2 decoders of output size  $2^{k_2/2}=2$

# 3-to-8 Decoder - 2

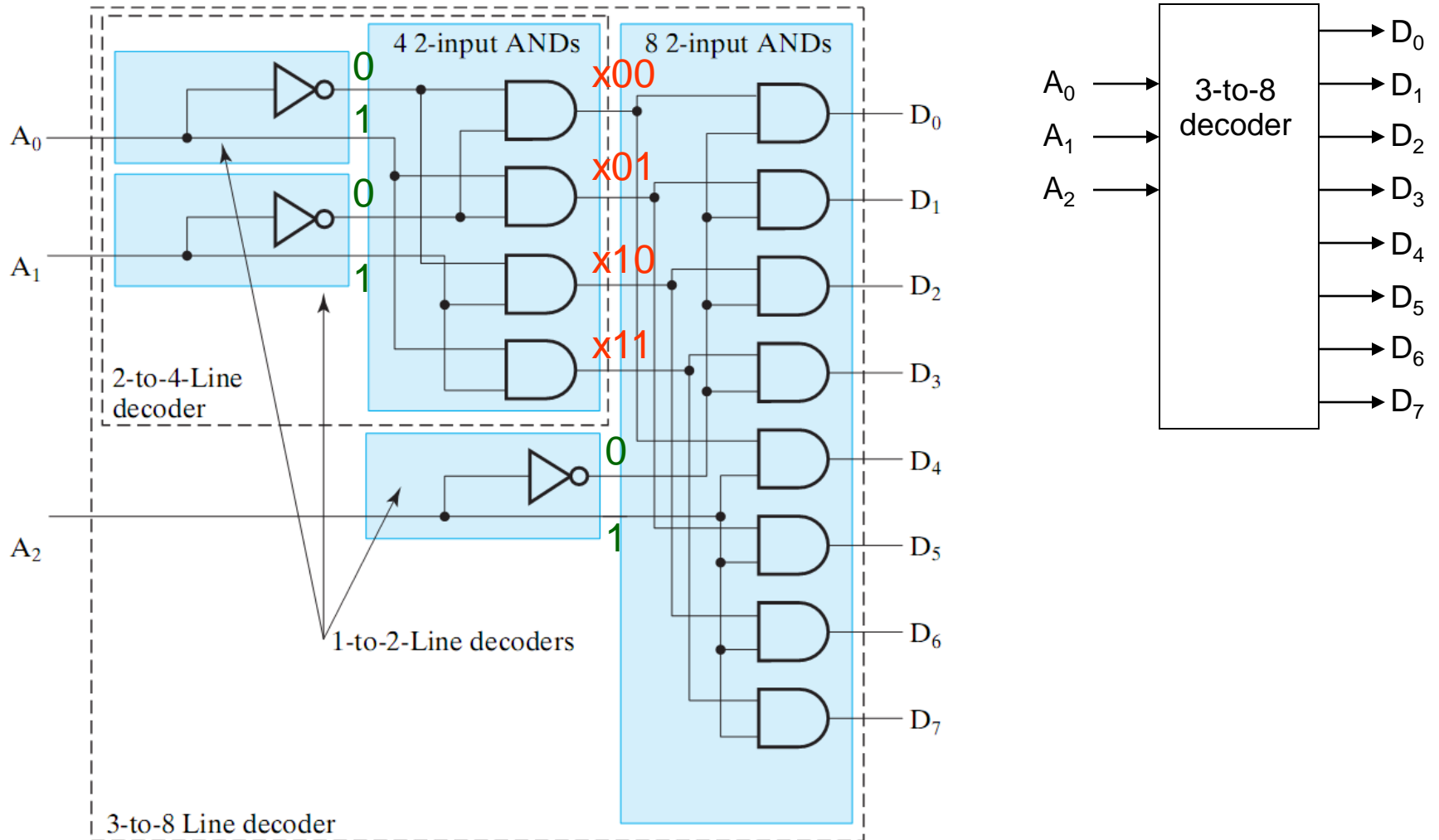

 
# 6-to-64 Decoder - 1

- 6-to-64-line decoders, i.e.  $n=6$ 
  - $k_1=n=6$ 
    - $2^{k_1}=64$  2-input AND gates
    - Driven by 2 decoders of output size  $2^{k_1/2}=8$  ( $k_2=k_1/2=3$ )
  - $k_2=3$ 
    - $2^{k_2}=8$  2-input AND gates
    - Driven by
      - 1 decoder of output size  $2^{k_2-1/2}=2$  (no further reduction) and
      - 1 decoder of output size  $2^{k_2+1/2}=4$  ( $k_3=k_2+1/2=2$ )
  - $k_3=2$ 
    - $2^{k_3}=4$  2-input AND gates
    - Driven by 2 decoders of output size 2





# 6-to-64 Decoder - 2

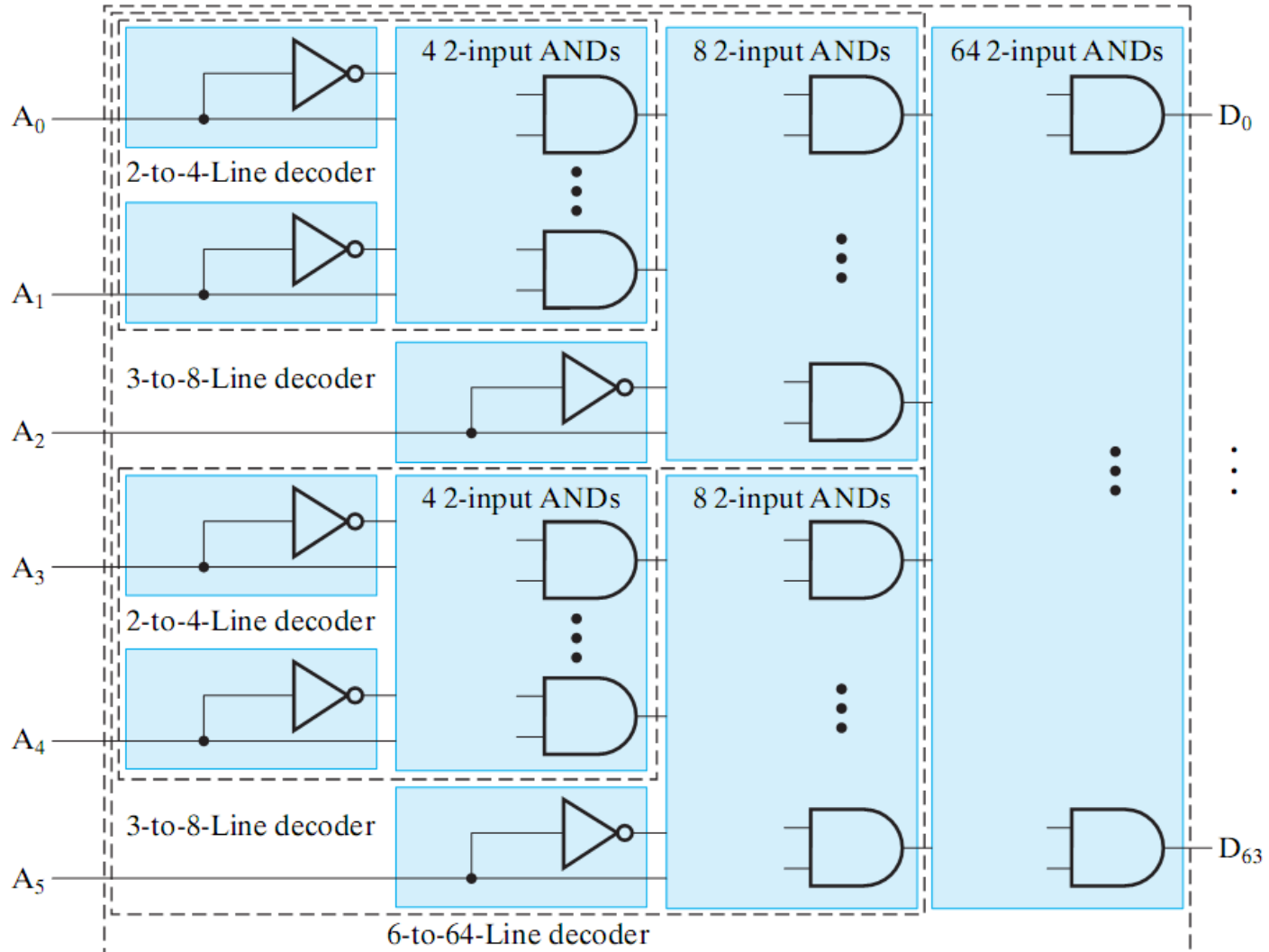


# Decoders – the Cost

- *Gate input costs* - the number of inputs to the gates in the implementation corresponding exactly to the given equation or equations
  - G - inverters not counted, GN - inverters counted
- For 6-to-64 decoder, if a single AND gate for each *minterm* were used
  - Gate-input cost
    - $GN = 3 + (6 \times 64) = 387$
- Smaller decoders used
  - Gate-input cost
    - $GN = 6 + 2(2 \times 4) + 2(2 \times 8) + 2 \times 64 = 185$

 
# Decoder with Enable

- Large decoders can be constructed using smaller (one level, i.e.  $m/2$ ) decoders with enabling
  - For example, 3x8 decoders with enable inputs connected to form a 4x16 decoder
    - When  $w=0$  (top decoder enabled)
      - Top outputs generate *minterms* 0000 to 0111
    - When  $w=1$  (bottom decoder enabled)
      - Bottom outputs generate *minterms* 1000 to 1111


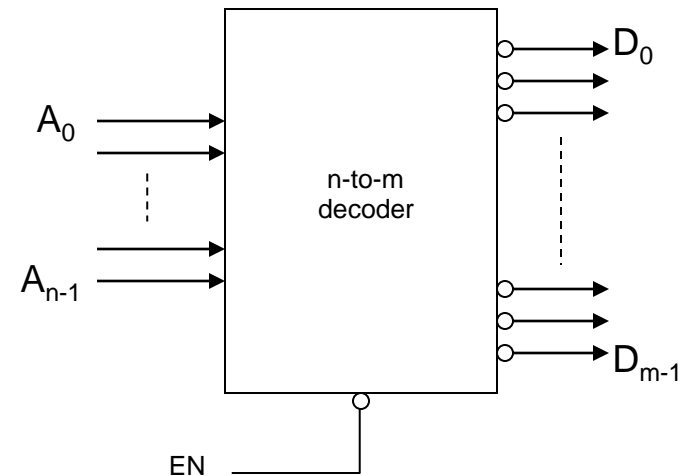
# Active-Hi vs Active-Lo

- To implement with NAND gates, it becomes more economical to generate the decoder minterms in their complemented form
- Small circles on the output lines indicate this
  - decoders designed to produce active-LOW outputs, where only the selected output is LOW while all others are HIGH
- Input can also be active-lo
  - $EN=1$ , decoder disabled (all output inactive)
  - $EN=0$ , decoder enabled




# Implement CLN using Decoders

- Any combinational circuit with  $n$  inputs and  $m$  outputs, expressed as sum of minterms can be implemented with
  - an  $n$ -to- $2^n$  decoder and
  - $m$  OR gates
- We can practically implement any *CLN* by expressing the output functions in sum of *minterms*
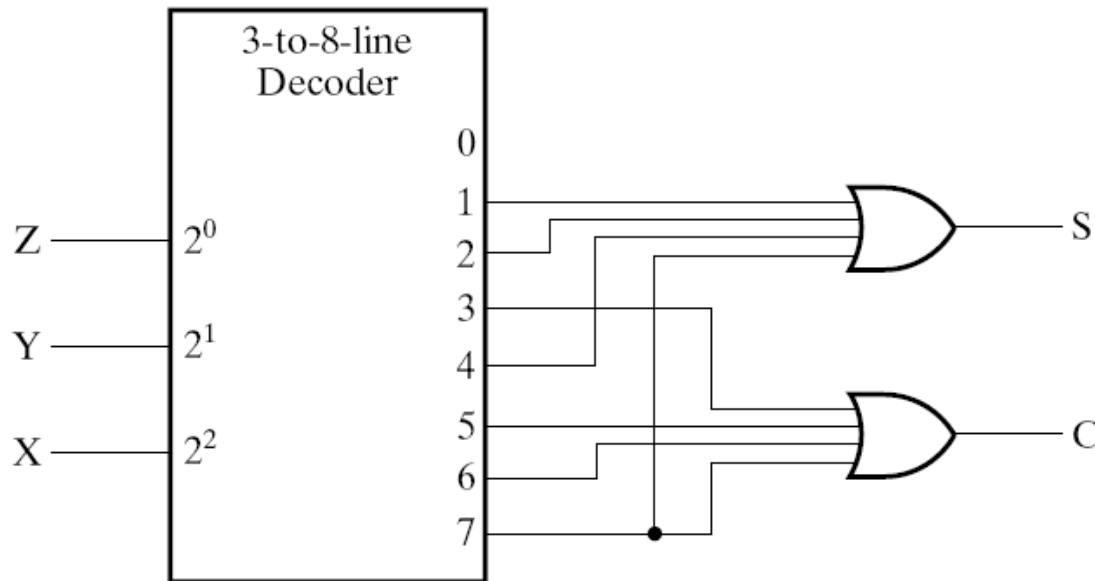
# Decoder Application Example


- Binary adder (one-bit with carry-in)
  - $S(X,Y,Z) = \Sigma m(1,2,4,7)$
  - $C(X,Y,Z) = \Sigma m(3,5,6,7)$



X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1
 
# Encoders

- Performs inverse operation of a decoder
- Has  $2^n$  (or fewer) input and  $n$  output lines
- Only one input has 1 at any time
  - simplify output expressions
- Usages:
  - converting “anything” to binary
  - encoding inputs, e.g. keyboards



When  $D_0=1$ ,  $A_n \dots A_2 A_1 A_0 = 0$

When  $D_3=1$ ,  $A_n \dots A_2 A_1 A_0 = 3$


# Encoder Example: Octal-to-binary

Inputs								Outputs		
D <sub>7</sub>	D <sub>6</sub>	D <sub>5</sub>	D <sub>4</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

- Octal-to-binary encoder
    - 8 inputs, one for each octal digit
    - 3 outputs that generate the corresponding binary number
    - Truth table has only 8 rows
      - For the remaining 56 rows, all outputs are don't cares
- $A_0 = D_1 + D_3 + D_5 + D_7$   
 $A_1 = D_2 + D_3 + D_6 + D_7$   
 $A_2 = D_4 + D_5 + D_6 + D_7$



# Draw the circuit: Octal to binary

 

# Priority encoder

- 2 inputs cannot be active simultaneously
  - If  $D_3$  and  $D_6$  are 1 simultaneously, encoder output is 111 (7), not 3 or 6
    - output is incorrect
    - to resolve, establish input priority
- Priority encoder ensures if 2 or more inputs are active simultaneously
  - Highest priority input will take precedence
- Another ambiguity
  - Output 000 generated when all inputs 0
    - but 000 output when  $D_0=1$
    - to resolve, assign another valid-output indicator to indicate at least one input is 1

# Priority Encoder Illustration - 1



- $D_3$  has the highest priority
  - When  $D_3 = 1$ 
    - Output for  $A_1A_0$  is 11
  - When  $D_2 = 1$ 
    - Output is 10, provided  $D_3 = 0$ 
      - Otherwise output is 11

Inputs				Outputs		
$D_3$	$D_2$	$D_1$	$D_0$	$A_1$	$A_0$	$V$
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1


# Priority Encoder Illustration - 2

- Output for  $D_1$  generated only if higher-priority inputs are 0
- Valid-output indicator  $V$  is set to 1
  - only when one or more inputs equal 1
  - if all inputs 0,  $V=0$ , and  $A_1A_0$  not used
- Boolean functions
  - $A_0 = D_3 + D_1D_2'$
  - $A_1 = D_2 + D_3$
  - $V = D_0 + D_1 + D_2 + D_3$

# Priority Encoder Illustration - 3

  

# Priority Encoder Illustration - 4

 


# Selecting

- Selection of info is a very important function
- Circuits that perform selection typically have
  - A set of inputs from which selection are made
  - A single output
  - A set of control lines for making the selection

# Multiplexers
 
## $2^n$ -to-1 MUX

- **Multiplexer** selects binary info from one of many input lines and directs it to a single output line
  - Normally, there are  $2^n$  input lines and  $n$  selection lines whose bit combinations determine which input is selected





# Example: 2-to-1 Multiplexer - 1


- **2-to-1** mux has
  - 2 inputs  $I_0$  and  $I_1$ , and
  - Selection line  $S$
  - When  $S = 0$ ,
    - Output  $Y = I_0$
  - When  $S = 1$ ,
    - Output  $Y = I_1$
  - Thus  $S$  selects which input to appear at  $Y$
  - $Y = S' I_0 + S I_1$

S	$I_0$	$I_1$	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


$S I_0 I_1$	00	01	11	10
0	0	0	1	1
1	0	1	1	0
 
# Example: 2-to-1 Multiplexer - 2


- *Multiplexer* can be constructed from:
  - an  $n$ -to- $2^n$  decoder
  - $n$  **AND** gates (enabling circuit); one at each decoder output
  - an **OR** gate at the output



(b) Block diagram

 


(a) Logic diagram

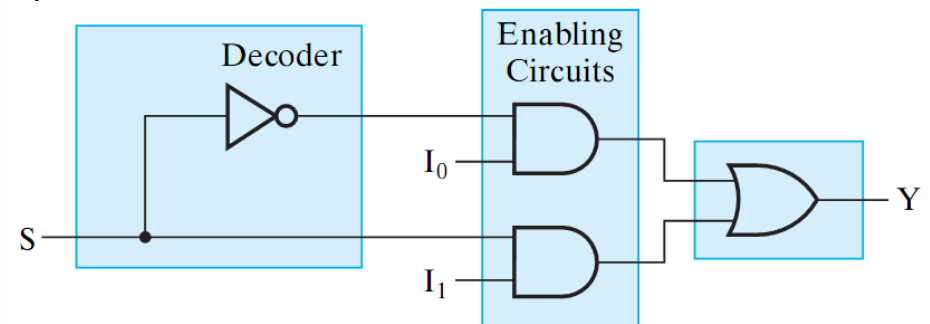

 
# Example: 4-to-1 Multiplexer - 1


- 4-to-1-line multiplexer
  - When  $s_1s_0=10$ 
    - AND gate associated with  $I_2$  has 2 inputs equal 1;
    - The other 3 AND gates have at least one input 0



$s_1$	$s_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

 

# Example: 4-to-1 Multiplexer - 2

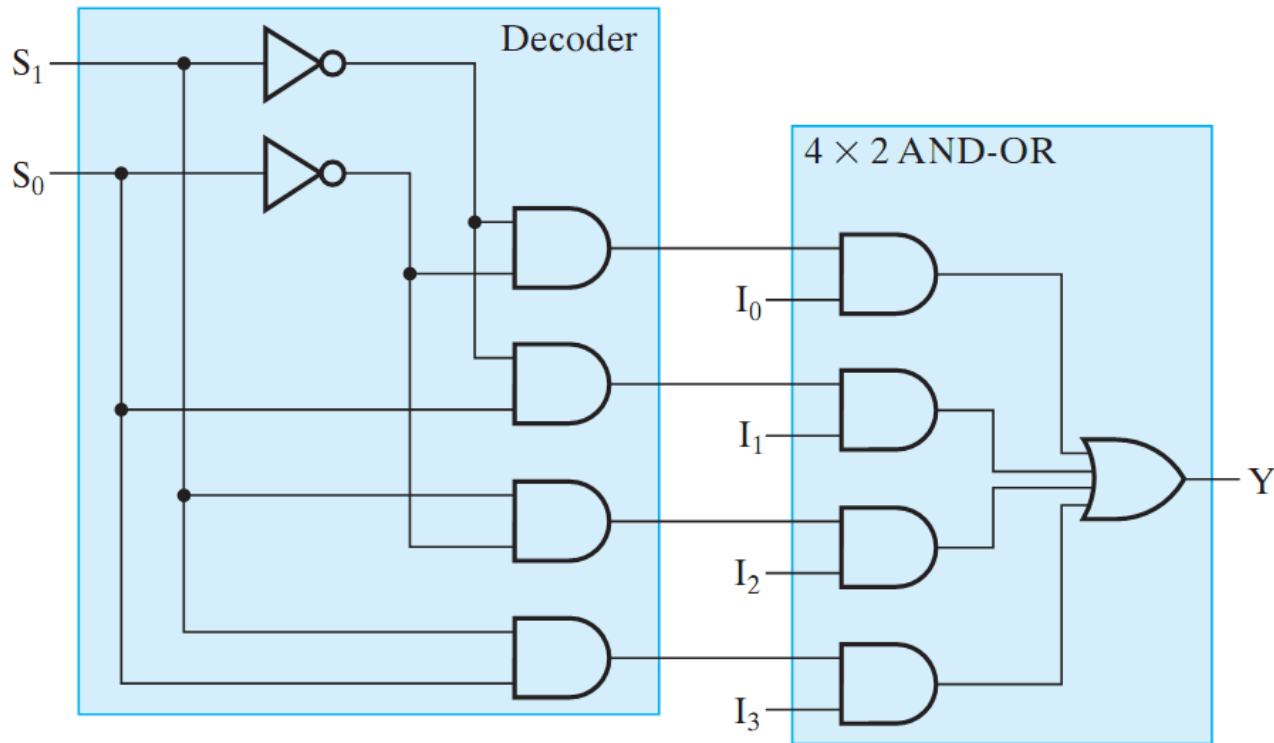

# Implement CLN using MUXs - 1


- **MUXs** consist of decoders and an **OR** gate, which makes it possible to implement **CLN** using **MUXs** without any other gate
- Procedure for implementing function of  $n$  variables with a  $2^{n-1}$ -to-1 multiplexer
  1. Express function in sum of minterms
  2. Assume ordered sequence of variables is ABCD... where A is the leftmost variable
  3. Choose one variable as input, usually the right most
  4. Connect remaining  $n-1$  variables to selection lines, with the rightmost variable connected to lowest-order selection line ( $S_0$ )

# Implement CLN using MUXs - 2

5. Construct truth table and divide into sections with identical values for the remaining  $n-1$  variables
6. Associate function output with the chosen input variable
  - This function will have value of either 0, 1 or the literal of the chosen input

$x$	$y$	$z$	$F$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


(a) Truth table

 

(b) Multiplexer implementation

# MUX Implementation Example

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>	
0	0	0	0	0	
0	0	0	1	1	$F = D$
0	0	1	0	0	
0	0	1	1	1	$F = D$
0	1	0	0	1	
0	1	0	1	0	$F = D'$
0	1	1	0	0	
0	1	1	1	0	$F = 0$
1	0	0	0	0	
1	0	0	1	0	$F = 0$
1	0	1	0	0	
1	0	1	1	1	$F = D$
1	1	0	0	1	
1	1	0	1	1	$F = 1$
1	1	1	0	1	
1	1	1	1	1	$F = 1$

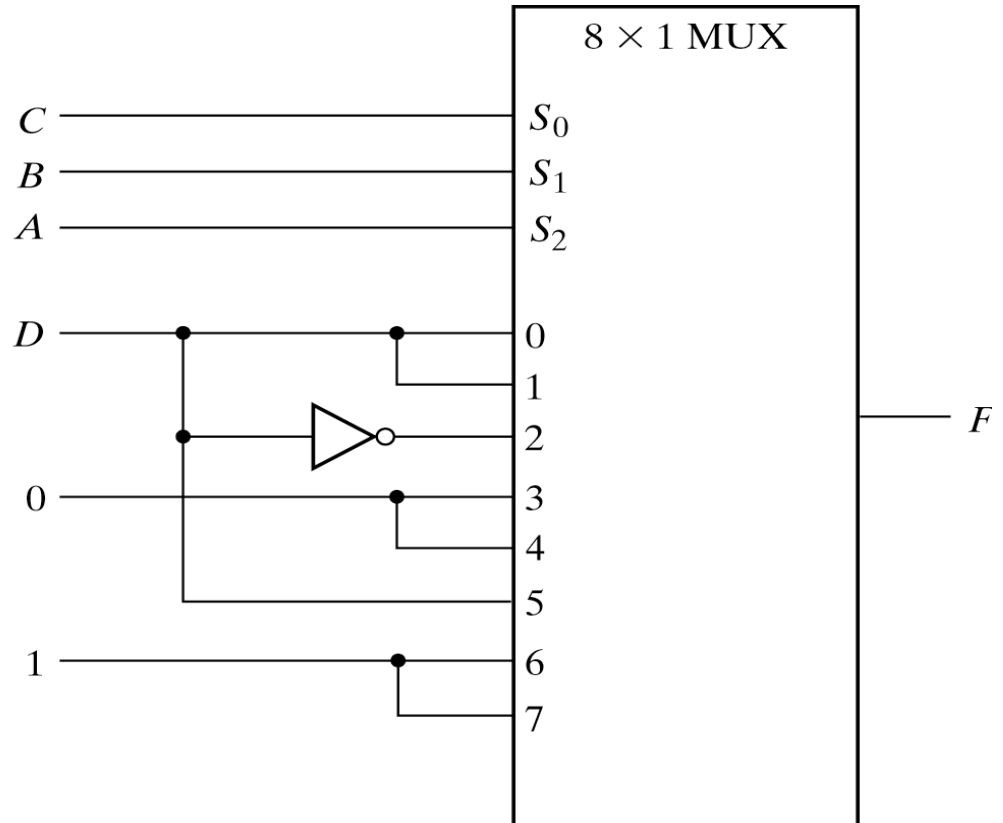


# Demultiplexers


- A decoder with an enable input can function as a *demultiplexer*
  - the *Enable* ( $EN$ ) line is taken as data input line while the *Binary* ( $A_1A_0$ ) inputs as selection lines
- A *demultiplexer* receives info on a single line and transmits this info to one of  $2^n$  possible output
  - $EN$  has a path to all 4 outputs



# Demultiplexers

 

 if  $A_{0-n} = Y$ ,  $D_Y = \text{Input}$ , else  $D_Y = 0$



1:4 Demux using 2-4 Decoder

# Arithmetic Circuits

# Adders

- Digital computers perform a variety of information-processing tasks
  - The most basic arithmetic operation is the addition of two binary digits
- Addition consists of 4 possible elementary operations:
  - $0 + 0 = 0$
  - $0 + 1 = 1$
  - $1 + 0 = 1$
  - $1 + 1 = 10$
- When augend and addend bits are 1, the binary sum consists of 2 digits, *carry* and *sum*
  - carry is the higher significant bit

# Adders

- *Half adder*
  - addition of 2 bits (two 1-bit numbers)
- *Full adder*
  - addition of 3 bits
  - i.e. two 1-bit numbers and 1 carry
- 2 half adders can be employed to implement a full-adder

# Half Adder: 1-bit

- Half-adder adds 2 bits (1 bit to 1 bit) and produces a sum and carry output


- $S = x'y + xy'$

$$= x \oplus y$$

- $C = xy$

$$\begin{array}{r} \phantom{+} \phantom{X} \\ + \phantom{X} \phantom{Y} \\ \hline \phantom{+} C \phantom{S} \\ \hline \end{array}$$


*X and Y are 1-bit*

 

Inputs		Outputs	
X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 
# More than 1-bit

- Each half adder add each bit (position)



	1	1	
	1	0	1
+	0	1	1
	1	0	0
	e.g. $X=101$ and $Y=11$		

 *Will the circuit below give correct sum?*




# Full Adder


- Problem with half adder is that we cannot use it to build adders that can add more than two 1-bit no.
- A full adder takes 3 inputs and generates 2 outputs
- z represents the carry from the previous lower significant position

Inputs			Outputs	
X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# Full Adder: K-Map

 
 
$$\begin{aligned}
 S &= \overline{X}\overline{Y}Z + \overline{X}Y\overline{Z} + X\overline{Y}\overline{Z} + XYZ \\
 &= X \oplus Y \oplus Z
 \end{aligned}$$




$$\begin{aligned}
 C &= XY + XZ + YZ \\
 &= XY + Z(XY + \overline{X}Y) \\
 &= XY + Z(X \oplus Y)
 \end{aligned}$$


 
# Full Adder: Circuit

- Using 2 half adders and an OR gate
  - $S = z \oplus (x \oplus y)$
  - $C = z(x \oplus y) + xy$



# Binary Adder - 1


- Adding 2 binary numbers of  $n$  bits each
- Bits added with full adders, starting from least significant position (i.e. subscript 0)
- The input carry  $C$  ( $Z$  is the input carry) in the least significant position (i.e.  $C_0$ ) must be 0
- The value of input carry  $C_{i+1}$  is the output carry  $C_i$  of the full-adder to the right

# Binary Adder - 2

- Sum bits generated as soon as the previous carry bit is generated
- Sum can be generated in serial or parallel fashion
  - Serial method uses only one full adder and a storage device to hold the generated carry
  - Parallel method uses  $n$  full adder, and all bits of augend and addend are applied simultaneously
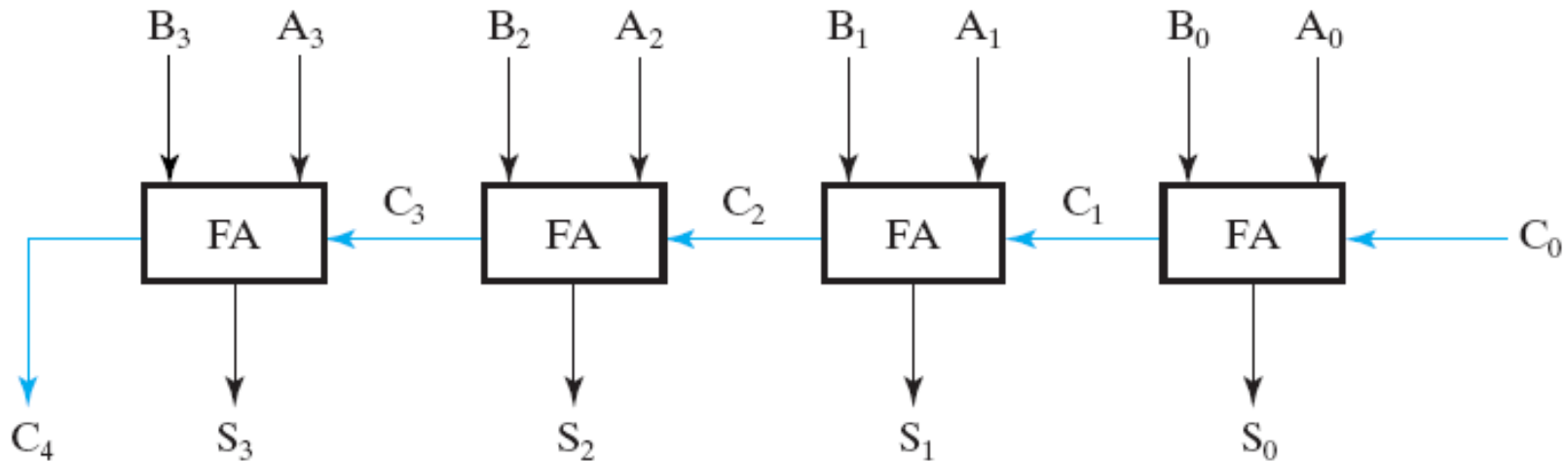
# Binary Parallel Adder

- Consists of full adders connected in chain, with the output carry from each full-adder connected to the input carry of the next full-adder
- $n$ -bit parallel adder requires  $n$  FA



# Binary Parallel Adder: Cons - 1

- Parallel adder has a long delay due to many gates in the carry path from the least significant bit to the most significant bit
  - Each bit of output sum depends on input carry
- Outputs not correct unless signals given enough time to propagate
- *Total propagation time = typical gate delay x number of gate levels*


# Binary Parallel Adder: Cons - 2

- Signal from input carry  $C_i$  to output carry  $C_{i+1}$  propagates through an **AND** and **OR** gate (i.e. 2 gate-levels)
- $n$ -bit parallel adder  $\approx 2n$  gate level carry propagation

# Carry Look-ahead Adder - 1

- To reduce carry propagation delay in parallel adder
  - Employ faster gates
  - Several reduction techniques, but carry look-ahead most widely used
- Two conditions for a carry:
  - $G_i$  carry generate
    - produces an output carry when  $A_i$  and  $B_i$  are available, regardless of input carry
  - $P_i$  carry propagate
    - associated with propagation of carry from  $C_i$  to  $C_{i+1}$

# Carry Look-ahead Adder - 2

 

- Define  $P_i = A_i \oplus B_i$  (equally valid using  $P_i = A_i + B_i$  for carry look-ahead)

$$G_i = A_i B_i$$

- Hence  $S_i = P_i \oplus C_i$

$$C_{i+1} = G_i + P_i C_i$$



# Carry Look-ahead Generator


For 2-bit adder,

$$C_1 = G_0 + P_0C_0$$

$$\begin{aligned} C_2 &= G_1 + P_1C_1 \\ &= G_1 + P_1G_0 + P_1P_0C_0 \end{aligned}$$


$$\begin{aligned} C_3 &= G_2 + P_2C_2 \\ &= G_2 + P_2G_1 + P_2P_1G_0 + \\ &\quad P_2P_1P_0C_0 \end{aligned}$$

 Note that all Carries are generated directly from  $C_0$  and the augend and addend bits, i.e. no carry propagation


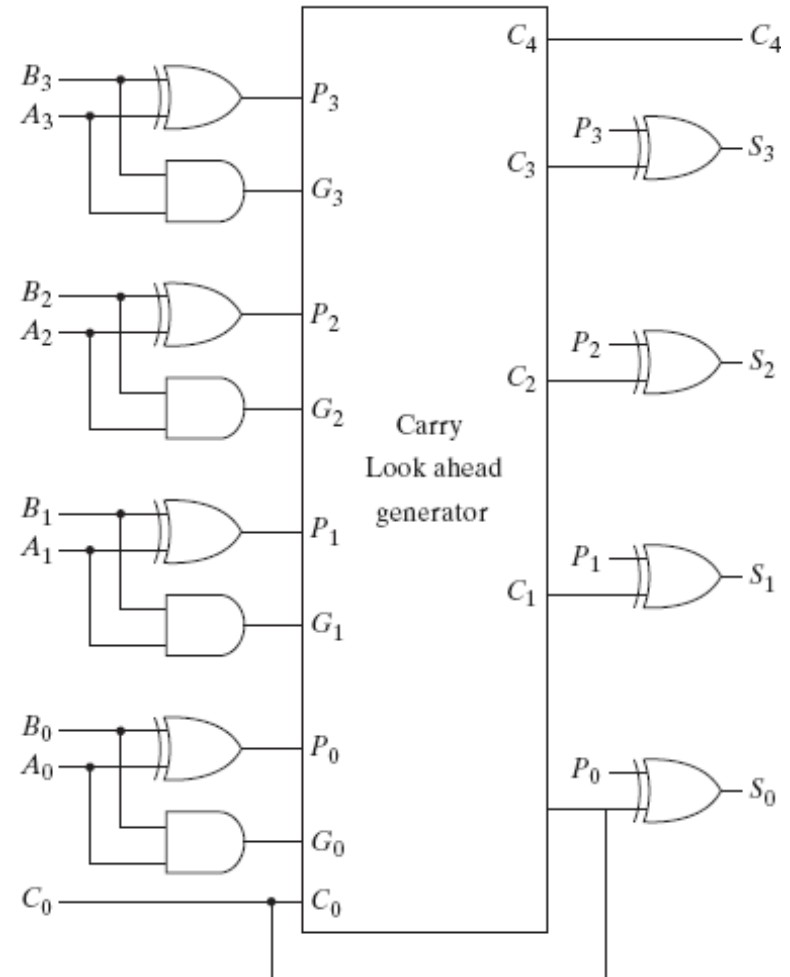
# Carry Look-ahead Adder - 3

- After P and G signals settle into their steady-state values, all outputs generated after a delay of 2 levels of gates.
- $S_1$ ,  $S_2$ , and  $S_3$  have equal propagation delay



# Signed Binary - 1

- If the binary number is signed, then the leftmost bit represents the sign and the rest represent the number
  - In convention, sign bit 0 for +ve and 1 for -ve
  - E.g. 11001 can be considered as
    - 25 (unsigned)
    - -9 (signed)

# Signed Binary - 2

- In a *signed-complement* system, a –ve number is represent by its complement

Decimal	Signed 2's Complement	Signed 1's Complement	Signed Magnitude
+ 7	0111	0111	0111
+ 6	0110	0110	0110
+ 5	0101	0101	0101
+ 4	0100	0100	0100
+ 3	0011	0011	0011
+ 2	0010	0010	0010
+ 1	0001	0001	0001
+ 0	0000	0000	0000
– 0	—	1111	1000
– 1	1111	1110	1001
– 2	1110	1101	1010
– 3	1101	1100	1011
– 4	1100	1011	1100
– 5	1011	1010	1101
– 6	1010	1001	1110
– 7	1001	1000	1111
– 8	1000	—	—

# Signed Binary - 3

- Signed-magnitude system is awkward when employed in computer arithmetic
  - Separate handling of the sign
  - Correction step required for subtraction
- 1's complement imposes difficulty
  - +0 and -0 seldom used for arithmetic operations
- Signed-2's complement most prevalent in modern system

# Signed Binary - 4

- **1's** complement of a binary number is formed by complementing each of the bits
  - E.g. 1's complement of 0001111 is 1110000
- **2's** complement can be formed by
  - Adding 1 to the 1's complement value, or
  - Leaving all least significant 0's and the first 1 unchanged and then complementing all higher significant bits
  - E.g. 2's complement of 1101100 is 0010100
- Note that the complement of the complement restores the number to its original value

# Binary Subtraction - 1

- **Subtraction** can be done by negate then add:
  - $A - B$  can be done by finding the negative of B and then add to A
  - $A - B = A + (-B)$
- Using either **1's** or **2's** complement, subtraction can be performed using
  - **Complementer** and
  - **Adder**

*(complement then add)*

# Binary Subtraction - 2

- Signed addition using 2's complement
  - Any carry out of the sign bit position is discarded, and negative results are automatically in 2's complement form
- Signed subtraction using 2's complement
  - 2's complement the subtrahend and add
- One common hardware can be used to handle both signed and unsigned binary addition and subtraction
  - But the results must be interpreted differently depending on whether the numbers are signed or unsigned
  - The same circuit in next slide can be used with no correction step required for signed-2's complement



# Signed Binary Subtraction

- 2's complement

$$x = 0101100 \text{ (44)}, y = 0111101 \text{ (61)}$$

$$x - y = x + (-y)$$


$$x = 0101100$$

$$-y = 1000011 \text{ (2's complement of } y)$$

$$\text{sum} = 1101111 \text{ (-17)}$$

$$x - y = 0010001 \text{ (-2's complement of sum)}$$

# Adder-subtractor - 1

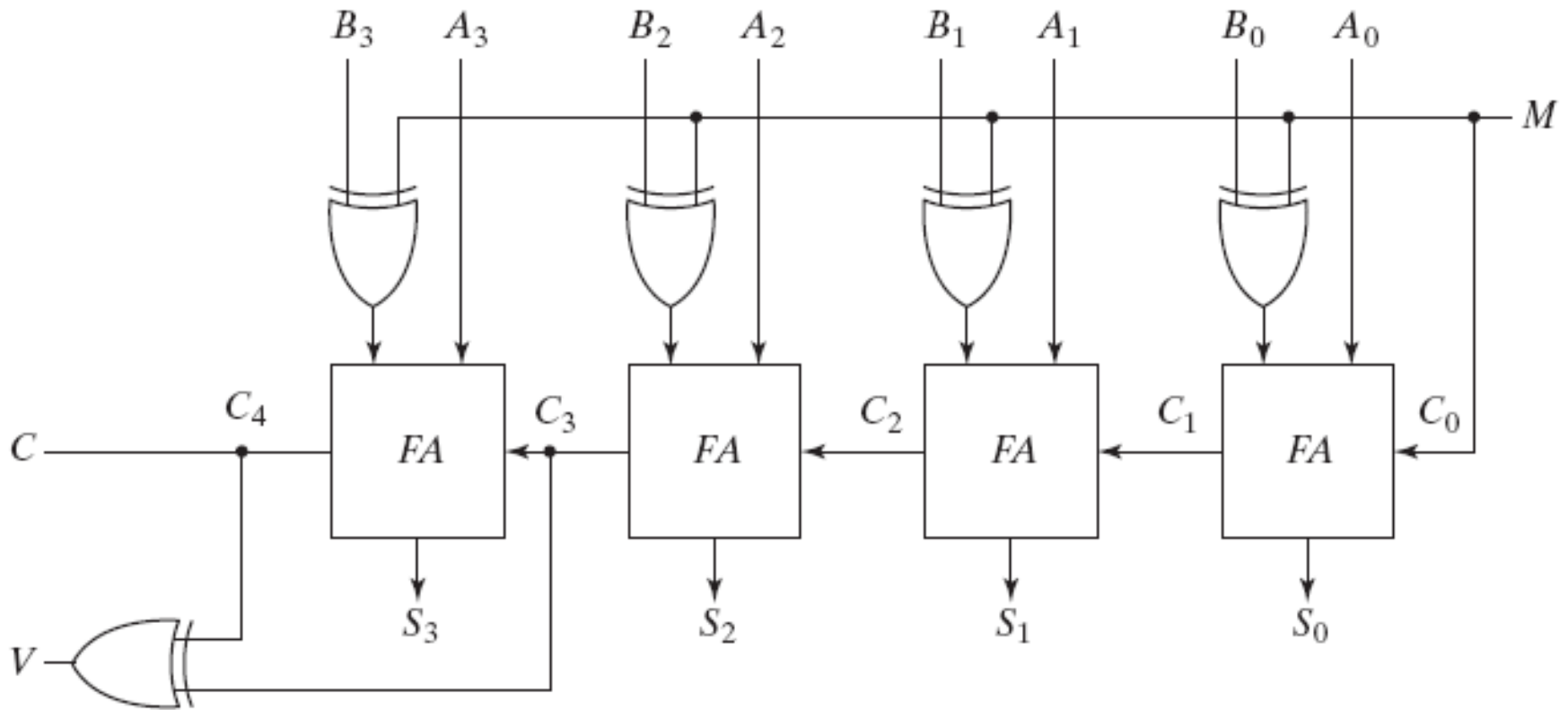

# Adder-subtractor - 2

- $A - B = A + 2$ 's complement of  $B$   
=  $A + 1$ 's complement of  $B + 1$
- 1 can be added to sum through input carry
  - therefore  $C_0$  must be equal to 1 when subtract
- When  $M = 0$ , adder
  - $B \oplus 0 = B$ , and  $C_0 = 0$
- When  $M = 1$ , subtractor
  - $B \oplus 1 = B'$ , and  $C_0 = 1$

# Overflow

- If we start with two  $n$ -bit numbers, but the result occupies  $n+1$  bits, an *overflow* occurs
  - For unsigned numbers, an overflow is detected from the end carry out of the most significant position
  - For signed numbers, if the carry into and carry out of the sign bit position are not equal, an overflow has occurred
    - If  $V = 0$ , no overflow
    - If  $V = 1$ , overflow

# Overflow

Carries:	0 1		1 0
+ 70	01000110	- 70	10111010
+ 80	01010000	- 80	10110000
<hr/>		<hr/>	
+ 150	10010110	- 150	01101010

range of 8-bit signed: -128 to +127

# BCD Adder - 1

- A decimal adder (4-bit) requires a minimum of 9 inputs and 5 outputs
- Adder produce sum in binary and range from 0 to 19
- Find rule to convert invalid binary sum to correct BCD representation
  - Binary sum  $\leq 1001$  (9), no conversion needed
  - Binary sum  $> 1001$ , invalid BCD  $\therefore$  add 0110 (6)

# Binary vs BCD

Binary Sum					BCD Sum					Decimal
K	Z <sub>8</sub>	Z <sub>4</sub>	Z <sub>2</sub>	Z <sub>1</sub>	C	S <sub>8</sub>	S <sub>4</sub>	S <sub>2</sub>	S <sub>1</sub>	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

→  
+6


# BCD Adder - 2

- Correction needed when:
  - Carry  $K = 1$
  - Combinations that have 1 in position  $Z_8$  and 1 either in  $Z_4$  or  $Z_2$  (to distinguish valid  $1000$  and  $1001$ )
- BCD addition

0110 (6)	0100	0111 (47)	0101	1001 (59)
<u>+ 0111 (7)</u>	<u>+ 0011</u>	<u>0101 (35)</u>	<u>+ 0011</u>	<u>1000 (38)</u>
1101 invalid	0111	1100 invalid	1000	0001 invalid
<u>+ 0110 (+6)</u>	<u>+ 1</u>	<u>0110 (+6)</u>	<u>+ 1</u>	<u>0110 (+6)</u>
0001 0011 (13)	1000	0010 (82)	1001	0111 (97)



# BCD Adder - 3


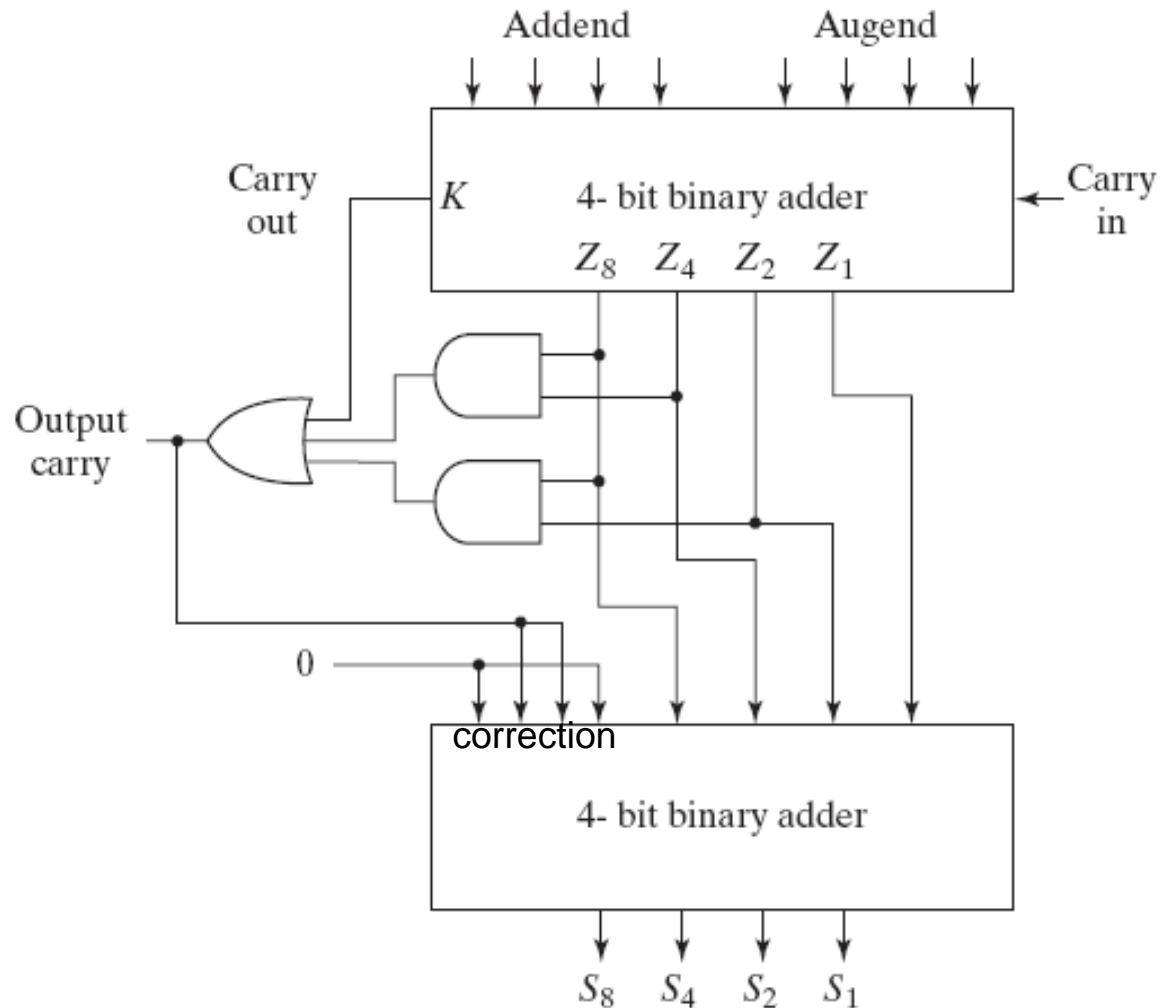


# BCD Adder - 3

- Condition for correction and an output carry
$$C = K + Z_8Z_4 + Z_8Z_2$$
- When  $C = 1$ , add **0110** through bottom 4-bit binary adder
- When  $C = 0$ , add **0000**
- Output carry generated from bottom adder ignored


# Binary Multiplier - 1

- 2-bit by 2-bit binary multiplier

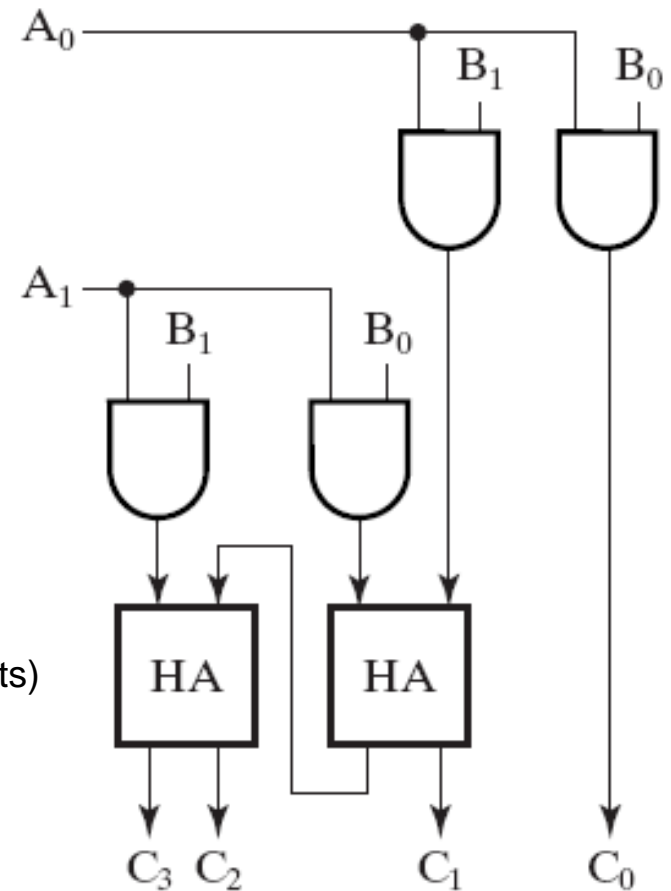 

# Binary Multiplier - 2

- 4-bit by 3-bit binary multiplier

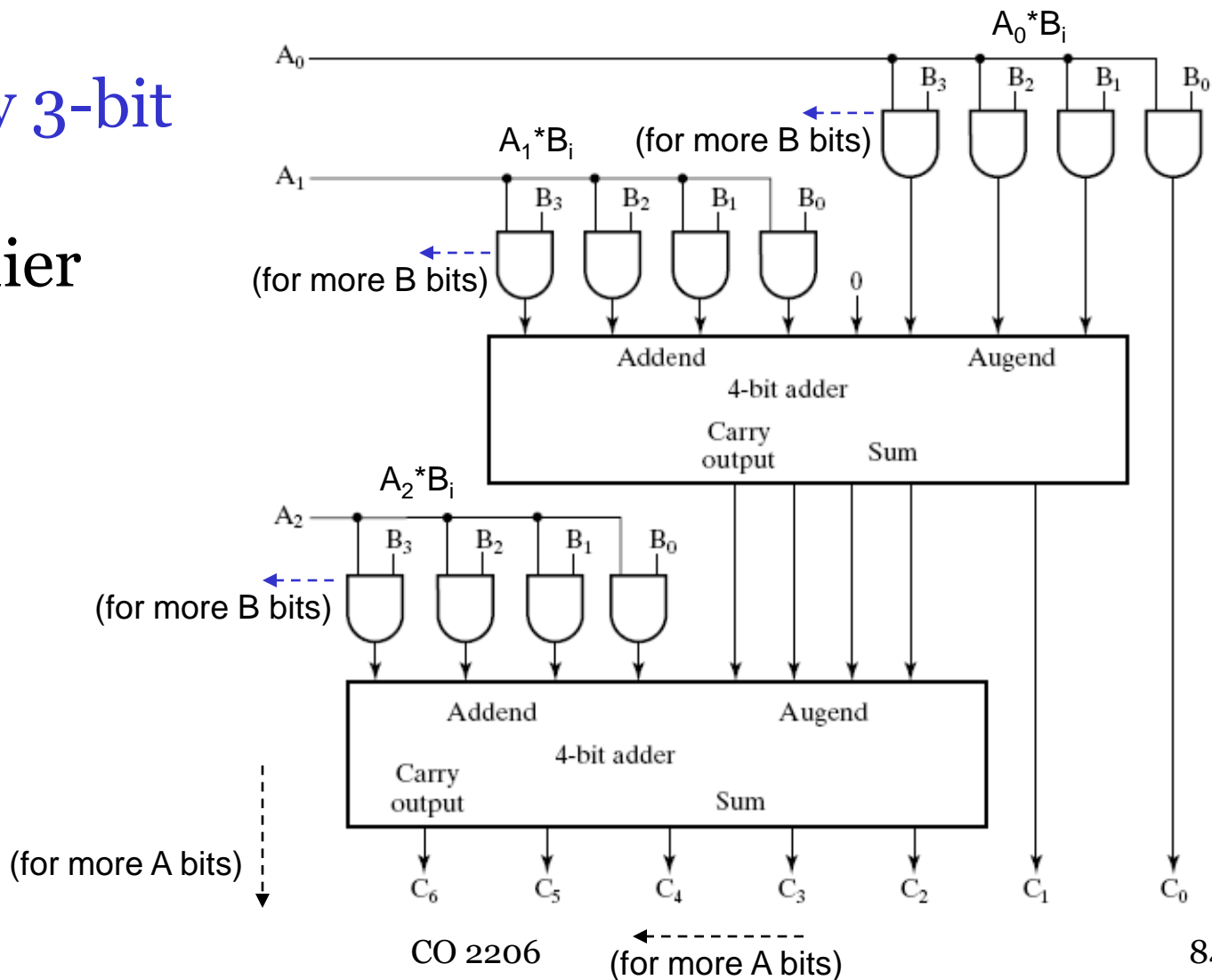


# Magnitude Comparator - 1

- A circuit that compares two numbers and determine their relative magnitudes
- Consider A, B with 4 digits each
  - $A = A_3A_2A_1A_0$        $B = B_3B_2B_1B_0$
- Equality relation of each pair of bits can be expressed as  $x_i = A_iB_i + A_i'B_i'$ 
  - $x_i = 1$  only if the pair of bits in position i are equal
  - $(A=B) = x_3x_2x_1x_0$

# Magnitude Comparator - 2

- $(A > B) = A_3 B_3' + x_3 A_2 B_2' + x_3 x_2 A_1 B_1' + x_3 x_2 x_1 A_0 B_0'$ 
  - if  $A_3 > B_3$  or  $A_3 = B_3$  but  $A_2 > B_2$  or  $A_3 = B_3, A_2 = B_2$  but  $A_1 > B_1$  or  $A_3 = B_3, A_2 = B_2, A_1 = B_1$  but  $A_0 > B_0$
- $(A < B) = A_3' B_3 + x_3 A_2' B_2 + x_3 x_2 A_1' B_1 + x_3 x_2 x_1 A_0' B_0$
- Comparison starts from MSB until a pair of unequal bits is reached
  - if  $A_i$  is 1 and  $B_i$  is 0,  $A_i > B_i$
  - If  $A_i$  is 0 and  $B_i$  is 1,  $A_i < B_i$

# Magnitude Comparator

 

# Summary

- Important combinational functional blocks were introduced
- Functional blocks are build from logic gates or smaller functional blocks
- Design of functional blocks based on truth-table, i.e. knowing its function
- Some designs simplified based on confined definition of the function, i.e. not all input combinations need to be considered
- These functional blocks will be used to build up larger system, eventually the computer