

VHSIC Hardware Description Language




CO 2206 Computer Organization

Topics

- Hardware Description Language
- VHDL History
- VHDL Characteristics
- Abstract Levels in IC Design
- Abstract Levels and VHDL
- VHDL – file structure, syntax
- VHDL Models: Structural, Behavioral
- Test Bench

Hardware Description Language - 1

   - **HDL** resembles programming language, but are specifically oriented to **describing hardware structures and behavior**
 - HDL represent extensive **parallel operation**
 - whereas most programming languages represent serial operation
- Usages (for digital networks) - to describe and simulate complex digital systems:
 - **Modelling**
 - **Simulation**
 - **Synthesis**



Hardware Description Language - 2

- HDL models are reusable
 - re-used in several designs/projects
 - frequently needed function blocks are collected in model libraries
- Reasons for HDL
 - Logic simulation and synthesis are the main reason for the growth in the use of HDL
 - HDLs are portable across CAD tools, whereas schematic capture tools are typically unique to particular vendor
- Few HDL languages
 - VHDL (VHSIC HDL) – we will only learn VHDL
 - Verilog
 - ABEL (Advanced Boolean Equation Language)

VHDL History

VHDL = VHSIC HDL = Very High Speed Integrated Circuit HDL


- **Early '70s:** Initial discussions
- **1981:** First introduced for the US Department of Defense (DoD) under the VHSIC program with the goal to develop very high-speed integrated circuit; IEEE sponsored
- **1983:** IBM, Texas Instruments and Intermetrics started to develop this language
- **1985:** VHDL 7.2 version was released
- **1987:** IEEE standardized the language as IEEE 1076
- **1993:** New standard IEEE 1076-1993

VHDL Characteristics

- **Execution** of assignments:
 - **Sequential** statements are executed one after another. The order of the assignment must be considered when sequential statements are used.
 - **Concurrent** statements are active continuously. So the order of the statements is not relevant. Concurrent statements are especially suited to model the parallelism of hardware.
- **Methodologies**:
 - **Abstraction** allows for the description of different parts of a system with different amount of detail.
 - **Modularity** enables the designer(s) to split big functional blocks and to write a model for each part.
 - **Hierarchy** lets the designer build a design out of submodules which may consist of several submodules, themselves.

Abstraction Levels in IC Design - 1

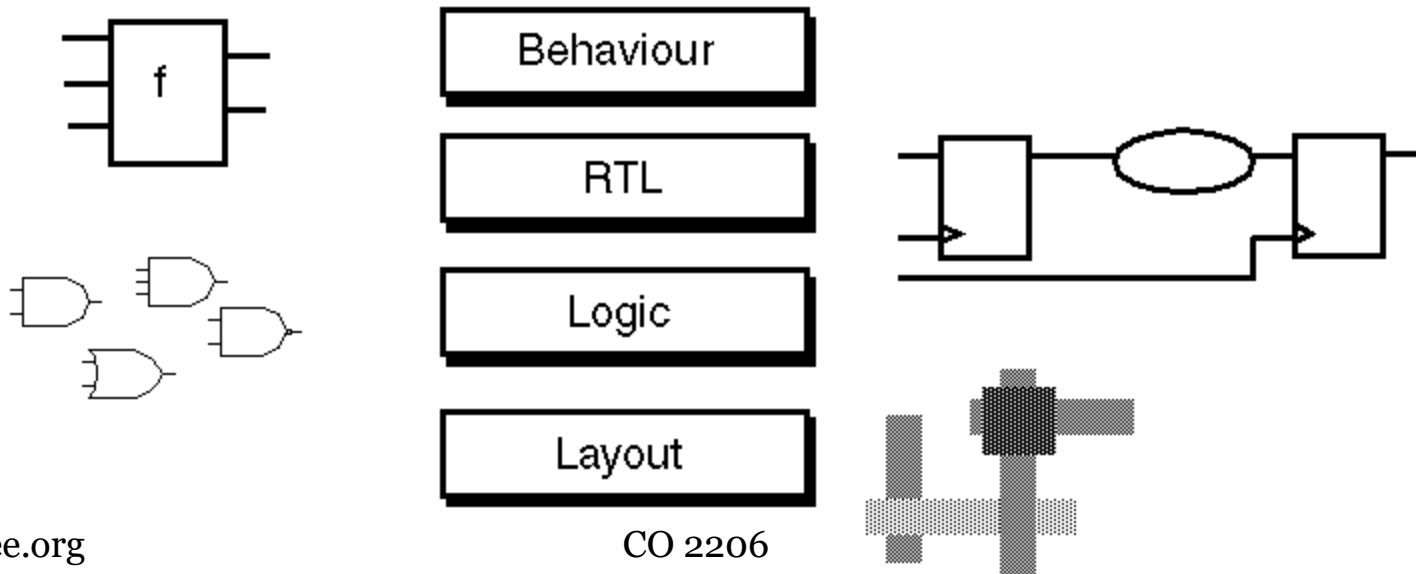- **Abstraction** is hiding of details:
 - Differentiation between essential and nonessential information
- Creation of abstraction **levels**:
 - On every abstraction level only the essential information is considered, nonessential information is left out
- Equability of the abstraction:
 - All information of a model on one abstraction level contains the same degree of abstraction




Abstraction Levels in IC Design - 2

- **Behavioral** - the function
 - no system clock and signal transitions are asynchronous with respect to the switching time
 - usually simulatable but not synthesizable.
- **Register Transfer Level (RTL)** - the design is divided into combinational logic and storage elements
 - controlled by a system clock
 - called synthesizable description
- **Logic level** - netlist (interconnections) with logic gates (AND, OR, NOT, ...) and storage elements
- **Layout** - at the bottom of the hierarchy
 - different cells of the target technology are placed on the chip and the connections are routed


Abstraction levels and VHDL

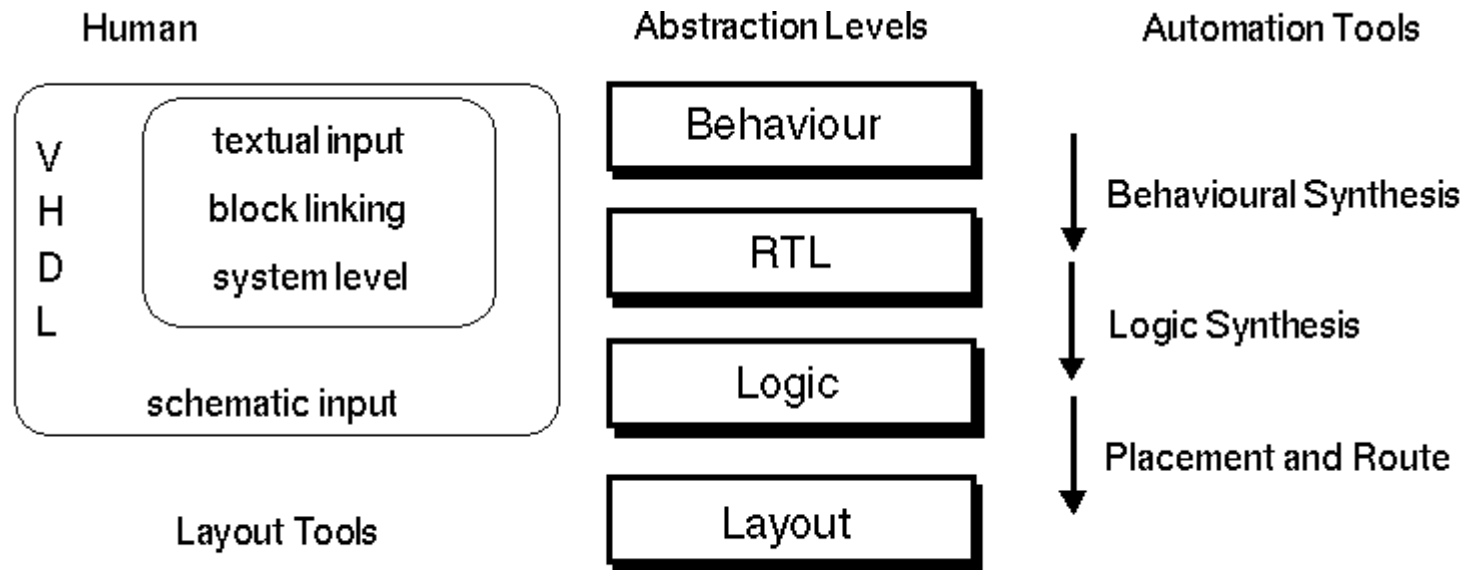- **VHDL** is applicable to the upper three abstraction levels
 - not suitable to describe a layout



ASIC Development Process

An Example VHDL Application

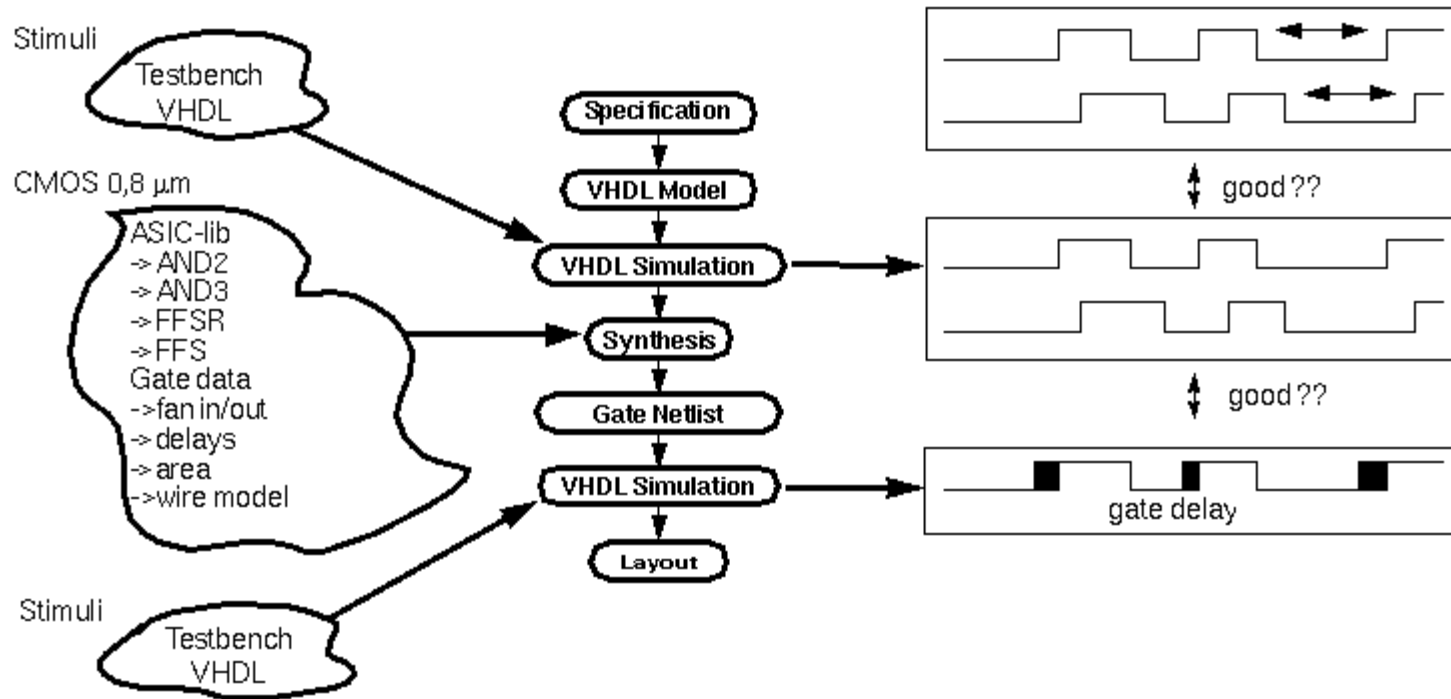


VHDL File Structure

- Two major parts:
 - **Entity** describes the interface
 - **Architecture** contains the description of the function

```
-- comment
library ieee;
use ieee.std_logic_1164.all;

-- declaration of the entity
entity entity_name is
    -- declarations
end entity_name;

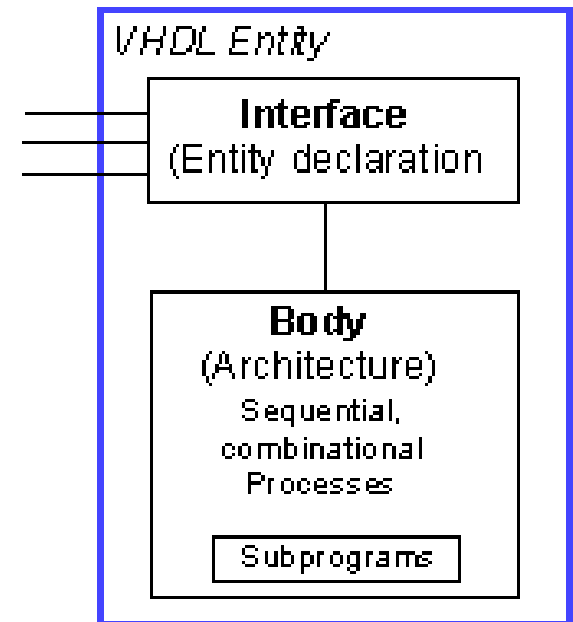-- body (architecture)
architecture arch_name of entity_name is
    -- declarative
begin
    -- definitions
end arch_name;
```



VHDL Syntax Rules


- Case insensitive
- Comments: '--' until end of line
- Statements are terminated by ';' – (may span multiple lines)
- List delimiter: ','
- Signal assignment: '<='
- User defined names:
 - letters, numbers, underscores
 - start with a letter

Entity Declaration

```
entity NAME_OF_ENTITY is [generic generic_declarations];  
    port (signal_names: mode type;  
          signal_names: mode type;  
          :  
          signal_names: mode type;  
end [NAME_OF_ENTITY];
```


- Interface description
- No behavioral definition
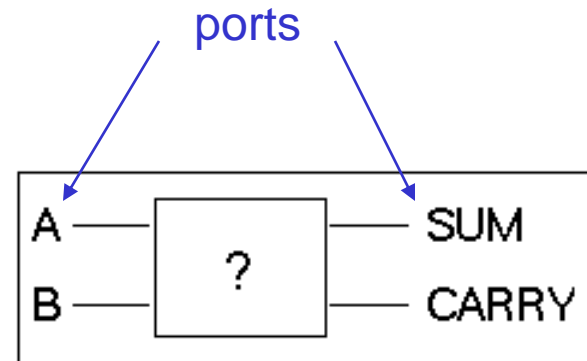
```
entity HALFADDER is  
    port (  
        A,B: in bit;  
        SUM,CARRY: out bit);  
end HALFADDER;
```



Port Modes and Data Types

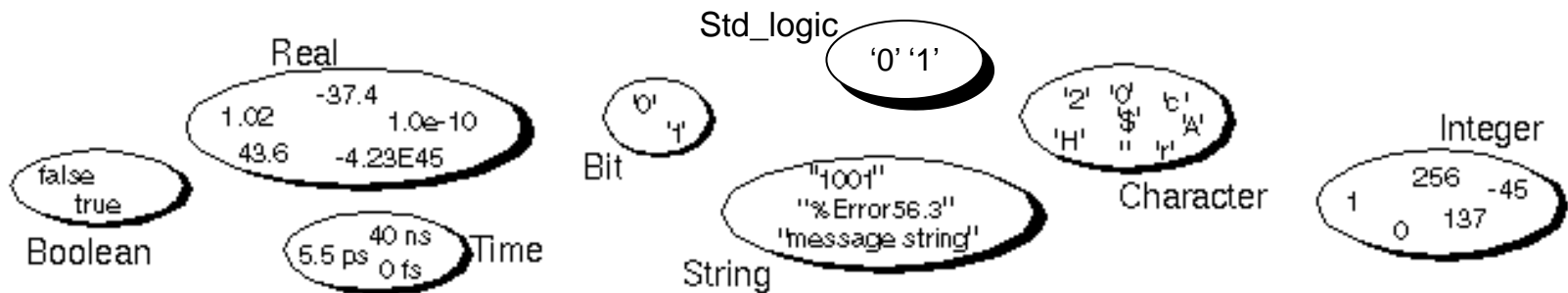- *in*:
 - signal values are read-only
- *out*:
 - signal values are write-only
 - multiple drivers
- *buffer*:
 - comparable to out
 - signal values may be read, as well
 - only 1 driver
- *inout*:
 - bidirectional port



Definition of Array

- Collection of signals of the same type
- Predefined arrays
 - `bit_vector` (array of bit)
 - `string` (array of character)


```
signal A_BUS, Z_BUS : bit_vector (3 downto 0);
```

alternative: `bit_vector(0 to 3)`

```
Z_BUS <= A_BUS
```



```
Z_BUS(3) <= A_BUS(0)
```

 

Types of Assignment for 'bit' Data Types

- Single bit values are enclosed in `' '`
- Vector values are enclosed in `"..."`
 - optional base specification (default: binary)
 - values may be separated by underscores to improve readability

```
architecture EXAMPLE of ASSIGNMENT is

    signal Z_BUS : bit_vector (3 downto 0);
    signal BIG_BUS : bit_vector (15 downto 0);

begin

    -- legal assignments:
    Z_BUS(3) <= '1';
    Z_BUS    <= "1100";

    Z_BUS    <= b"1100";
    BIG_BUS  <= B"0000_0001_0010_0011";

end EXAMPLE;
```

 

Architecture - 1

- **Implementation** of the design

```
architecture ARCHITECTURE_NAME of ENTITY_NAME is  
    -- declarative statements  
begin  
    -- definitive concurrent statements  
end ARCHITECTURE_NAME;
```

- always connected with a specific **entity**
- one entity can have several architectures
- entity ports are available as signals within the architecture
- contains **concurrent statements**

```
architecture RTL of HALFADDER is  
  
begin  
    SUM    <= A xor B;  
    CARRY  <= A and B;  
end RTL;
```



Architecture - 2

- Each architecture is split into an optional *declarative part* and the *definition part*
- **Declarative part** (between the keywords 'is' and 'begin'):
 - new objects that are needed only within the architecture
 - constants, data types, signals (actual), subprograms, etc. can be declared here
 - components are declared here
- **Definition part** (after 'begin'):
 - holds concurrent statements (order not important)
 - can be simple signal assignments, process statements, which group together sequential statements, and component instantiations

Architecture Models - 1

- **Architecture descriptions** can be in the following models:
 - **Structural modeling** - ports
 - **Behavioral:**
 - **Algorithmic** modeling – process with sequential statements
 - **Dataflow** modeling – signals in concurrent statements
 - Mixed
- Both **structural** and **dataflow** describes the entity based on its **implementation**, i.e. connections (of signals or ports)
- Behavioral (**algorithmic**) approach to modeling hardware components is different from the other two methods in that it does not necessarily in any way reflect how the design is implemented
 - basically the **black box approach** to modeling

Structural Model

- Describes a circuit in terms of the **interconnection** of components, consisting of:
 - Components declaration
 - Signal assignments
 - Components instantiation
 - Concurrent statements
- “Connections” are made through:
 - Named association (port mapping using port=>local):
 - left side: “formals” (port names from component declaration)
 - right side: “actuals” (architecture signals)
 - independent of order in component declaration
 - If using unnamed port mapping then order is important

Structural Model: An Example

Entity Declaration

-- Simple Logic Circuit

library ieee, lcdf_vhdl;


use ieee.std_logic_1164.**all**, lcdf_vhdl.func_prims.**all**;

entity s_circuit **is**

port(A,B,C: **in** std_logic;

 F: **out** std_logic);

end s_circuit;

 

Structural Model: An Example

Components Declaration and Signal Assignment

architecture structural_1 **of** s_circuit **is**

component AND2

```
port( in1, in2: in std_logic;  
      out1: out std_logic);
```




end component;

component OR2

```
port( in1, in2: in std_logic;  
      out1: out std_logic);
```

end component;

signal x: std_logic;

   

AND2 and OR2 are described in the
"lcdf_vhdl.func_prims" library

Structural Model: An Example

Connections (Port Mapping)


We can use named association, where order is not important:

begin

```
g0: AND2 port map (in1 =>A, out1 =>x, in2 =>B);
```

```
g1: OR2 port map (in1 =>x, in2=>C, out1 =>F);
```

end structural_1;

 

Component labels (instantiation)

Alternatively, using unnamed association:

begin

```
g0: AND2 port map (A, B, x);
```

```
g1: OR2 port map (x,C,F);
```

end structural_1;

Order must be in (in1,in2,out2)
as per declaration

Behavioral Model: Dataflow

- Behavioral modeling can be done with sequential statements using the process construct or with concurrent statements
- **Dataflow** modeling describes a circuit, using concurrent statements, in terms of its function and the flow of data through the circuit
 - different from the structural modeling that describes a circuit in terms of the interconnection of components
- Consists of:
 - Signal assignment statements
 - Concurrent statements

Dataflow Model: The Example

Entity Declaration

-- Simple Logic Circuit

library ieee;

use ieee.std_logic_1164.all;


entity s_circuit **is**

port(A,B,C: **in** std_logic;

 F: **out** std_logic);

end s_circuit;

 Basically the same, however we are not using any component from the "lcdf_vhdl" library



Dataflow Model: The Example

Signal Assignment & Concurrent Statements

architecture dataflow_1 **of** s_circuit **is**

signal x: std_logic;


begin

x <= A **and** B;

F <= x **or** C;

end dataflow_1;

no components declaration

 

- no port mapping, use operators instead
- dataflow from left to right (in to out)
- these statements execute concurrently

note the statements in dataflow model are based on the circuit implementation, i.e. the path of signals

Behavioral Model: Algorithmic Functional Description a.k.a. “High Level” Behavioral

- Model the function just like writing programming language
 - **black box approach** – no implementation information
 - to model complex components that would be tedious to model using the other methods
 - uses **process** construct
- Consists of:
 - **Process** statements
 - Sensitivity list (parameters)
 - Sequential statements
 - Signal (\leq) and variable ($:=$) assignment statements
 - Wait statements

Process

```
PROCESS_NAME: process (SENSITIVITY_LIST)
begin
  -- SEQUESTIAL STATEMENTS
end process;
```

process name and sensitivity list are optional

- Appear in the body of an architecture declaration just as the signal assignment statement does
- Include sequential statements like those found in software programming languages
- Compute the outputs of the process from its inputs
- No direct correspondence to a hardware implementation
- Signal assignment within process is only evaluated when events occur on the signals in the process' sensitivity list
- The process are performed (or executed) in order from first to last

```
s_process: process (A,B,C)
begin
  -- SEQUESTIAL STATEMENTS
end process;
```

```
process (A,B,C)
begin
  -- SEQUESTIAL STATEMENTS
end process;
```

```
s_process: process
begin
  -- SEQUESTIAL STATEMENTS
end process;
```

Algorithmic Model: The Example

```
-- Simple Logic Circuit  
library ieee, lcdf_vhdl;  
use ieee.std_logic_1164.all;
```

```
entity s_circuit is  
  port( A,B,C: in std_logic;  
         F: out std_logic);  
end s_circuit;
```

```
architecture algorithmic_1 of s_circuit is
```

```
s_process: process (A,B,C)  
  begin  
    F <= (A and B) or C;  
  end process;
```

```
end algorithmic_1;
```



← same as in dataflow

← may have signal assignments

← sensitivity list (optional)

Logic Simulator: Test Bench

- *Logic Simulator* interprets HDL description and uses a defined *stimulus* to produce readable output, such as timing diagram that predicts how hardware will behave
 - the stimulus is called a *test bench*
- *Test bench* is used for generating stimulus for the entity under test
 - allows design verification and detection of functional errors without having to physically create circuit
- *Test bench* is written also in VHDL, which delivers the verification environment for the model
 - stimuli are described as input signals for the model
 - expected model responses can be checked
 - appears as the top hierarchy level, and therefore has neither input- nor output ports

Test Bench: The Example - 1

-- library where s_circuit is described (or can be omitted if s_circuit is already added in the compiler environment)

```
entity tb_scircuit is           ← declare test bench entity, without ports  
end tb_scircuit;
```

```
architecture test_1 of tb_scircuit is
```

```
  component s_circuit  
    port (A, B, C: in std_logic;  
          F: out std_logic);    ← component to test  
                                (must be in library)  
  end component;
```

```
  signal A_I, B_I, C_I, F_I: std_logic;    ← test signals
```

Test Bench: The Example

begin

DUT: s_circuit **port map** (A_I, B_I, C_I, F_I);

- instantiate test component
- DUT is the instance name

STIMULUS: **process**

begin

A_I <= '0'; B_I <= '0'; C_I <= '0'
wait for 10 ns;

A_I <= '0'; B_I <= '0'; C_I <= '1'
wait for 10 ns;

-- and so on ...

end process STIMULUS;

end test_1;

- assign test signals,
- input combinations

configuration cfg_tb_scircuit **of** tb_scircuit **is**


for test_1

end for;

end cfg_tb_scircuit;

← configure to use test_1 architecture

Structural VHDL 2-to-4 Decoder

 

Structural VHDL 2-to-4 Decoder

-- 2-to-4 Line Decoder with Enable: Structural VHDL
-- Description

```
library ieee, lcdf_vhdl;  
use ieee.std_logic_1164.all, lcdf_vhdl.func_prims.all;  
  
entity decoder_2_to_4_w_enable is  
    port( EN, A0, A1: in std_logic;  
          Do, D1, D2, D3: out std_logic);  
end decoder_2_to_4_w_enable;
```

Structural VHDL 2-to-4 Decoder

```
architecture structural_1 of decoder_2_to_4_w_enable is  
  
  component NOT1  
    port( in1: in std_logic;  
          out1: out std_logic);  
  end component;  
  
  component AND2  
    port( in1, in2: in std_logic;  
          out1: out std_logic);  
  end component;  
  
  signal A0_n, A1_n, No, N1, N2, N3: std_logic;
```

Structural VHDL 2-to-4 Decoder

begin

g0: NOT1 port map (in1 => A0, out1 => A0_n);

g1: NOT1 port map (in1 => A1, out1 => A1_n);

g2: AND2 port map (in1 => A0_n, in2 => A1_n, out1 => N0);

g3: AND2 port map (in1 => A0, in2 => A1_n, out1 => N1);

g4: AND2 port map (in1 => A0_n, in2 => A1, out1 => N2);

g5: AND2 port map (in1 => A0, in2 => A1, out1 => N3);

g6: AND2 port map (in1 => EN, in2 => N0, out1 => D0);


g7: AND2 port map (in1 => EN, in2 => N1, out1 => D1);

g8: AND2 port map (in1 => EN, in2 => N2, out1 => D2);


g9: AND2 port map (in1 => EN, in2 => N3, out1 => D3);

end structural_1;

Structural VHDL 2-to-4 Decoder

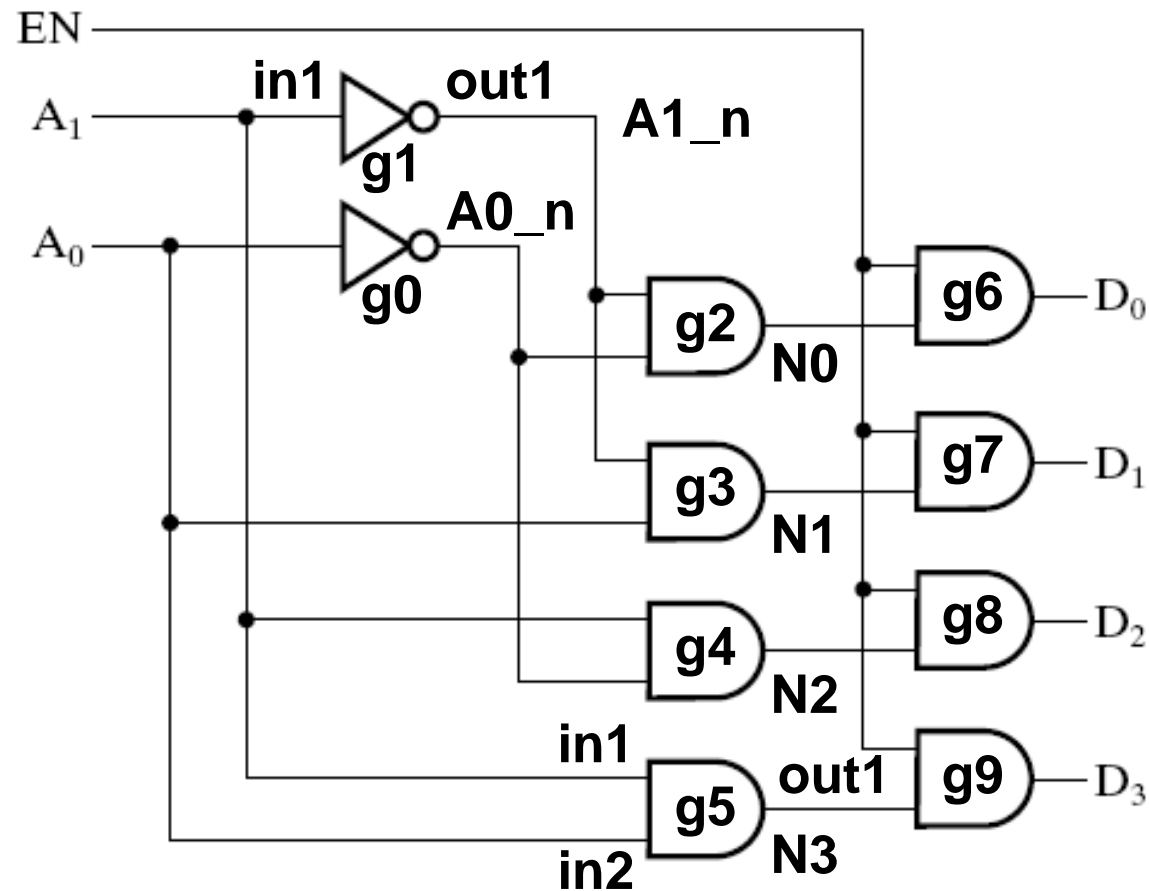

Structural VHDL 4-to-1 Multiplexer

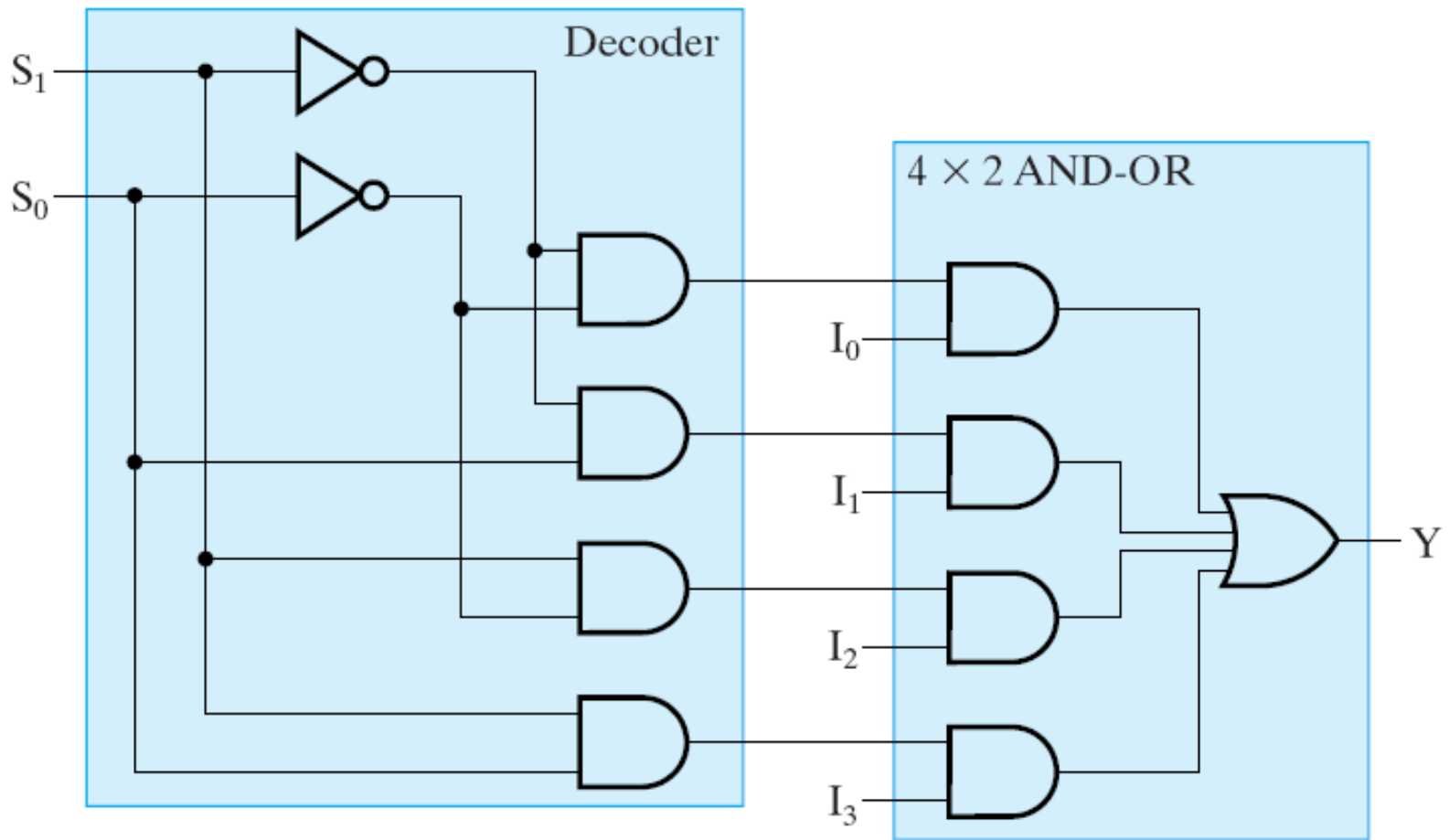

Structural VHDL 4-to-1 Multiplexer

-- 4-to-1 Line Multiplexer: Structural VHDL Description

```
library ieee, lcdf_vhdl;
```

```
use ieee.std_logic_1164.all, lcdf_vhdl.func_prims.all;
```

```
entity multiplexer_4_to_1_st is
```

```
  port( S: in std_logic_vector(0 to 1);
```

```
        I: in std_logic_vector(0 to 3);
```

```
        Y: out std_logic);
```

```
end multiplexer_4_to_1_st;
```

Structural VHDL 4-to-1 Multiplexer

```
architecture structural_2 of multiplexer_4_to_1_st is
```

```
  component NOT1
```

```
    port( in1: in std_logic;  
          out1: out std_logic);
```

```
end component;
```

```
  component AND2
```

```
    port( in1, in2: in std_logic;  
          out1: out std_logic);
```

```
end component;
```


Structural VHDL 4-to-1 Multiplexer

```
component OR4  
    port( in1, in2, in3, in4: in std_logic;  
          out1: out std_logic);  
end component;  
  
signal S_n: std_logic_vector(0 to 1);  
signal D, N: std_logic_vector(0 to 3);
```

Structural VHDL 4-to-1 Multiplexer

begin

g0: NOT1 port map (S(0), S_n(0));

g1: NOT1 port map (S(1), S_n(1));

g2: AND2 port map (S_n(1), S_n(0), D(0));

g3: AND2 port map (S_n(1), S(0), D(1));

g4: AND2 port map (S(1), S_n(0), D(2));

g5: AND2 port map (S(1), S(0), D(3));

g6: AND2 port map (D(0), I(0), N(0));

g7: AND2 port map (D(1), I(1), N(1));

g8: AND2 port map (D(2), I(2), N(2));

g9: AND2 port map (D(3), I(3), N(3));

g10: OR4 port map (N(0), N(1), N(2), N(3), Y);

end structural_2;

Dataflow VHDL 2-to-4 Decoder

- A dataflow description describes a circuit in terms of function rather than structure
- Concurrent assignment statements are executed concurrently whenever one of the values on the right-side of the statement changes

Dataflow VHDL 2-to-4 Decoder

-- 2-to-4 Line Decoder: Dataflow VHDL Description

```
library ieee, lcdf_vhdl;  
use ieee.std_logic_1164.all;  
  
entity decoder_2_to_4_w_enable is  
    port( EN, A0, A1: in std_logic;  
          D0, D1, D2, D3: out std_logic);  
end decoder_2_to_4_w_enable;
```

Dataflow VHDL 2-to-4 Decoder

architecture dataflow_1 **of** decoder_2_to_4_w_enable **is**

signal A0_n, A1_n: std_logic;

begin

A0_n <= **not** A0;

A1_n <= **not** A1;

D0 <= A0_n **and** A1_n **and** EN;

D1 <= A0 **and** A1_n **and** EN;

D2 <= A0_n **and** A1 **and** EN;

D3 <= A0 **and** A1 **and** EN;

end dataflow_1;

Behavioral VHDL 4-to-1 Multiplexer (1) - 1 (using When-Else)

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity multiplexer_4_to_1_we is  
    port ( S : in std_logic_vector(1 downto 0);  
          I : in std_logic_vector(3 downto 0);  
          Y : out std_logic);  
end multiplexer_4_to_1_we;
```

Behavioral VHDL 4-to-1 Multiplexer (1) - 2

(using When-Else)

```
architecture function_table of multiplexer_4_to_1 is  
begin  
    Y <= I(0) when S = "00" else  
        I(1) when S = "01" else  
        I(2) when S = "10" else  
        I(3) when S = "11" else  
            'X';  
end function_table;
```

Behavioral VHDL 4-to-1 Multiplexer (2) - 1 (using With-Select)

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity multiplexer_4_to_1_ws is  
    port (S : in std_logic_vector(1 downto 0);  
          I : in std_logic_vector(3 downto 0);  
          Y : out std_logic);  
end multiplexer_4_to_1_ws;
```


Behavioral VHDL 4-to-1 Multiplexer (2) - 2

(using With-Select)

```
architecture function_table_ws of multiplexer_4_to_1_ws is  
begin  
  with S select  
    Y <= I(0) when "00",  
      I(1) when "01",  
      I(2) when "10",  
      I(3) when "11",  
      'X' when others;  
end function_table_ws;
```

Behavioral VHDL 4-to-1 Multiplexer

- **When-else** permits decisions on multiple distinct signals
 - Synthesis typically results in more complex logical structure
 - Needs to take into account priority order
- **With-select** can depend on only a single Boolean condition
- ‘**x**’ is an ‘**unknown**’ value, which will be generated during simulation. However, **Y** will always take on a **0** or **1** value in an actual circuit.

More examples: hierarchical

```
-- 4-bit Adder: Hierarchical  
Dataflow/Structural  
-- (See Figures 4-4 and 4-5 for logic  
diagrams)
```

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity half_adder is  
    port (x, y : in std_logic;  
          s, c : out std_logic);  
end half_adder;  
  
architecture dataflow_3 of  
    half_adder is  
  
begin  
    s <= x xor y;  
    c <= x and y;  
end dataflow_3;
```

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity full_adder is  
    port (x, y, z : in std_logic;  
          s, c : out std_logic);  
end full_adder;  
  
architecture struc_dataflow_3 of  
    full_adder is  
  
component half_adder  
    port(x, y : in std_logic;  
          s, c : out std_logic);  
end component;  
  
signal hs, hc, tc: std_logic;  
-- use 2 HA to make 1 FA  
begin  
    HA1: half_adder  
        port map (x, y, hs, hc);  
    HA2: half_adder  
        port map (hs, z, s, tc);  
    c <= tc or hc;  
end struc_dataflow_3;
```

```

library ieee;
use ieee.std_logic_1164.all;

entity adder_4 is
    port(B, A : in std_logic_vector(3 downto 0);
        C0 : in std_logic;
        S : out std_logic_vector(3 downto 0);
        C4: out std_logic);
end adder_4;

architecture structural_4 of adder_4 is

    component full_adder
        port(x, y, z : in std_logic;
            s, c : out std_logic);
    end component;

    signal C: std_logic_vector(4 downto 0);
    -- use 4 FA to make 4-bit FA
    begin
        Bit0: full_adder
        port map (B(0), A(0), C(0), S(0), C(1));
        Bit1: full_adder
        port map (B(1), A(1), C(1), S(1), C(2));
        Bit2: full_adder
        port map (B(2), A(2), C(2), S(2), C(3));
        Bit3: full_adder
        port map (B(3), A(3), C(3), S(3), C(4));
        C(0) <= C0;
        C4 <= C(4);
    end structural_4;

```

previous slide



More examples: high-level behavioral

```
-- 4-bit Adder: Behavioral Description
-- compare with dataflow/structural description in previous slides
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity adder_4_b is
    port(B, A : in std_logic_vector(3 downto 0);
        C0 : in std_logic;
        S : out std_logic_vector(3 downto 0);
        C4: out std_logic);
end adder_4_b;

architecture behavioral of adder_4_b is

    signal sum : std_logic_vector(4 downto 0);

begin
    sum <= ('0' & A) + ('0' & B) + ("0000" & C0);
    C4 <= sum(4);
    S <= sum(3 downto 0);
end behavioral;
```

References

- http://www.seas.upenn.edu/~ese201/vhdl/vhdl_primer.html
- http://www.vhdl-online.de/tutorial/englisch/t_2.htm
- <http://www.gmvhdl.com/VHDL.html>
- M Morris Mano, Charles R Kime, “Logic and Computer Design Fundamentals”, 4th Edition

Summary

- HDL – high level representation of hardware
- VHDL is one of few popular HDL
- VHDL describes hardware in three models:
 - Structural
 - Behavioral - Dataflow
 - Behavioral – Algorithmic (High Level)
- Test Bench is VHDL describing stimulus to the inputs of a hardware device to observe its output