

Tutorial 2 – Sample Solution

Digital Logic

CO 2206 Computer Organization

Logic Gate ICs – Ans.

- **Task 1:** Determine (research) a part number of the IC for the following logic gates:
 - 2-input NAND gates: 7400 (can be any series/manufacturer) or CD4011
 - 3-input NAND gates: 7410 or CD4023
 - 2-input NOR gates: 7402 or CD4001
 - 3-input NOR gates: 7427 or CD4025
 - NOT gates: 7404 or CD4049
 - OR gates: 7432 or CD4071
 - AND gates: 7408 or CD4073, CD4081
 - XOR gates: 7486, 74136, 74386

Boolean Algebra – 1 – Ans.1


- Task 2:** Solve the following problems

- Prove the *absorption law* using *Boolean Algebra*: $x \cdot (x+y) = x$


$$\begin{aligned}
 x \cdot (x+y) &= (x \cdot x) + (x \cdot y) && \text{distribution law} \\
 &= x + (x \cdot y) && \text{idempotence law} \\
 &= (x \cdot 1) + (x \cdot y) && \text{identity law} \\
 &= x \cdot (1 + y) && \text{distribution law} \\
 &= x \cdot 1 && \text{null law} \\
 &= x && \text{identity law}
 \end{aligned}$$

- Prove the implementations of *AND*, *OR* and *NOT* using *NAND*

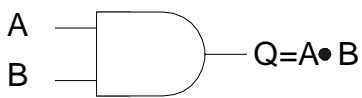- Prove above using *Truth Table* and *Boolean Algebra*



A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

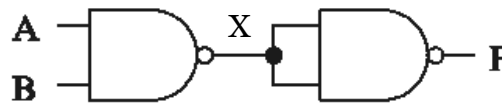

A	B	X	F
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1

$F = (X \cdot X)'$
 $= X'$ idempotent
 $= (A \cdot B)''$
 $= A \cdot B$ double negation

Boolean Algebra – 1 – Ans.2

– Prove equivalence, $(xyz)' = x' + y' + z'$ by means of *truth table*

x	y	z	xyz	(xyz)'	x'	y'	z'	x'+y'+z'
0	0	0	0	1	1	1	1	1
0	0	1	0	1	1	1	0	1
0	1	0	0	1	1	0	1	1
0	1	1	0	1	1	0	0	1
1	0	0	0	1	0	1	1	1
1	0	1	0	1	0	1	0	1
1	1	0	0	1	0	0	1	1
1	1	1	1	0	0	0	0	0

Boolean Algebra – 1 – Ans.3

– Prove equivalence by means of *Boolean algebra*:

- $(x+y)' \cdot (x'+y) = 0$
 - $xy = (x+y)(x+y')(x'+y)$
 - $xy + x'z = xy + x'z + yz$
- | | |
|---|-------------|
| $(x+y)' \cdot (x'+y) = (x' \cdot y') \cdot (x \cdot y)$ | de Morgan |
| $= (x' \cdot y' \cdot x) \cdot y$ | associative |
| $= [(x' \cdot x) \cdot y'] \cdot y$ | commutative |
| $= (0 \cdot y') \cdot y$ | idempotent |
| $= 0 \cdot y = 0$ | null, null |

$$\begin{aligned}
 (x+y)(x+y')(x'+y) &= (x+y)(x+y)(x+y')(x'+y) && \text{idempotent} \\
 &= (x+y)(x+y')(x+y)(x'+y) && \text{associative} \\
 &= [xx+xy'+xy+yy'] [xx'+xy+yx'+yy] && \text{distribution} \\
 &= [x+x(y+y')+0] [0+y(x+x')+y] && \text{idempotent, distribution, complement} \\
 &= (x+x \cdot 1)(y \cdot 1+y) && \text{complement} \\
 &= (x+x)(y+y) && \text{identity} \\
 &= xy && \text{idempotent}
 \end{aligned}$$

$$\begin{aligned}
 xy+x'z+yz &= xy + x'z + yz(x + x') && \text{complement and identity} \\
 &= xy + x'z + xyz + x'yz && \text{distribution} \\
 &= xy(1+z) + x'z(1+y) && \text{distribution} \\
 &= xy + x'z && \text{null}
 \end{aligned}$$

Boolean Algebra - 2

- **Task 3:** Solve the following problems
 - Demonstrate by means of truth tables the validity of the following identity:
 - XOR's inverse: $(x \oplus y)' = x \oplus y'$
 - Prove the identity of each of the following *Boolean equations*, using algebraic manipulation:
 - Prove $A'B' + AB = (A \oplus B)'$. Hint: use double negation
 - $(a \oplus b)' \oplus c = a'b'c' + abc' + a'bc + ab'c$
 - Simplify the following logic functions using *Boolean algebra* rules:
 - $ab + ab'$
 - $xyz + x'y + xyz'x' + xy + xz' + xy'z'$
 - Obtain the truth table of the function $(xy + z)(y + xz)$ and express the function in *sum-of-minterms* and *product-of-maxterms*

Boolean Algebra – 2 – Ans.1

x	y	$x \oplus y$	$(x \oplus y)'$	x	y'	$x \oplus y'$
0	0	0	1	0	1	1
0	1	1	0	0	0	0
1	0	1	0	1	1	0
1	1	0	1	1	0	1

$$\begin{aligned}
 A'B' + AB &= (A'B' + AB)'' && \text{double negating} \\
 &= ((A'B')'(AB))' && \text{de Morgan on inner negation} \\
 &= ((A+B)(A'+B'))' && \text{de Morgan} \\
 &= (AA' + AB' + A'B + BB')' && \text{distribution} \\
 &= (0 + AB' + A'B + 0)' && \text{complement} \\
 &= (A \oplus B)' && \text{XNOR}
 \end{aligned}$$

$$\begin{aligned}
 (a \oplus b)' \oplus c &= (a \oplus b)'c' + (a \oplus b)c && \text{XOR: } x \oplus y = x'y + xy' \\
 &= (a \oplus b)'c' + (a \oplus b)c && \text{XOR inverse: } (x \oplus y)' = x \oplus y' \\
 &= (ab + a'b)'c' + (ab' + a'b)c && \text{XOR: } x \oplus y = x'y + xy' \\
 &= abc' + a'b'c' + ab'c + a'bc && \text{distributive} \\
 &= a'b'c' + abc' + a'bc + ab'c && \text{associative}
 \end{aligned}$$

$$\begin{aligned}
 ab + ab' &= a(b+b') && \text{distributive} \\
 &= a \cdot 1 && \text{complement} \\
 &= a && \text{identity}
 \end{aligned}$$

Boolean Algebra – 2 – Ans.2

$$\begin{aligned}
 &xyz + x'y + xyz'x' + xy + xz' + xy'z' \\
 = &xyz + x'y + yz'.0 + xy + xz' + xy'z' \quad \text{complement: } xx' = 0 \\
 = &xy(z+1) + x'y + xz'(y+1) \quad \text{null: } yz'.0 = 0; \text{ distributive } ab+a = a(b+1) \\
 = &xy + x'y + xz' \quad \text{null} \\
 = &y(x+x') + xz' \quad \text{distributive} \\
 = &y + xz' \quad \text{complement}
 \end{aligned}$$

Let $F = (xy+z)(y+xz)$

x	y	z	minterms	maxterms	xy	xz	xy + z	y + xz	F
0	0	0	m0 = x'y'z'	M0 = x+y+z	0	0	0	0	0
0	0	1	m1 = x'y'z	M1 = x+y+z'	0	0	1	0	0
0	1	0	m2 = x'yz'	M2 = x+y'+z	0	0	0	1	0
0	1	1	m3 = x'yz	M3 = x+y'+z'	0	0	1	1	1
1	0	0	m4 = xy'z'	M4 = x'+y+z	0	0	0	0	0
1	0	1	m5 = xy'z	M5 = x'+y+z'	0	1	1	1	1
1	1	0	m6 = xyz'	M6 = x'+y'+z	1	0	1	1	1
1	1	1	m7 = xyz	M7 = x'+y'+z'	1	1	1	1	1

$$F(x,y,z) = \sum m(3,5,6,7)$$

$$F(x,y,z) = \prod M(0,1,2,4)$$

;sum of minterms are sum of m terms when F=1

;product of maxterms are product of M terms when F=0