

Tutorial 3 – Sample Solution


Logic Circuit Design

CO 2206 Computer Organization


Task 1: Ans.1

- Simplify the following Boolean functions using Karnaugh map:
 - $F(x,y,z) = \sum m(0,1,5,7)$
 - $F(x,y,z) = \sum m(0,1,2,4,6)$
 - $F(w,x,y,z) = \sum m(1,4,6,7,8,9,10,11,15)$
 - $F(A,B,C,D) = \sum m(0,2,5,6,8,10,13,14,15)$


$$F = x'y + xz$$

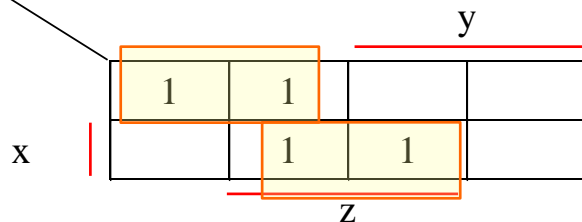

$$F = z' + x'y'$$

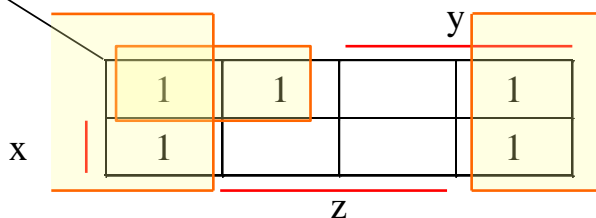


$$F = x'y'z' + w'xz' + xyz + wx'$$

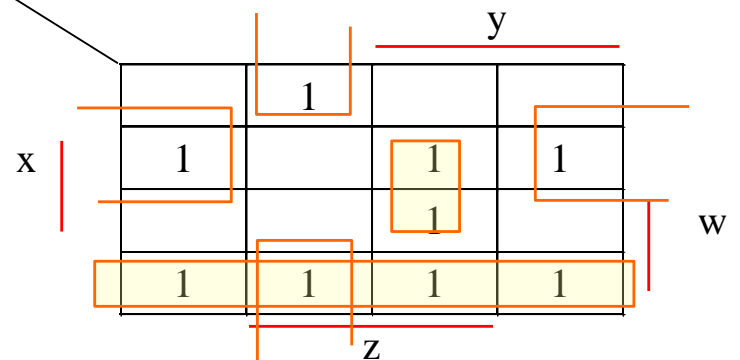

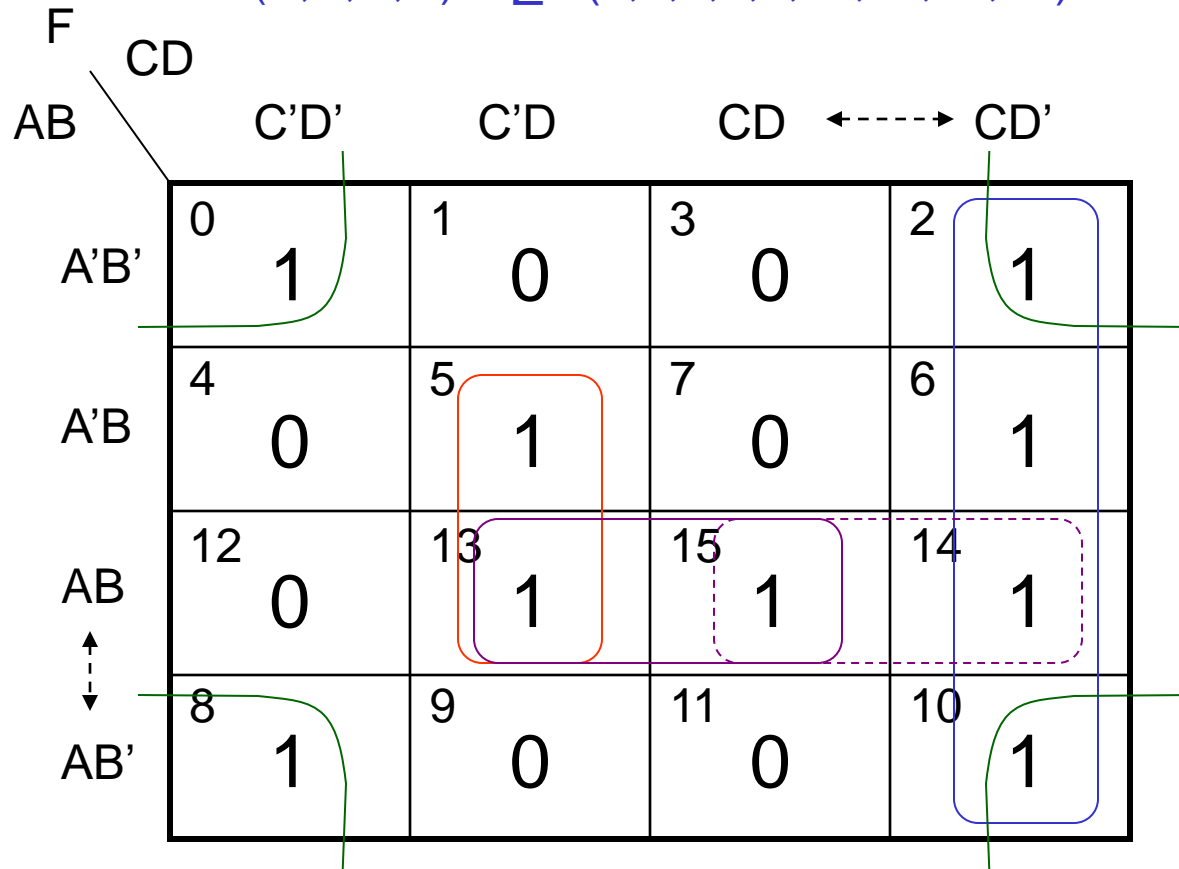Task 1: Ans.2

$$F(A,B,C,D) = \sum m(0,2,5,6,8,10,13,14,15)$$




$$F = B'D' + CD' + BCD' + ABD$$

Task 1: Ans.3

- Find the simplest sum of products form for the function **F** using the don't care condition **G**, where
 - $F(a,b,c,d) = \sum m(0,2,8,10,14)$ and
 - $G(a,b,c,d) = \sum m(5,7,12,13)$

$$F = b'd' + ad'$$

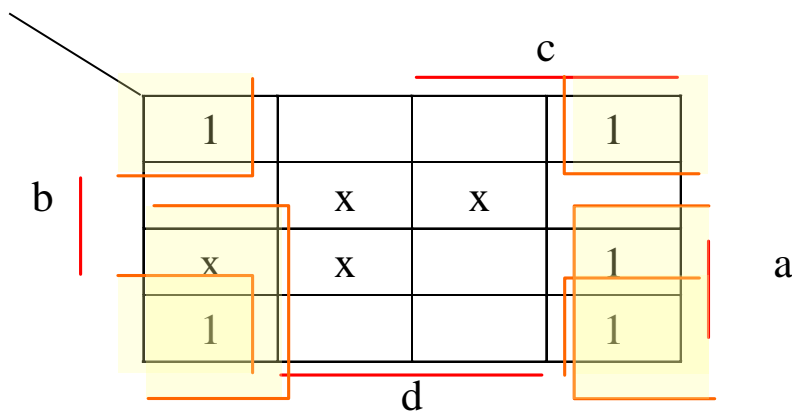

Task 1: Ans.4

- Simplify $F(A,B,C,D) = \prod M(1,3,4,6,9,11)$ together with the don't care conditions $d(A,B,C,D) = \sum m(0,2,5,10,12,14)$ in (i) *sum of products* and (ii) *products of sums*

i) $F = B'D' + BD$

	C		
	x	0	0
B	0	x	1
	x	1	1
	1	0	0
		D	
			x


ii) $F = (B'+D)(B+D')$

	C'		
	x	0	0
B'	0	x	1
	x	1	1
	1	0	0
		D'	
			x
			A'

Task 1: Ans.5

- Simplify the even parity function using XOR

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

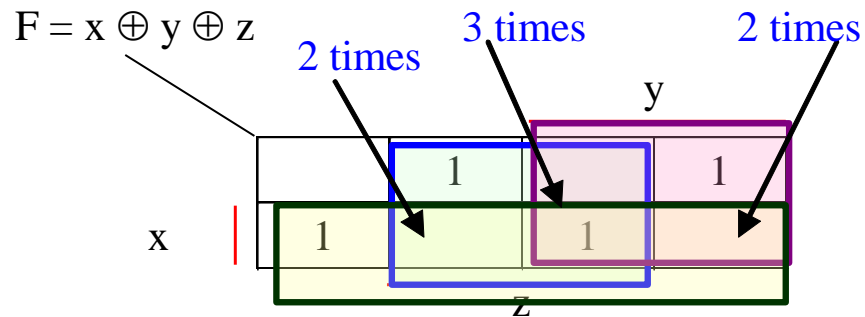

Task 2: Ans.1

- Minimize the following functions using the *Quine-McCluskey* minimization:
 - $F(x,y,z) = \sum m(0,1,2,4,6)$
 - $f_1(x_1, x_2, x_3, x_4) = \sum m(0, 6, 7, 9, 13, 14, 15)$
 - $f_2(x_1, x_2, x_3, x_4, x_5) = \sum m(0, 2, 6, 10, 13, 16, 18, 20, 21, 23, 24, 26, 30, 31)$

Task 2: Ans.2


$$F(x,y,z) = \sum m (0,1,2,4,6)$$

no.		xyz		min	group
0	=	000	≡	$x'y'z'$	0
1	=	001	≡	$x'y'z$	1
2	=	010	≡	$x'yz'$	1
4	=	100	≡	$xy'z'$	1
6	=	110	≡	xyz'	2

Task 2: Ans.3

	(a)	(b)	(c)
Group 0	(0) $x'y'z'$ ✓	$x'y'$ (0,1)	z' (0,2,4,6)
Group 1	(1) $x'y'z$ ✓	$x'z'$ (0,2) ✓	z' (0,4,2,6)
	(2) $x'yz'$ ✓	$y'z'$ (0,4) ✓	
	(4) $xy'z'$ ✓	yz' (2,6) ✓	
Group 2	(6) xyz' ✓	xz' (4,6) ✓	

Task 2: Ans.4

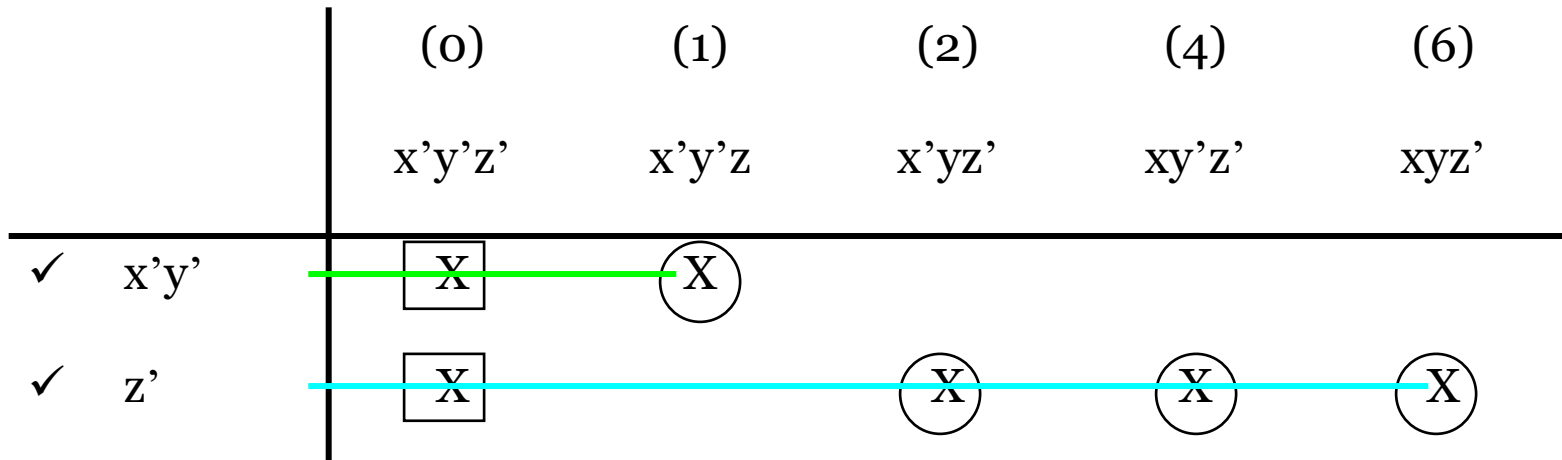

✓ = essential prime implicant

$$F = x'y' + z'$$

Task 2: Ans.5

$$f_1(x_1, x_2, x_3, x_4) = \sum(0, 6, 7, 9, 13, 14, 15)$$

Calculation of the tuples:

	$x_4x_3x_2x_1$	2^1 -tuple	2^2 -tuple
0	0 0 0 0	(6,7) 0 1 1 - ✓	[(6,7)(14,15)] - 1 1 -
6	0 1 1 0 ✓	(6,14) - 1 1 0 ✓	[(6,14)(7,15)] - 1 1 -
9	1 0 0 1 ✓	(9,13) 1 - 0 1	
7	0 1 1 1 ✓	(7,15) - 1 1 1 ✓	
13	1 1 0 1 ✓	(13,15) 1 1 - 1	
14	1 1 1 0 ✓	(14,15) 1 1 1 - ✓	
15	1 1 1 1 ✓		

Determination of the cheapest overlapping:

2^n	0	6	9	7	13	14	15	a
(6,7,14,15)		⊗		⊗		⊗	⊗	*
(9,13)			⊗		⊗			*
(13,15)					*		*	
(0)	⊗							*

(row a: * = essential prime implicant)

In this case these prime implicants already determine a cover

$$\Rightarrow f = x_2x_3 + x_1x'_2x_4 + x'_1x'_2x'_3x'_4$$

Task 2: Ans.6

b) $f_2(x_1, x_2, x_3, x_4, x_5) = \sum(0, 2, 6, 10, 13, 16, 18, 20, 21, 23, 24, 26, 30, 31)$

Calculation of the tuples:

	$x_5x_4x_3x_2x_1$	2^1 -tuple	2^2 -tuple
0	0 0 0 0 0 ✓	(0,2) 0 0 0 - 0 ✓	(0,2,16,18) - 0 0 - 0 (0,16,2,18)
2	0 0 0 1 0 ✓	(0,16) - 0 0 0 0	(2,18,10,26) - - 0 1 0
16	1 0 0 0 0 ✓	(2,6) 0 0 - 1 0	(16,18,24,26) 1 - 0 - 0 (16,24,18,26)
6	0 0 1 1 0 ✓	(2,10) 0 - 0 1 0	
10	0 1 0 1 0 ✓	(2,18) - 0 0 1 0 ✓	
18	1 0 0 1 0 ✓	(16,18) 1 0 0 - 0 ✓	
20	1 0 1 0 0 ✓	(16,20) 1 0 - 0 0	
24	1 1 0 0 0 ✓	(16,24) 1 - 0 0 0	
		(10,26) - 1 0 1 0 ✓	
13	0 1 1 0 1	(18,26) 1 - 0 1 0	
21	1 0 1 0 1 ✓	(20,21) 1 0 1 0 -	
26	1 1 0 1 0 ✓	(24,26) 1 1 0 - 0 ✓	
23	1 0 1 1 1 ✓	(21,23) 1 0 1 - 1	
30	1 1 1 1 0 ✓	(26,30) 1 1 - 1 0	
31	1 1 1 1 1 ✓	(23,31) 1 - 1 1 1	
		(30,31) 1 1 1 1 -	

Task 2: Ans.7

Determination of the cheapest overlapping:

2^n	0	2	16	6	10	18	20	24	13	21	26	23	30	31	a	b	c
(0,2,16,18)	⊗	⊠	⊠			⊠									*	*	*
(2,18,10,26)		*			*	*					*				**	**	**
(16,18,24,26)			*			⊠		⊗			⊠				*	*	*
(2,6)		⊠		⊗											*	*	*
(2,10)		*			*												
(16,20)			*				*										**
(20,21)							*			*					**	**	
(21,23)										*		*				**	**
(26,30)											*		*		**		
(23,31)												*		*	**		
(30,31)													*	*		**	**
(13)									⊗						*	*	*

(rows a,b,c: * = essential prime implicant, ** = additional implicants selected to get an overlapping)

One possible overlapping (using the implicants from row b)








$$f = x'_1x'_3x'_4 + x'_1x_2x'_3 + x'_1x'_3x_5 + x'_1x_2x'_4x'_5 + x'_1x'_2x'_4x_5 + x_1x_3x'_4x_5 + x_2x_3x_4x_5 + x_1x'_2x_3x_4x'_5$$

Another possible overlapping (using the implicants from row c)

$$f = x'_1x'_3x'_4 + x'_1x_2x'_3 + x'_1x'_3x_5 + x'_1x_2x'_4x'_5 + x'_2x_3x'_4x_5 + x'_1x_2x_4x_5 + x_2x_3x_4x_5 + x_1x'_2x_3x_4$$




Task 3: Ans.1

- Ignoring gate-input cost:
 - Implement all functions in **Task 1** using any combination of logic gates

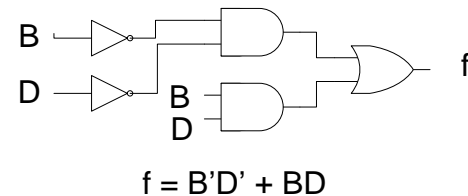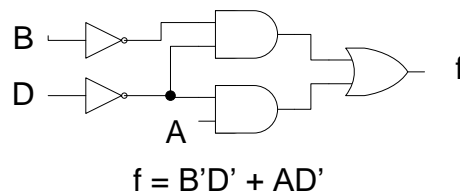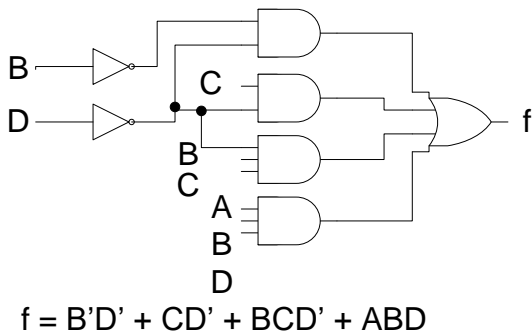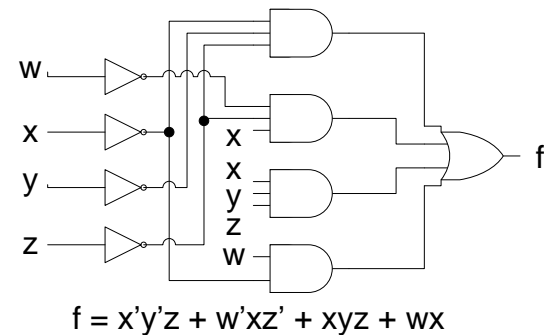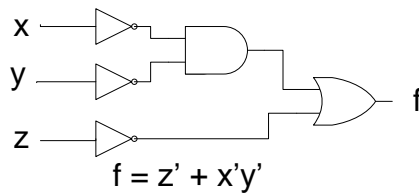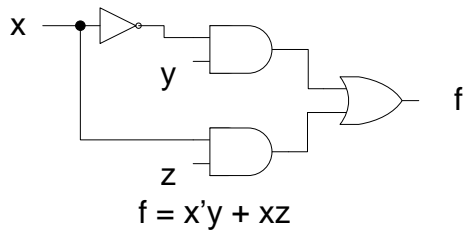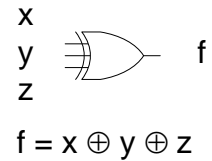

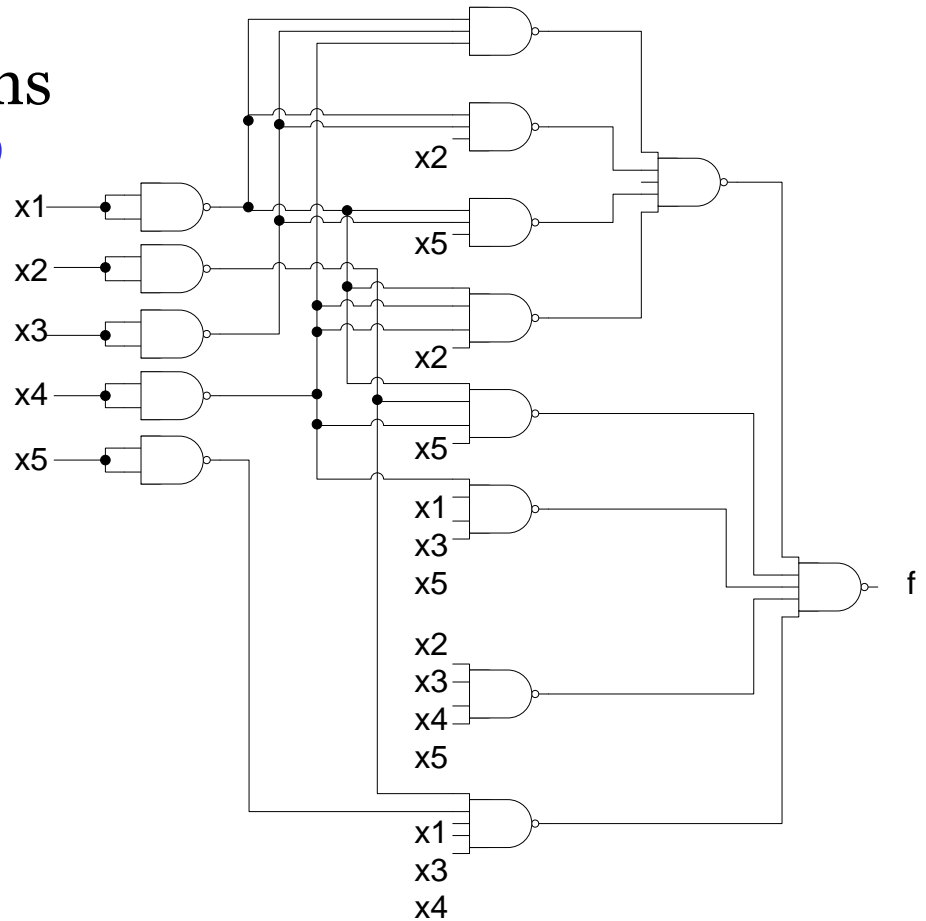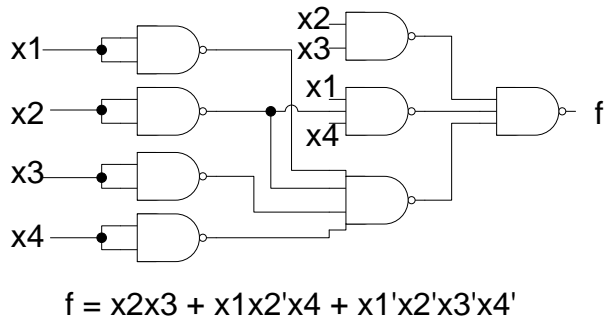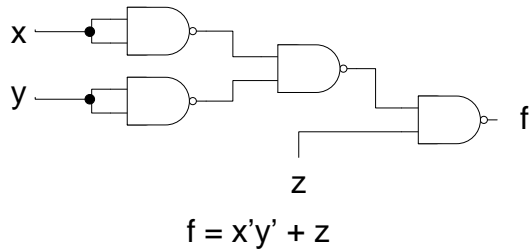Task 3: Ans.1

– Implement all functions in Task 2 using **NAND** only





$f = x_1'x_3'x_4' + x_1'x_2x_3' + x_1'x_3'x_5 + x_1'x_2x_4'x_5' + x_1'x_2'x_4'x_5 + x_1x_3x_4'x_5 + x_2x_3x_4x_5 + x_1x_2'x_3x_4x_5'$

Task 3: Ans.1

- Draw the *NOR* implementation of the function $F = \Sigma m(0,1,2,8,10,11,14,15)$. Hint: Use $F' = \text{SOP}$.

$$F' = BC' + AC'D + A'CD + A'BC$$

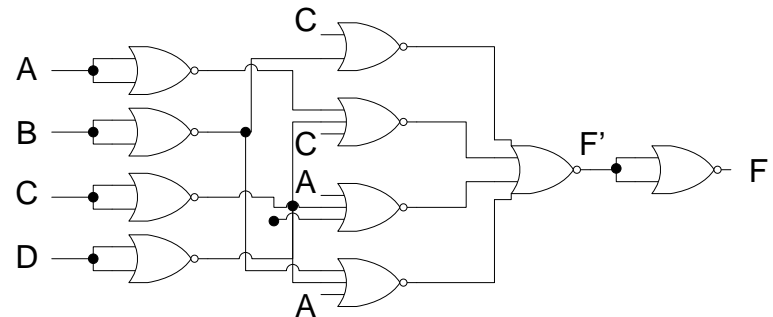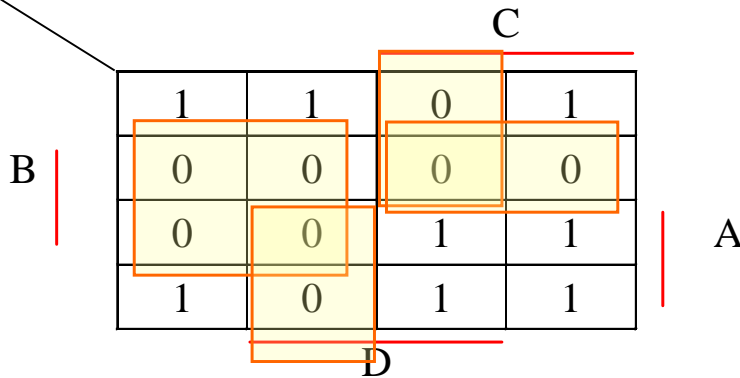

$$\begin{aligned}
 F' &= BC' + AC'D + A'CD + A'BC \\
 &= (B'+C)' + (A'+C+D)'+ (A+C'+D)'+ (A+B'+C)'
 \end{aligned}$$