

Tutorial 4

Combinational Logic

CO 2206 Computer Organization

CLN Functional Block ICs

- **Task 1:** Determine (research for) the part numbers and descriptions for decoder, encoder, multiplexer, demultiplexer and full adder IC (TTL)
 - there will be different versions for each type of IC, e.g. different sizes of decoder
 - state up to three part number for each type (if available), which you feel will be useful (or make sense to you from what you learnt in the lectures)

Using the Functional Blocks

- **Task 2:** Implement the following functions using an appropriate decoder:
 - $F(x,y,z) = \sum m(0,1,2,4,6)$
 - $F(w,x,y,z) = \sum m(1,4,6,7,8,9,10,11,15)$
- **Task 3:** Implement the above functions using an appropriate Multiplexer.
- **Task 4:** Design a circuit that multiplies a 4-bit multiplicand by the constant 1010