


Tutorial 5 – Sample Solutions

VHDL

CO 2206 Computer Organization

Task 1

- For the logic circuit given below,
 - Determine the Boolean function for A_0 , A_1 and V .
 - Write a high-level behavioral VHDL description to describe it.
 - Write a structural VHDL description to describe it.

 

Task 1: Ans.

- $A_0 = B_3 + D_2'D_1$; $A_1 = D_3 + D_2$; $V = D_3 + D_2 + D_1 + D_0$

-- Task 1

-- Behavioral VHDL Description

```
library ieee, lcdf_vhdl;  
use ieee.std_logic_1164.all, lcdf_vhdl.func_prims.all;
```

```
entity question3_cct is  
    port(D3,D2,D1,D0:in std_logic;  
         A0,A1,V:out std_logic);  
end question3_cct;
```

architecture dataflow_1 of question3_cct is

begin

```
A0 <= D3 or ( (not D2) and D1);  
A1 <= D3 or D2;  
V <= D3 or D2 or D1 or D0;
```

end structural_1;

-- Task 1

-- Structural VHDL Description

```
library ieee, lcdf_vhdl;  
use ieee.std_logic_1164.all, lcdf_vhdl.func_prims.all;
```

```
entity question3_cct is  
    port(D3,D2,D1,D0:in std_logic;  
         A0,A1,V:out std_logic);  
end question3_cct;
```

architecture structural_1 of question3_cct is

-- complete this section with gates declaration

signal D2_n,N1: std_logic;

begin


```
g0: NOT1 port map(D2,D2_n);  
g1: AND2 port map(D2_n,D1,N1);  
g2: OR2 port map(D3,N1,A0);  
g3: OR2 port map(D3,D2,A1);  
g4: OR4 port map(D3,D2,D1,D0,V);
```

end structural_1;

CO 2206


Task 2

- Write a dataflow description for the circuit in the figure below by using the Boolean equation for the output F.
- Write a test bench to simulate the operation of the circuit for all input combinations.

 

Task 2. Ans (1)

- Label internal signals

 

Task 2. Ans (2) Dataflow

```
-- data flow for Tutorial 5, Task 2
library ieee;
use ieee.std_logic_1164.all;
entity comb_ckt_2 is
    port (X,Y,Z: in std_logic;
          F: out std_logic);
end comb_ckt_2;

architecture dataflow_1 of comb_ckt_2 is

    signal a,b,c,d,e: std_logic;

begin
    a <= X nand Y; b<= X nand a; c <= Y nand a;
    d <= b nand (c nand Z); e <= c nand Z;
    F <= d nand e;
end dataflow_1;
```

Task 2. Ans (2) Testbench

```
-- Test bench for Tutorial 5, Task 2
library ieee;
use ieee.std_logic_1164.all;
entity comb_ckt_2_tb is
end comb_ckt_2_tb;

architecture testbench_1 of comb_ckt_2 is

component comb_ckt_2 is
    port (X,Y,Z: in std_logic;
          F: out std_logic);
end component;

signal Xt,Yt,Zt,Ft: std_logic;

begin
    DUT: comb_ckt_2 port map (Xt,Yt,Zt,Ft);
    STIMULUS: process
        begin
            Xt <= '0'; Yt <= '0'; Zt <= '0';
            wait for 10 ns;
            Xt <= '0'; Yt <= '0'; Zt <= '1';
            wait for 10 ns;
            Xt <= '0'; Yt <= '1'; Zt <= '0';
            wait for 10 ns;
            Xt <= '1'; Yt <= '0'; Zt <= '0';
            wait for 10 ns;
            Xt <= '1'; Yt <= '0'; Zt <= '1';
            wait for 10 ns;
            Xt <= '1'; Yt <= '1'; Zt <= '0';
            wait for 10 ns;
            Xt <= '1'; Yt <= '1'; Zt <= '1';
            wait for 10 ns;
        end process STIMULUS;
end testbench_1;
```

Task 3


- Find a logic diagram representing minimum two-level logic to implement the VHDL dataflow description below. Note that complemented inputs are available.

```
-- Tutorial 5, Task 3
library ieee;
use ieee.std_logic_1164.all;
entity comb_ckt_3 is
    port (a, b, c, d, a_n, b_n, c_n, d_n: in std_logic;
          f, g: out std_logic);
-- a_n, b_n, ... are complements of a, b, ..., respectively
end comb_ckt_3;

architecture dataflow_1 of comb_ckt_3 is
begin
    f <= b and ((a or (a_n and c)) or (b_n and (c and d_n)));
    g <= b and (c or (a_n and c_n) or (c_n and d_n));
end dataflow_1;
```



Task 3. Ans (1)

- $f \leq b \text{ and } ((a \text{ or } (\overline{a} \text{ and } c)) \text{ or } (\overline{b} \text{ and } (c \text{ and } \overline{d})))$;

  

Task 3. Ans (2)


- $g \leq b \text{ and } (c \text{ or } (a_n \text{ and } c_n) \text{ or } (c_n \text{ and } d_n)) ;$



 Task 3. Ans (3)


- However the previous implementation was not “two-level”. A two –level implementation can be either in SOP or POS. SOP or POS can be obtained by expanding the function or using K-map.

$$\begin{aligned} f &= b \cdot ((a + (a' \cdot c)) + (b' \cdot (c \cdot d'))) \\ &= b \cdot ((a+a').(a+c) + b'.c.d') \\ &= b \cdot (a + c + b'.c.d') \\ &= b.a + b.c + b.b'.c.d' \\ &= b.a + b.c \end{aligned}$$



$$f = b.a + b.c$$
 
$$\begin{aligned} g &= b \cdot (c + (a' \cdot c') + (c' \cdot d')) \\ &= b \cdot ((c+a').(c+c') + c'.d') \\ &= b \cdot (c + a' + c'd') \\ &= b.c + a'.b + bc'd' \end{aligned}$$



$$g = b.c + a'.b + bc'd'$$

Task 4


- Write a high-level behavioral VHDL description for a 1-bit full adder.
- Write a structural VHDL description for a 1-bit adder-subtractor. Make use of the 1-bit full adder above as a component.
- Write a high-level behavioral VHDL description for a 1-bit adder-subtractor.

Task 4. Ans (1)

```
-- 1-bit Full Adder: Dataflow  
library ieee;  
use ieee.std_logic_1164.all;
```


```
entity full_adder is  
    port (x, y, z : in std_logic;  
          s, cout : out std_logic);  
end full_adder;
```

```
architecture dataflow_1 of full_adder is  
begin  
    s <= (x xor y) xor z;  
    cout <= (z and (x xor y)) or (x and y);  
end dataflow_1;
```

 

Task 4. Ans (2)

- 1-bit Adder-Subtractor:
 - $M = 1 \rightarrow$ Subtractor
 - $M = 0 \rightarrow$ Adder

 

Task 4. Ans (3)

```
-- 1-bit Adder-Subtractor: Structural
library ieee;
use ieee.std_logic_1164.all;

entity adder_subtractor is
    port (a, b, ci, m : in std_logic;
        s, co : out std_logic);
end adder_subtractor;

architecture struc_1 of adder_subtractor is

signal b_n: std_logic;

component full_adder
    port(x,y,z: in std_logic;
        s,cout: out std_logic);
end component;
...
```

Task 4. Ans (4)

...

```
component XOR2
    port (in1, in2: in std_logic;
          out1: out std_logic);
end component;

begin
    g0: XOR2 port map (m, b, b_n);
    FA: full_adder port map (a, b, ci, s, co);
    -- for bit 0, z or ci of FA will be connected to m,
    for higher order bits, z of FA will be
    -- connected to co of previous bit
end struc_1;
```


Task 4. Ans (5)

```
-- 1-bit Adder-Subtractor: Behavioral
library ieee;
use ieee.std_logic_1164.all;

entity adder_subtractor2 is
    port (a, b, ci, m : in std_logic;
          s, co : out std_logic);
end adder_subtractor2;

architecture behavioral_1 of adder_subtractor2 is
begin
    s <= ((a xor b) xor ci) when m = '1' else
          ((a xor (not b)) xor ci);
    co <= ((ci and (a xor b)) or (a and b)) when m = '1' else
          ((ci and (a xor (not b))) or (a and (not b)));
end behavioral_1;
```