



Tutorial 7

Registers and RTL

CO 2206 Computer Organization

Task 1. Register

- Knowing the function of a D flip-flop with enable, complete the following timing diagram (for the outputs). Assume initially $Q=0$ and $Q'=1$.

  

Task 2. Shift Register

- Modify the 4-bit universal shift register on Slide 19, Chapter 7, such that the functions are:
 - when $s_1s_0 = 00$,
 - no change of states
 - when $s_1s_0 = 01$,
 - parallel load
 - when $s_1s_0 = 10$,
 - shift right
 - when $s_1s_0 = 11$,
 - shift left


Task 3. Register Cell Design

- Draw the circuit diagram to implement the ad-hoc register cell design on Slide 41, Chapter 7
- By referring to the ad-hoc design above, design (and draw the circuit of) a register cell to implement the following register transfer:
 - Op1: $A \leftarrow A'$
 - Op2: $A \leftarrow A + B$
 - Op3: $A \leftarrow A - B$
 - Assume that
 - Only one of Op1, Op2, Op3 is equal to 1
 - For Op1, Op2, Op3 equal to 0, A remains unchanged
 - You can use NOT gate(s) and a Full Adder in your design.

Task 4. Mux-Based Transfer

- Determine the value for the select (S_2, S_1, S_0) signals and load (L_2, L_1, L_0) signals to perform the following register transfer operations:

- $R_0 \leftarrow R_1$
- $R_1 \leftarrow R_2$
- $R_1 \leftarrow R_0, R_2 \leftarrow R_0$

 

Task 5. RTL

• Express the following statement in *RTL*

```
if (ABC = 001) then
(R0 = R1) else if
(ABC = 010) then (R0
= R2) else if (ABC =
011) then (R0 = R3)
else if (ABC = 101)
then (R0 = R0 OR R1)
```

Operation	Text RTL
Combinational Assignment	=
Register Transfer	←
Addition	+
Subtraction	-
Bitwise AND	^
Bitwise OR	∨
Bitwise XOR	⊕
Bitwise NOT	—
Shift left (logical)	sl
Shift right (logical)	sr
Vectors/Registers	A(3:0)
Concatenation	

Task 6. Serial Register Operation

- Modify the circuit on Slide 59 of Chapter 7 to perform a serial operation of the following logic function:
 - $B = A' B$ where A and B are both 16-bit

Task 7

- **Task 7:** Use 4-bit binary counter with synchronous parallel load (in block diagram) and logic gates to design the following counters:
 - a. Modulo-3 that counts 0,1,2 repeatedly
 - b. Modulo-6 that counts 2,3,4,5,6,7 repeatedly